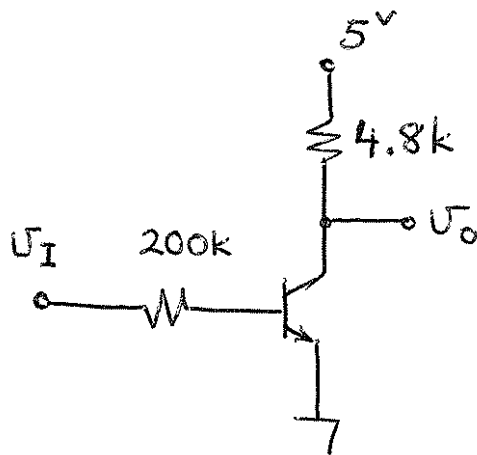


Problem Set 4
Not graded

1.



$$\beta = 100$$

$$V_{BE(ON)} = 0.6V$$

$$V_{CE(SAT)} = 0.2V$$

plot U_O vs U_I

for $0 \leq U_I \leq 5V$

2. Draw the energy band diagram of a pnp bipolar junction transistor that is in active state. Show the flow of electrons and holes. Show the base-emitter and base-collector voltages.
3. Problem 5.5
4. Problem 5.7
5. Problem 5.15 (a)
6. Problem 5.15 (b)
7. For the following circuits, determine the state of each diode and transistors. Calculate all voltages and currents given in the figures.

BJT parameters $\beta=100$, $\beta_R=2$, $V_{BE(ON)} = 0.7V$ $V_{CE(SAT)} = 0.2V$
 $V_{EB(ON)} = 0.7V$ $V_{EC(SAT)} = 0.2V$

Diode parameters $V_\gamma = 0.7V$

