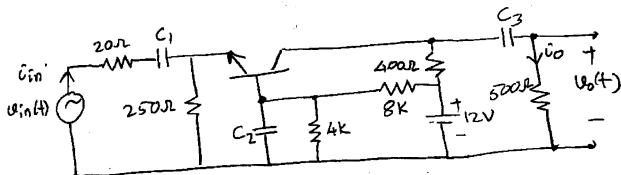


Question 2 (20 points)




At the circuit given above, all the capacitors are very large, $\beta=100$, $V_{BE}=0.8$ Volts and $n=1$. Temperature of the transistor junction is 300 °K. Please answer the following:

- (6 points) Find the state and the bias of the transistor (Voltages and currents of the transistor),
- (7 points) Find the current gain of the amplifier measured as i_o/i_{in} as shown at the figure assuming that the transistor is at forward active state.
- (7 points) Find the voltage gain of the transistor in dB measured as v_o/v_{in} again assuming that the transistor is at forward active state.

a-)

Alternatively for (a)

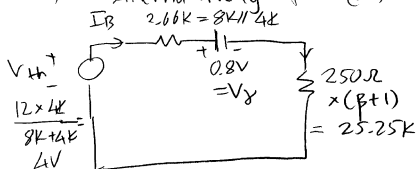

$$I_B = \frac{4 - 0.8}{27.9166k} = 114.63 \mu A$$

$$I_C = \beta I_B = 11.46 mA$$

$$I_E = (\beta + 1) I_B = 11.58 mA$$


$$V_{CE} = 12 - 0.65 \times 11.46 = 4.475 V$$

Question 3 (20 points)

Consider the differential amplifier shown in the figure. The two n-channel depletion-mode MOSFETs are identical with $K_n = 2\text{mA/V}^2$, $V_{TH} = -2\text{ Volts}$ and $\lambda=0$.

- (10 points) Determine the Q-point and find V_{GS1Q} , V_{GS2Q} , I_{D1Q} , I_{D2Q} , V_{DS1Q} and V_{DS2Q} at the common-mode input equal to 0 Volts.
- (10 points) Determine the differential gain A_d (in dB) and the common-mode rejection ratio (CMRR, in dB)

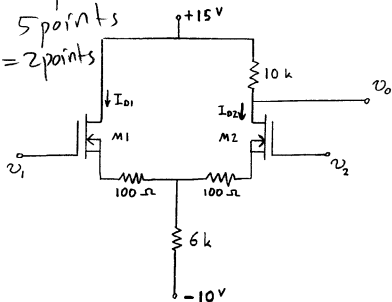$A_{cm} \rightarrow 3 \text{ points}$
 $A_d \Rightarrow 5 \text{ points}$
 $CMRR = 2 \text{ points}$



(a) $V_{GS1Q} =$	$V_{GS2Q} =$	$I_{D1Q} =$	$I_{D2Q} =$
$V_{DS1Q} =$	$V_{DS2Q} =$		
(b) $A_d(\text{dB}) =$	$CMRR(\text{dB}) =$		

Q-3 - D.C. solution

①
DC

$$V_{GS} + 100 I_D + 6000 \times 2 I_D = 10 V$$

$$V_{GS} + 12100 I_D = 10 V$$

$$V_{GS} + 12100 K_n [V_{GS} + 2]^2 = 10$$

$$V_{GS} + 12100 \times 2 \times 10^{-3} [V_{GS}^2 + 4V_{GS} + 4] = 10$$

$$V_{GS} + 24.2 [V_{GS}^2 + 4V_{GS} + 4] = 10$$

$$V_{GS} + 24.2 V_{GS}^2 + 96.8 V_{GS} + 96.8 - 10 = 0$$

$$24.2 V_{GS}^2 + 97.8 V_{GS} + 86.8 = 0$$

$$V_{GS_{1,2}} = \frac{-b}{2a} \pm \frac{\sqrt{b^2 - 4ac}}{2a} = -2.02066 \pm 0.70448$$

$$= -1.31618 V - \textcircled{2.72514 V} \text{ beyond cut-off}$$

$$\approx -1.3162$$

hence discarded

but if you neglect $R = 100 \Omega$ in the DC-analysis

$$V_{GS} + 12000 I_D = 10 \Rightarrow V_{GS} + 24 [V_{GS} + 2]^2 = 10$$

$$V_{GS} + 24 [V_{GS}^2 + 4V_{GS} + 4] - 10 = 0$$

$$24 V_{GS}^2 + 97 V_{GS} + 86 = 0$$

$$V_{GS_{1,2}} = \frac{-b}{2a} \pm \frac{\sqrt{b^2 - 4ac}}{2a} = -2.02083 \pm 0.70741 \Rightarrow$$

$$V_{GS_{1,2}} = -1.3, -2.7 \Rightarrow V_{GS} = -1.3$$

$$\Rightarrow g_m = 2 K_n (V_{GS} + 2) = 0.02828 \text{ siemens}$$

$$I_D = 2 \times 10^{-3} (-1.3 + 2)^2 = 1 \text{ mA} \quad \text{or more precisely if needed}$$

$$I_D = 2 \times 10^{-3} (-1.3162 + 2)^2 = 0.9352 \text{ mA}$$

$$\Rightarrow g_m = 0.002735 \text{ siemens}$$

Q. 3

①

A.C. analysis (formal)

$$V_1 = V_{cm} + \frac{V_d}{2} \quad V_2 = V_{cm} - \frac{V_d}{2}$$

$$V_d = V_1 - V_2 \quad V_{cm} = \frac{V_1 + V_2}{2}$$

$$g_m u_{gs1} + g_m u_{gs2} = V_x / R_o \Rightarrow g_m (u_{gs1} + u_{gs2}) = \frac{V_x}{R_o}$$

$$V_1 - (1 + g_m R) u_{gs1} - V_x = 0$$

$$u_{gs1} + u_{gs2} = \frac{V_x}{g_m R_o}$$

$$V_2 - (1 + g_m R) u_{gs2} - V_x = 0$$

$$g_m R (u_{gs1} + u_{gs2}) = \frac{V_x R}{R_o}$$

$$V_1 + V_2 - (1 + g_m R) (u_{gs1} + u_{gs2}) - 2V_x = 0$$

$$V_1 + V_2 - (u_{gs1} + u_{gs2}) - g_m R (u_{gs1} + u_{gs2}) - 2V_x = 0$$

$$V_1 + V_2 - \frac{V_x}{g_m R_o} - \frac{V_x R}{R_o} = 2V_x$$

$$V_1 + V_2 = V_x \left[2 + \frac{1}{g_m R_o} + \frac{R}{R_o} \right] \Rightarrow$$

$$V_x = \frac{V_1 + V_2}{2 + \frac{1}{g_m R_o} + \frac{R}{R_o}}$$

$$V_2 - V_x = V_{cm} - \frac{V_d}{2} - V_x = V_{cm} - \frac{V_d}{2} - \frac{V_1 + V_2}{2 + \frac{1}{g_m R_o} + \frac{R}{R_o}}$$

$$V_2 - V_x = V_{cm} \left[1 - \frac{2}{2 + \frac{1}{g_m R_o} + \frac{R}{R_o}} \right] - \frac{V_d}{2}$$

(2)

$$V_2 - V_x = V_{cm} \left[\frac{Z + \frac{1}{g_m R_0} + \frac{R}{R_0} - Z}{2 + \frac{1}{g_m R_0} + \frac{R}{R_0}} \right] - \frac{V_d}{2}$$

$$V_2 - V_x = V_{cm} \frac{1}{R_0} \cdot \frac{\frac{1}{g_m} + R}{2 + \frac{1}{g_m R_0} + \frac{R}{R_0}} - \frac{V_d}{2}$$

$$\textcircled{1} \quad v_{gs2} = \frac{V_2 - V_x}{1 + g_m R} = \frac{1}{(1 + g_m R)} \left[\frac{V_{cm} \frac{1}{R_0} \left(\frac{1}{g_m} + R \right)}{2 + \frac{1}{g_m R_0} + \frac{R}{R_0}} - \frac{V_d}{2} \right]$$

$$v_{gs2} = V_{cm} \cdot \frac{\frac{1}{g_m} [1 + \cancel{g_m R}]}{[1 + \cancel{g_m R}] R_0} \cdot \frac{1}{2 + \frac{1}{g_m R_0} + \frac{R}{R_0}} - V_d \frac{1}{2(1 + g_m R)}$$

$$v_{gs2} = V_{cm} \frac{1}{g_m R_0} \frac{1}{2 + \frac{1}{g_m R_0} + \frac{R}{R_0}} - V_d \frac{1}{2(1 + g_m R)}$$

$$v_{gs2} = V_{cm} \frac{1}{2g_m R_0 + 1 + g_m R} - V_d \frac{1}{2(1 + g_m R)}$$

$$v_o = -g_m v_{gs2} R_0 = V_d \frac{\overbrace{g_m R_0}^{A_d}}{2(1 + g_m R)} - \frac{\overbrace{g_m R_0}^{A_{cm}}}{1 + 2g_m R_0 + g_m R} V_{cm}$$

$$\Rightarrow CMRR = \frac{1 + 2g_m R_0 + \cancel{g_m R}}{2(1 + g_m R)}$$

=

(3)

$$A_d = \frac{g_m R_D}{2(1+g_m R)} = \frac{0.002735 \times 10^4}{2(1+0.2735)} = 10.7389$$

$$= 20.62 \text{ dB}$$

$$|A_{cm}| = \frac{g_m R_D}{1+g_m(2R_D+R)} = \frac{2.735 \times 10^{-3} \times 10^4}{1+2.735 \times 10^{-3} [12000+100]} = 27$$

$$= \frac{27.35}{34.093} = 0.8022 \quad -1.91 \text{ dB}$$

$$CMR = \frac{1+2g_m R_D+g_m R}{2(1+g_m R)} = \frac{1+g_m(2R_D+R)}{2(1+g_m R)}$$

$$= \frac{27.35}{2.547} = 10.73 = 20.62 \text{ dB}$$

alternatively,



$$CMR = \frac{|A_d|}{|A_c|} = 20.62 - (-1.92) = 22.53 \text{ dB}$$

Q-3

AS

Alternative solution =

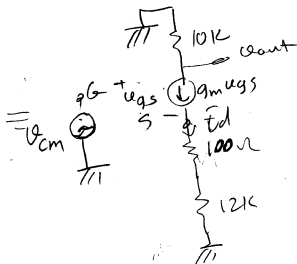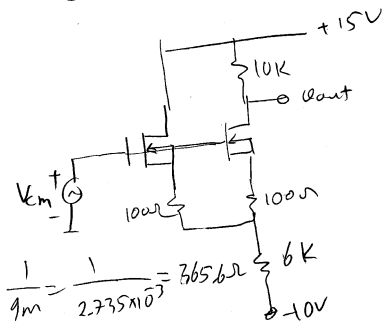
A common mode \Rightarrow the equivalent circuit becomes



$$i_d = v_{cm} \frac{1}{\frac{1}{g_m} + 12.1k} \Rightarrow A_{cm} = \frac{v_{out}}{v_{cm}} = \frac{10000}{365.6 + 12100} \approx 10$$

$$A_{cm} = 28022 \Rightarrow -1.91 \text{ dB}$$

(2)
45

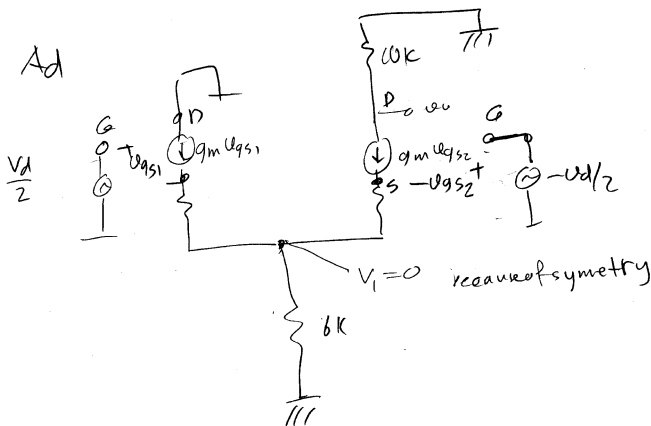

$$v_o = -(-g_m v_{gs}) = g_m v_d/2$$

$$i_{d2} = \frac{v_d}{2} \cdot \frac{1}{\frac{1}{g_m} + 100\Omega} = \frac{v_d}{2(365.6 + 100)} = \frac{v_d g_m}{(1 + g_m 100)2}$$

$$\frac{v_o}{v_d} = \frac{10000}{2(465.6)} = 10.7388 = 20.619 \text{ dB}$$

$\frac{v_o}{v_d} = \frac{g_m R_D}{(1 + g_m R)2}$

$$CMRR = \frac{A_d}{A_{cm}} = 20.619 - (-191) = 22.53 \text{ dB}$$