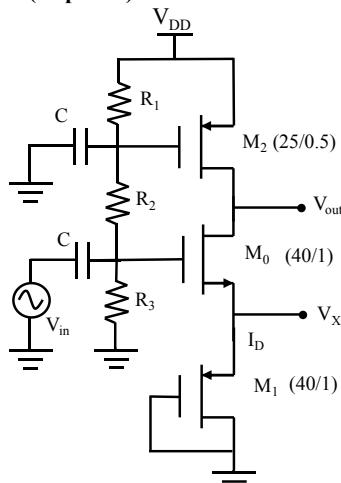



**Duration: 120 minutes.** Call 0312-290-3193 if your connection fails and you cannot reconnect.

**1. (30 points)**

- a. Calculate the Q points, small signal parameters for  $M_{0-1-2}$  and verify that they are in SAT. Consider the channel length modulation ( $\lambda \neq 0$ ) in this part also.

- b. Calculate  $V_{out}/V_{in}$  first symbolically and then find the numerical value.


**Hint:** You may consider the impedances looking into  $M_1$  from  $V_x$  and  $M_2$  from  $V_{out}$ .

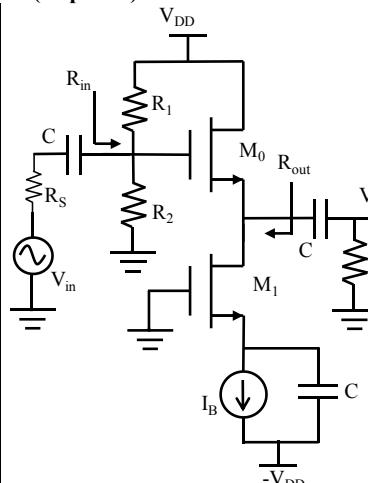**2. (30 points)**

- a. Calculate the small signal parameters for  $M_1$  and  $M_0$  assuming that they are in SAT

- b. Find  $V_{out}/V_{in}$ ,  $R_{out}$ , and  $R_{in}$  first symbolically and then find the numerical value

**Hint:** You may consider the impedance looking into  $M_1$  from  $V_{out}$ .

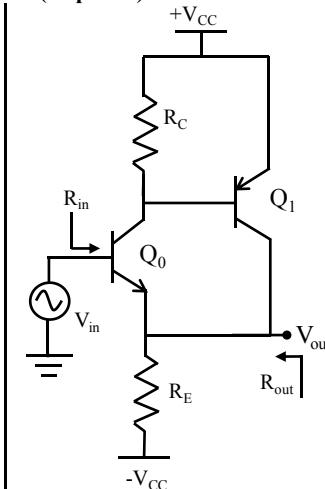**3. (40 points)**

$$\begin{aligned} +V_{CC} &= 5V \\ -V_{CC} &= -5V \\ \beta_0 &= \beta_1 = 50 \\ R_C &= 10k\Omega \\ R_E &= 2k\Omega \\ V_A &= \infty \\ V_{BEon0} &= 0.7V \\ V_{CESAT0} &= 0.2V \\ V_{EBon1} &= 0.7V \\ V_{ECSAT1} &= 0.2V \end{aligned}$$

- a. Find the Q points, small signal parameters for  $Q_0$  and  $Q_1$ , and verify transistor regions (states).

- b. Assuming Q point remains the same for  $Q_0$ , find  $R_{in}$  and  $R_{out}$  symbolically if  $Q_1$  is removed.  $V_{out}$  still remains on  $R_E$ , provide just expression no numbers.

- c. Find  $V_{out}/V_{in}$ ,  $R_{in}$ , and  $R_{out}$  for this circuit first symbolically and then find the numerical value. Comment on the effect of  $Q_1$  on  $R_{in}$  and  $R_{out}$ .

**On your 1<sup>st</sup> solution page write and sign:**

I pledge on my honor that I have not given or received any unauthorized assistance on this examination.

**Submission process:**

Solve each question on a new page. Scan your solutions into a single pdf file, upload it to Moodle using "Midterm Exam 2 upload" tab, and email to "eee313.spring19@gmail.com". The subject line and the name of the file should be "Midterm 2 -Your ID#-Name Surname".

**BJT:** in Forward Active region, B-E forward B-C reverse biased:  $I_C = I_S(e^{\frac{V_{BE}}{V_T}} - 1)$   
 $\alpha I_E = I_C, \quad I_C = \beta I_B, \quad \alpha = \beta / (\beta + 1)$

$$r_\pi = \frac{V_T}{I_{BQ}}, g_m = \frac{I_{CQ}}{V_T}, r_o = \frac{V_A}{I_{CQ}}, V_T = 26mV$$

**nMOS:** Non-Saturation ( $V_{DS} < V_{GS} - V_{TN}$ )


$$I_D = K_N [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2](1 + \lambda V_{DS})$$

SAT ( $V_{DS} > V_{GS} - V_{TN}$ ):  $I_D = K_N (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$

for pMOS replace  $V_{GS}$  with  $V_{SG}$ ,  $-V_{TN}$  with  $V_{TP}$ , and  $V_{DS}$  with  $V_{SD}$

$$g_m = 2K_N (V_{GSQ} - V_{th}) = 2\sqrt{K_N I_{DQ}}, r_o = \frac{1}{\lambda I_{DQ}}$$

Q.1. (30 points)

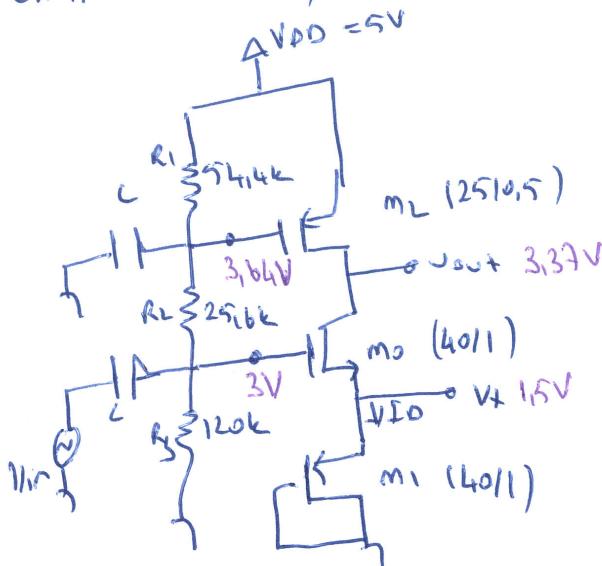

$$k'_n = 0.1 \text{ mA/V}^2 \quad V_{thn} = 0.5 \text{ V}$$

$$k'_p = 0.1 \text{ mA/V}^2 \quad V_{thp} = 0.5 \text{ V}$$

$$\lambda_2 = 0.05 \text{ V}^{-1}, \lambda_0 = \lambda_1 = 0$$

$$I_D = \frac{0.1}{2} \frac{40}{1} (3 - 1.5 - 0.5)^2 = 2 \text{ mA}$$

a) 9 points. (15 points)

$$V_{b1} = \frac{120}{200} \cdot 5 = 3 \text{ V} \quad (02)$$

$$V_{b2} = \frac{145.6}{200} \cdot 5 = 3.64 \text{ V}$$

$$\lambda_0 = \lambda_1 = 0$$

M<sub>0</sub> - M<sub>1</sub> SAT

$$\frac{0.1}{2} \cdot \frac{40}{1} (3 - V_L - 0.5)^2 = \frac{0.1}{2} \frac{40}{1} (V_L - 0.5)^2$$

$$(2.5 - V_L)^2 = (V_L - 0.5)^2$$

$$2.5 - V_L = V_L - 0.5 \quad \cancel{2.5 - V_L = 0.5 - V_L} \quad ?$$

$$\boxed{V_L = 1.5 \text{ V}} \quad (03)$$

$$\boxed{I_D = 2 \text{ mA}} \quad (02)$$

$$\text{for } M_2 \quad I = \frac{0.1}{2} \frac{2.5}{0.5} (5 - 3.64 - 0.5)^2 \cdot (1 + 0.05 \cdot \frac{(5 - V_{out})}{V_{th}}) \quad (03)$$

$$I = 1.85 \cdot (1 + 0.05 \cdot V_{SD})$$

$$V_{SD} = \frac{1.63}{2} \Rightarrow V_{out} = 5 - 1.63 \Rightarrow \boxed{V_{out} = 3.37 \text{ V}}$$

M<sub>1</sub>  
already in SAT.

$$\frac{M_1}{1.5 - 0.5} < 3.37 - 1.5$$

$$\frac{M_2}{5 - 3.64 - 0.5} < 1.65 \quad (02)$$

transistor verification  
operator verification

$$g_m = 2 \sqrt{k_n I_D} \\ = 2 \sqrt{\frac{0.1}{2} \cdot 40 \cdot 2}$$

$$g_m = 2 \sqrt{\frac{0.1}{2} \cdot 40 \cdot 2}$$

$$g_{m2} = 4 \text{ mA/V}$$

$$g_{m2} = 2 \sqrt{\frac{0.1}{2} \cdot 50 \cdot 2}$$

$$g_{m2} = 4.47 \text{ mA/V}$$

$$r_{o2} = \frac{1}{2 I_D} = \frac{1}{0.05 \cdot 2} = 10 \text{ k}\Omega$$

(03) → S.S. parameter calculation.

1. a.)  $\lambda_2$  ignored in DC analysis. mat 9 points.

$$\underline{M2}$$

$$I_D = \frac{V_{G2}}{2} = \frac{3}{2} \text{ mA} \quad (02)$$

$$V_{G2} = 3.66 \text{ V}$$

$$\underline{M2}$$

$$I_D = \frac{0.1}{2} \cdot \frac{25}{0.5} (5 - 3.66 - 0.5)^2 = 1.65 \text{ mA} \quad (02)$$

$$\underline{M3}$$

$$1.65 \text{ mA} = \frac{0.1}{2} \cdot \frac{40}{1} \cdot (3 - V_x - 0.5)^2 \quad (02)$$

$$1.65 = 2 \cdot (2.5 - V_x)^2$$

$$2.5 - V_x = \pm 0.9 \text{ b}$$

$$V_x = 1.54 \text{ V} \quad \text{or} \quad V_x = 3.46 \text{ V} \quad \text{which one to pick is not obvious here.}$$

$$\underline{M1} \quad (01)$$

already in SAT

$$g_m = 2\sqrt{\frac{0.1}{2} \cdot 40 \cdot 1.65}$$

$$g_m = 3.8 \text{ mA/V}$$

$$\underline{M3}$$

state: cannot be verified

$$g_{m3} = g_m = 3.8 \text{ mA/V}$$

(03) S.S. parameters.

$$\underline{M2}$$

state: cannot be verified

$$g_{m2} = 2\sqrt{\frac{0.1}{2} \cdot 350 \cdot 1.65}$$


$$g_{m2} = 4.3 \text{ mA/V}$$

$$r_o = \frac{1}{g_{m2} \cdot 1.65} = 10.8 \text{ k}\Omega$$

Since the DC potential cannot be calculated @ Vout with  $\lambda_2 = 0$   
 states of  $m_2$  and  $m_3$  cannot be verified. Also which solution to  
 pick for  $V_x$  DC point is not obvious.

b) Calculate  $\frac{V_{out}}{V_{in}}$


looking into the drain of  $M_2$ .

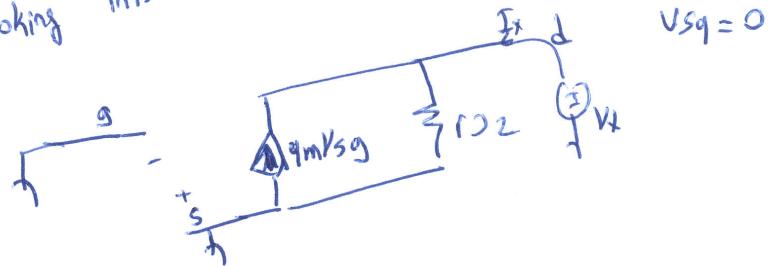

$$\frac{V_T}{I_T} = \beta_2$$


③

looking in the source of  $M_1$

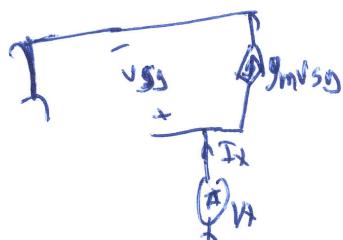

$$V_T = V_{SG} \Rightarrow \frac{V_T}{I_T} = \frac{1}{g_m 1}$$

③

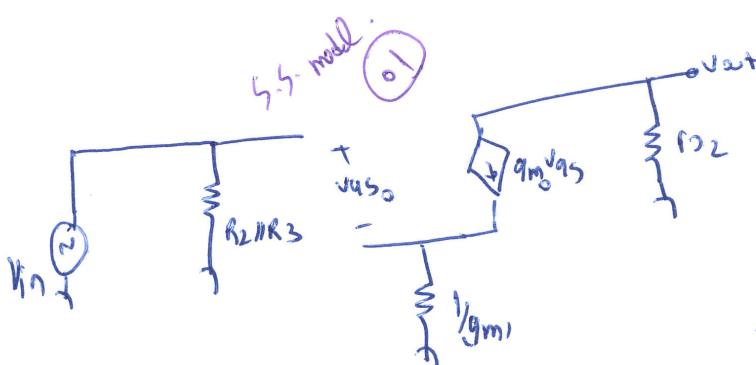

$$V_{out} = -g_m V_{SG} \quad \text{for } ①$$

$$V_{in} = V_{SG} + g_m V_{SG0} \cdot \frac{1}{g_m 1}$$


$$V_{in} = V_{SG} \left( 1 + \frac{g_m 0}{g_m 1} \right) \quad ②$$

$$V_{SG} = \frac{V_{in}}{1 + \frac{g_m 0}{g_m 1}}$$

$$V_{out} = -g_m \cdot \frac{V_{in}}{1 + \frac{g_m 0}{g_m 1}} \cdot R_2 \Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{-g_m \beta_2}{1 + \frac{g_m 0}{g_m 1}} = \frac{-4 \cdot 10}{1 + 1} = \boxed{A_v = -20 \frac{V}{V}}$$

② plugging in numbers.

b) alternative way.

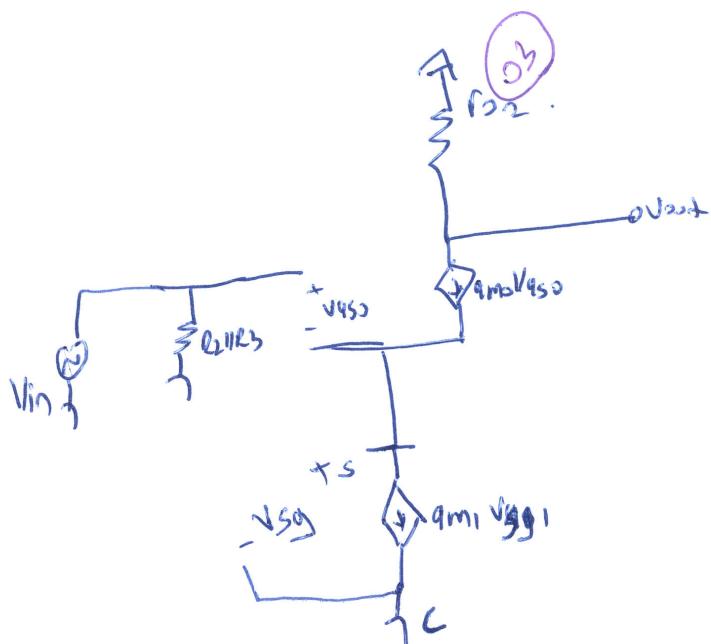

(03) model

$$V_{2+} = -q_{m0} V_{qso} \quad (01)$$

$$q_{m0} V_{qso} = q_{m1} V_{gg1} \quad (02)$$

$$V_{qso} = V_{gg1} \quad (03)$$

$$V_{in} = 2 V_{qso} = V_{qso} + V_{gg1}$$


$$V_{qso} = \frac{1}{2} V_{in} \quad (02)$$

$$V_{2+} = -q_{m0} \cdot \frac{1}{2} V_{in} \quad (01)$$

$$A_v = \frac{V_{2+}}{V_{in}} = -4 \cdot \frac{1}{2} \cdot 10 \quad (02)$$

$$\boxed{A_v = -20 \text{ V}}$$

Q.2 (30 points)

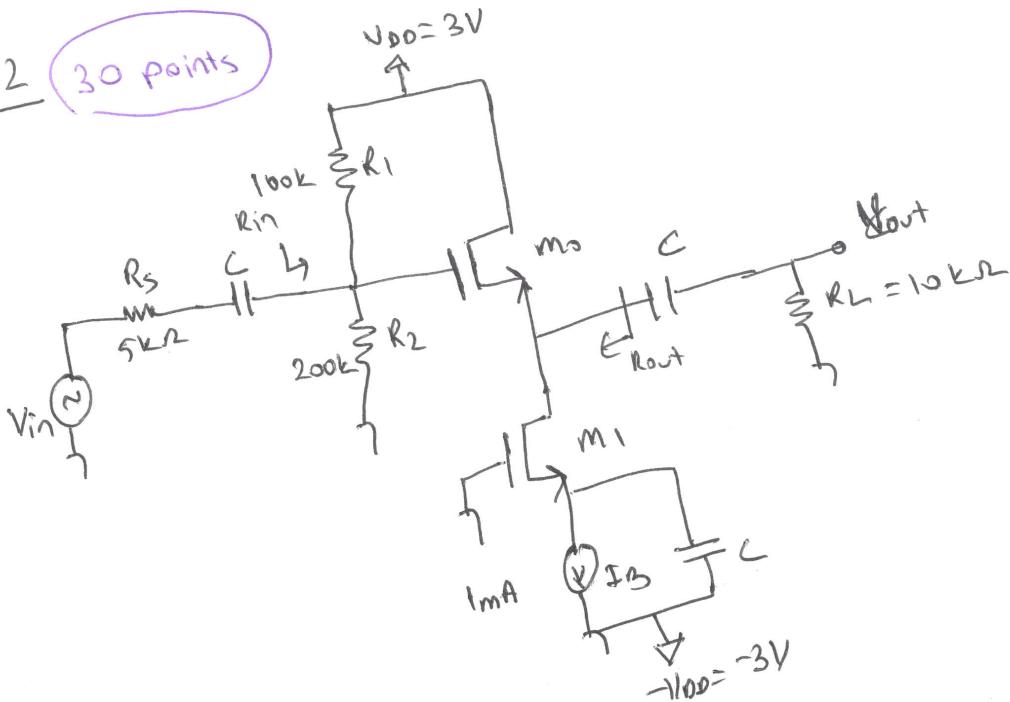

$$\begin{aligned}\Delta_0 &= 0,02 \text{ V}^{-1} \\ \beta_1 &= 0,04 \text{ V}^{-1} \\ k_{m_0} &= k_{m_1} = \frac{0,5 \text{ mA}}{\sqrt{2}} \\ V_{TN} &= 0,8 \text{ V}\end{aligned}$$

a) ⑤  $I_{D_{M_0}} = I_{D_{M_1}} = I_B = 1 \text{ mA}$  ①


$$g_{m_0} = 2 \sqrt{0,5 \cdot 1} = 1,41 \frac{\text{mA}}{\sqrt{\text{V}}}$$
 ①

$$g_{m_1} = 2 \sqrt{0,5 \cdot 1} = 1,41 \frac{\text{mA}}{\sqrt{\text{V}}}$$
 ①

$$r_{o_0} = \frac{1}{0,02 \cdot 1} = 50 \text{ k}\Omega$$
 ①

$$r_{o_1} = \frac{1}{0,04 \cdot 1} = 25 \text{ k}\Omega$$
 ①

b)

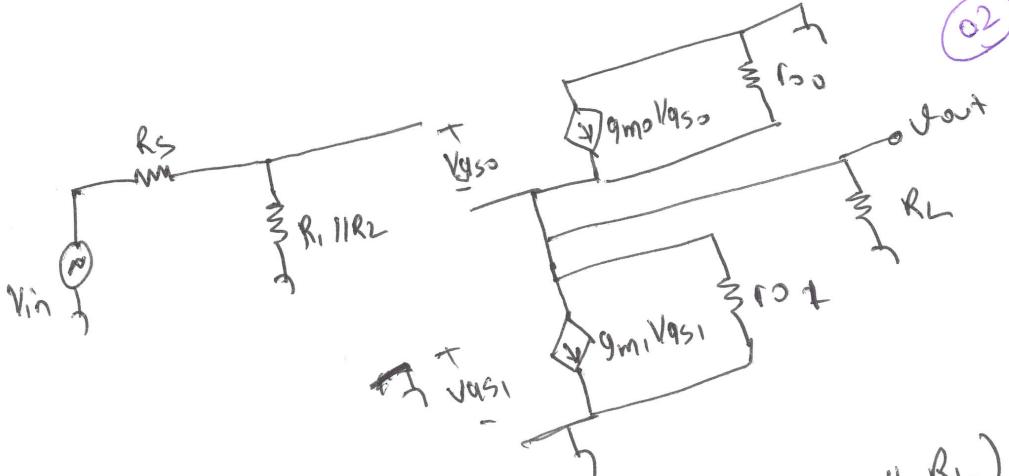

② S.S. model.

$$V_{gs1} = 0$$

$g_m V_{gs} \rightarrow$  open circuit.  
only  $r_{o_1}$  is seen looking  
into M1

$$V_{out} = g_{m_0} V_{gs_0} (r_{o_0} \parallel r_{o_1} \parallel R_L)$$
 ②

$$1/g_{s0} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S} \cdot V_{in} - g_{m_0} V_{gs_0} (r_{o_0} \parallel r_{o_1} \parallel R_L)$$
 ②

$$V_{gs_0} (1 + g_{m_0} (r_{o_0} \parallel r_{o_1} \parallel R_L)) = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S} \cdot V_{in}$$

$$1/g_{s0} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S} \cdot \frac{1}{1 + g_{m_0} (r_{o_0} \parallel r_{o_1} \parallel R_L)} \cdot V_{in}$$
 ②

$$V_{out} = g_{m_2} V_{g_{s_2}} (f_{o_2} || f_{o_1} || R_L)$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 || R_2}{R_1 || R_2 + r_s} \cdot \frac{g_{m_2} (f_{o_2} || f_{o_1} || R_L)}{1 + g_{m_2} (f_{o_2} || f_{o_1} || R_L)}$$


$$R_1 || R_2 = 100 || 200 = 66,7 \text{ k}\Omega$$

$$f_{o_2} || f_{o_1} || R_L = 50 || 25 || 10 = 6,25 \text{ k}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{66,7}{66,7 + 1} \cdot \frac{1,41 \cdot 6,25}{1 + 1,41 \cdot 6,25} = 0,93 \cdot 0,898$$

$$A_v = 0,84 \frac{\text{V}}{\text{V}}$$

$$R_{in} = R_1 || R_2 = 66,7 \text{ k}\Omega \quad (02)$$

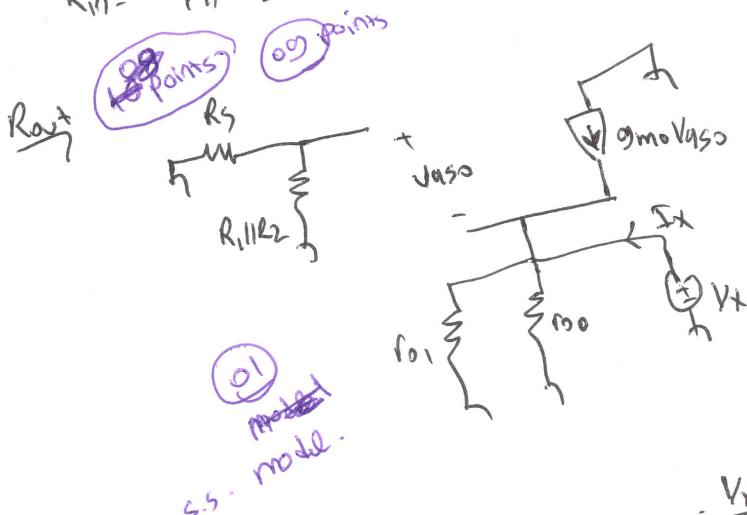

$$V_{g_{s_2}} = 0 - V_S = -V_S \quad (02)$$

$$V_X = +V_S \quad (02)$$

$$-I_X + \frac{V_X}{r_{o_2}} + \frac{V_X}{r_{o_1}} - g_{m_2} V_{g_{s_2}}$$

$$I_X = \frac{V_X}{r_{o_2}} + \frac{V_X}{r_{o_1}} + g_{m_2} V_S$$


$$R_{out} = \frac{V_X}{I_X} = \left( \frac{1}{r_{o_2}} + \frac{1}{r_{o_1}} + g_{m_2} \right)$$

$$R_{out} = f_{o_2} || f_{o_1} || \frac{1}{g_{m_2}} =$$

$$R_{out} = 50 || 25 || \frac{1}{1,41} = 0,68 \text{ k}\Omega = 680 \text{ }\Omega \quad (02)$$

### Q3 Solution

a) Assume both transistors are F.A.

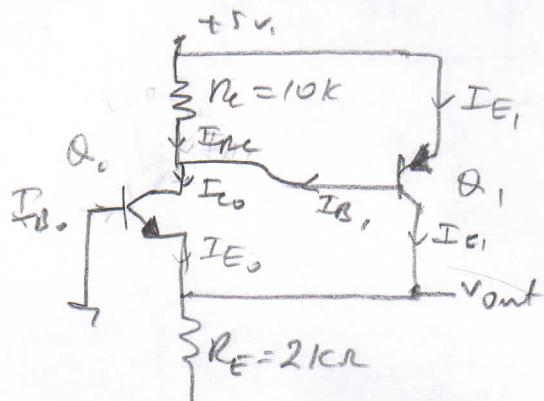

$$I_{B_1} = 50 \frac{I_{B_0}}{R_E} - 0.07$$

$$= 50 \times 0.002215 - 0.07$$

$$= 0.04075 \text{ mA} = 40.75 \mu\text{A}$$

$$\Rightarrow I_{C_1} = 2.038 \text{ mA}$$

$$V_{CE_1} = V_{C_0} - V_{E_1} = (5 - 0.7) - (-0.7) = 5 \text{ V} > 0.2 \text{ V}$$


$$V_{EC_1} = V_{E_1} - V_{C_1} = 5 - V_{E_1} = 5 - (-0.7) = 5.7 > 0.2 \text{ V}$$

$$r_{\pi_1} = \frac{0.026}{0.04075} = 0.638 \text{ k}\Omega \quad r_{\pi_0} = \frac{0.026}{0.002215} = 11.74 \text{ k}\Omega$$

$$g_{m_1} = \frac{50}{0.638} = 79.6 \text{ mA/V} \quad g_{m_0} = \frac{50}{11.74} = 4.26 \text{ mA/V}$$

2p for either  $r_{\pi}$ 's or  $g_{m}$ 's


$I_{C_0} 4P$	$\left. \begin{array}{l} I_{C_1} 4P \\ V_{CE_0} 2+1 \\ V_{CE_1} 2+1 \end{array} \right\} 14P \right)$
$I_{C_1} 4P$	

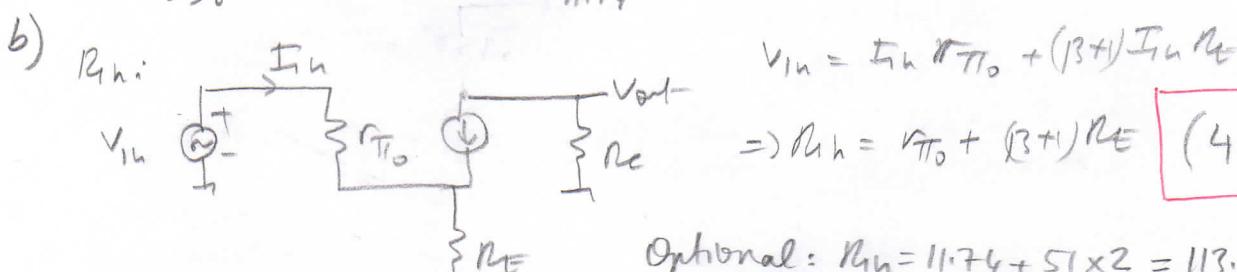

$$V_{in} = I_{in} R_{\pi_0} + (\beta + 1) I_{in} R_E$$

$$\Rightarrow R_{in} = R_{\pi_0} + (\beta + 1) R_E \quad (4P)$$
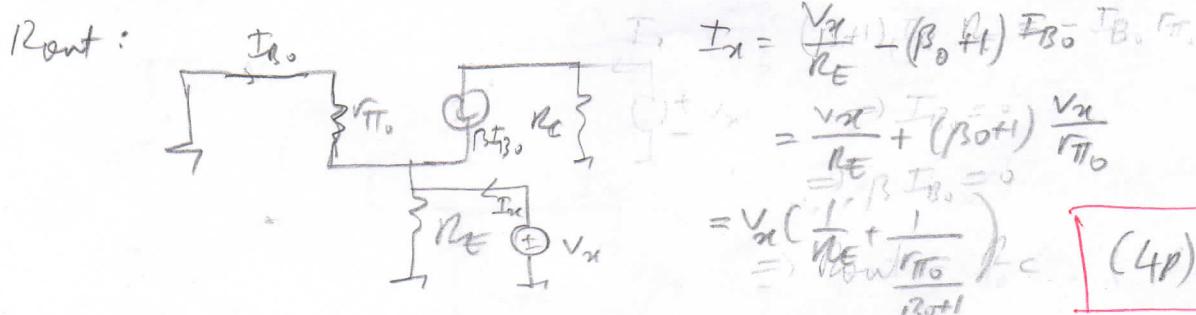
$$\text{Optional: } R_{in} = 11.74 + 51 \times 2 = 113.7 \text{ k}\Omega$$



$$I_C = I_{in} = \frac{V_{in}}{R_E} + (\beta + 1) I_{B_0} = \frac{V_{in}}{R_{\pi_0}} + (\beta + 1) \frac{V_{in}}{R_{\pi_0}} = \frac{V_{in}}{R_{\pi_0}} \left( \frac{1}{\beta + 1} + 1 \right)$$


$$= \frac{V_{in}}{R_{\pi_0} + R_E} \quad (4P)$$

Optional:

$$R_{out} = 2 // \frac{11.74}{51} = 2 // 0.23 = 206 \Omega$$

$$= R_{out} = R_E // \frac{R_{\pi_0}}{\beta + 1}$$

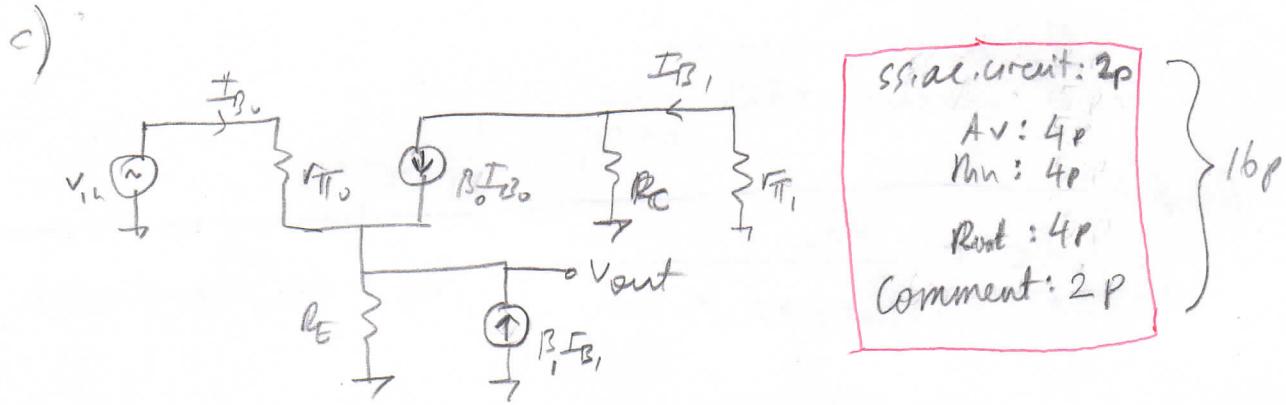\*  $\beta_1$  makes  $R_{in}$  very very large, and  $R_{out}$  very very small, therefore we have feedback  
compared to results in part b).



ssial.circuit: 2p  
Av: 4p  
Rin: 4p  
 Rout: 4p  
Comment: 2p

16p

$$V_{in} = I_{B0} r_{\pi_0} + [(\beta_0 + 1) I_{B0} + \beta_1 I_{B1}] / 2E$$

$$\boxed{I_{B1} = +\beta_0 I_{B0} \frac{R_c}{R_c + r_{\pi_1}}} \Rightarrow V_{in} = I_{B0} r_{\pi_0} + [(\beta_0 + 1) I_{B0} + \beta_1 \beta_0 \frac{R_c}{R_c + r_{\pi_1}} I_{B0}] R_E$$

$$V_{out} = [(\beta_0 + 1) I_{B0} + \beta_1 \beta_0 \frac{R_c}{R_c + r_{\pi_1}} I_{B0}] R_E = [(\beta_0 + 1) I_{B0} + \beta_1 \beta_0 \frac{R_c}{R_c + r_{\pi_1}} I_{B0}] R_E$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{[(\beta_0 + 1) + \beta_1 \beta_0 \frac{R_c}{R_c + r_{\pi_1}}] R_E}{r_{\pi_0} + [(\beta_0 + 1) + \beta_1 \beta_0 \frac{R_c}{R_c + r_{\pi_1}}] R_E}$$

$$r_{\pi_1} = \frac{0.026}{0.00221} = 0.638 \text{ k}\Omega \quad r_{\pi_0} = \frac{0.026}{0.00221} = 11.74 \text{ k}\Omega$$


$$A_v = \frac{[51 + 2500 \times \frac{10}{10 + 0.638}] \times 2}{11.74 + [51 + 2500 \times \frac{10}{10 + 0.638}] \times 2} = \frac{[51 + 2350] \times 2}{11.74 + [51 + 2350] \times 2} = \frac{4802}{4813.7} = 0.9976$$

$$R_{in}: \quad V_{in} = I_{B0} r_{\pi_0} + [(\beta_0 + 1) I_{B0} + \beta^2 \frac{R_c}{R_c + r_{\pi_1}} I_{B0}] R_E$$

$$\Rightarrow R_{in} = r_{\pi_0} + [(\beta_0 + 1) + \beta^2 \frac{R_c}{R_c + r_{\pi_1}}] \times 2 = 4813.7 \text{ k}\Omega \\ = 4.8137 \text{ M}\Omega$$

Rout:

(ignore  $R_E$  first)

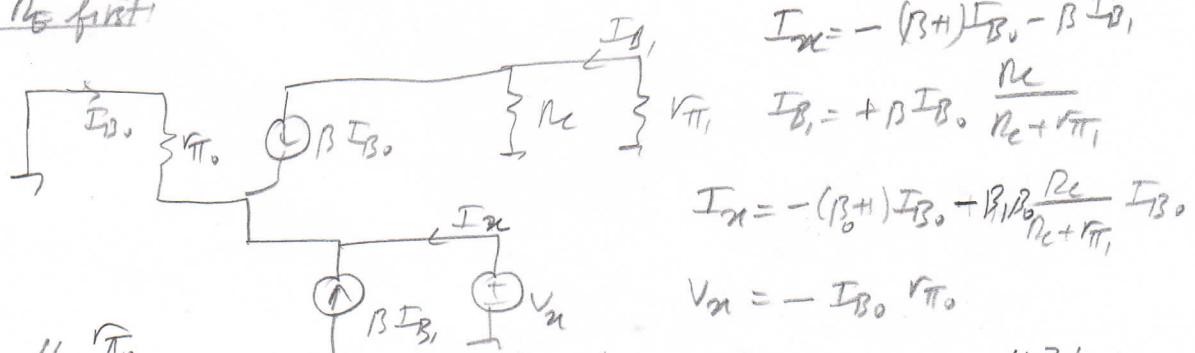

$$I_{in} = -(\beta_0 + 1) I_{B0} - \beta_1 I_{B1}$$

$$I_{B1} = +\beta_1 I_{B0} \frac{R_c}{R_c + r_{\pi_1}}$$

$$I_{in} = -(\beta_0 + 1) I_{B0} - \beta_1 \beta_0 \frac{R_c}{R_c + r_{\pi_1}} I_{B0}$$

$$V_{in} = -I_{B0} r_{\pi_0}$$

$$\frac{V_{in}}{I_{in}} = \frac{-r_{\pi_0}}{(\beta_0 + 1) + \beta_1 \beta_0 \frac{R_c}{R_c + r_{\pi_1}}} = \frac{11.74}{51 + 2500 \times \frac{10}{10 + 0.638}} = \frac{11.74}{2601} = 0.00489 \text{ k}\Omega$$

$$R_{out} = R_E // \frac{r_{\pi_0}}{(\beta_0 + 1) + \beta_1 \beta_0 \frac{R_c}{R_c + r_{\pi_1}}} \\ = 2 // 0.00489 = 0.00488 \text{ k}\Omega \\ = 4.88 \text{ M}\Omega$$