

Name: _____

Section: _____

Signature: _____

EEE 313 Fall 2014-2015

Bilkent University
Department of Electrical and Electronics Engineering
EEE 313 Electronic Circuit Design

Midterm 1

25 October 2014, 10:00
(4 questions, 120 minutes)

- This is a **closed book**, closed notes exam. No cheat sheet allowed.
- All cell-phones should be completely **turned off**.
- Use a calculator for numerical computations. Carry at least **4 significant digits** during calculations. Your final answer should be at least **3 significant digits**.
- Be sure to write the **units** of all numerical results.
- **Show** all work clearly.
- Please put your **final answer** for each part inside a box for easy identification. Do not give multiple answers, they will not be graded.
- Do not remove the **staple** from the exam sheets or separate pages of the exam. All extra pages must be stamped to your exam.
- You may leave the exam room when you are done. However, please do not leave during the **last five minutes** of the exam.
- At the end of the exam, please stay seated until **all** exam papers are collected.

FET equations:

n-channel MOSFET

$$i_D = K_n (v_{GS} - V_{Tn})^2 \quad \text{SAT}$$

$$i_D = K_n [2(v_{GS} - V_{Tn})v_{DS} - v_{DS}^2] \quad \text{NON-SAT}$$

p-channel MOSFET

$$i_D = K_p (v_{SG} + V_{Tp})^2 \quad \text{SAT}$$

$$i_D = K_p [2(v_{SG} + V_{Tp})v_{SD} - v_{SD}^2] \quad \text{NON-SAT}$$

n-channel JFET


$$i_D = \frac{I_{DSS}}{V_p^2} (v_{GS} - V_p)^2 \quad \text{SAT}$$

$$i_D = \frac{I_{DSS}}{V_p^2} [2(v_{GS} - V_p)v_{DS} - v_{DS}^2] \quad \text{NON-SAT}$$

Please do not write below this line


1. 25 pts.	
2. 20 pts.	
3. 25 pts.	
4. 30 pts.	
Total 100 pts.	

 1. (20 points) The input signal V_i is a sinusoid with an amplitude of 20 V. For the diode assume $V_g=0$ V (i.e., V_{on} voltage) and that the diodes are ideal. All resistors are equal to 10 k Ω . Determine the output signal V_o .




2. (20 points) For the following circuit, find the states of the n-channel MOS enhancement mode transistors Q1 and Q2, assuming that $V_{Tn1} = V_{Tn2} = 2.5V$, and $K_{n1} = 4$ $K_{n2} = 1mA/V^2$.

Q ₁ state	Q ₂ state	I _{D1}	I _{D1}	V _S

 

 3. (30 points) Consider the p-channel MOS common-gate circuit in the figure. The transistor parameters are: $V_{TP} = -1$ V, $K_p = 0.5$ mA/V², and $\lambda = 0$. (a) Determine R_S and R_D such that $I_{DQ} = 0.75$ mA and $V_{SDQ} = 6$ V. (b) Determine the input impedance R_i and the output impedance R_o . (c) Determine the load current i_o and the output voltage v_o , if $i_i = 5 \sin(\omega t)$ μ A. Assume all capacitors are very large. V^+ and V^- are applied DC voltages.



4. (30 points) Design the common source circuit below using an n-channel enhancement-mode MOSFET. The quiescent values are to be $I_{DQ} = 5\text{mA}$ and $V_{GSQ} = 4\text{V}$. The transconductance is $g_m = 10\text{mA/V}$. Let $R_L = 1\text{k}\Omega$, $A_v = v_{out}/v_{in} = -5$, $R_{in} = 48\text{k}\Omega$. Find:

- (10 points) R_1 and R_2
- (10 points) R_D
- (5 points) K_n
- (5 points) V_{tn}

