

21-04-2018
BILKENT UNIVERSITY
Department of Electrical and Electronics Engineering
EEE313 Electronic Circuit Design
Midterm Exam II
-- SOLUTION --

Surname: _____

Name: _____

ID-Number: _____


Signature: _____

Duration is 110 minutes. Solve all 4 questions. Show all your work.
No books or notes.

Q1 (24 points)	
Q2 (28 points)	
Q3 (24 points)	
Q4 (24 points)	
Total (100 points)	

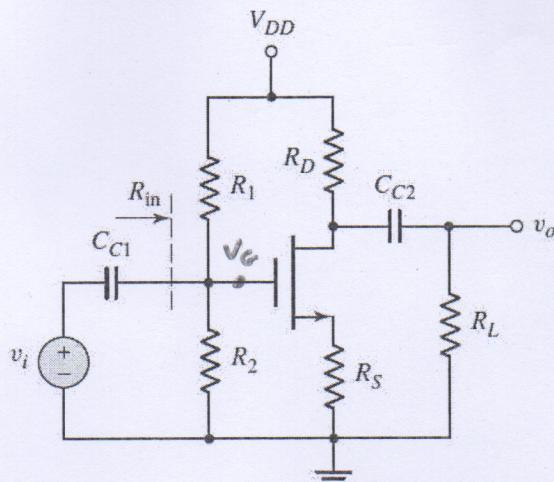Q1. For the NMOS common-source amplifier below, the transistor parameters are: $V_{TN} = 0.8$ V, $K_n = 1$ mA/V², and $\lambda = 0$. The circuit parameters are $V_{DD} = 5$ V, $R_S = 1$ k Ω , $R_D = 4$ k Ω , $R_1 = 225$ k Ω , and $R_2 = 175$ k Ω .

- (8 points) Calculate the quiescent values of I_{DQ} and V_{DSQ} . Check the state of the transistor.
- (10 points) Draw the small signal ac equivalent circuit; derive and determine the small-signal voltage gain v_o/v_i for $R_L = \infty$.
- (6 points) Determine the value of R_L that will reduce the small-signal voltage gain to 75 percent of the value in part b)



$$a) V_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{175}{175 + 225} \times 5 = \frac{35}{16} = 2.19 \text{ V}$$

$$\text{Assume SAT: } i_D = 1(V_{GS} - 0.8)^2$$

$$V_{GS} = V_G - i_D \times R_S = 2.19 - 1 \times 1 = 2.19 - V_{GS}$$

$$\Rightarrow i_D = 2.19 - V_{GS}$$

$$2.19 - V_{GS} = (V_{GS} - 0.8)^2 = V_{GS}^2 - 1.6V_{GS} + 0.64$$

$$V_{GS}^2 - 0.6V_{GS} + 0.64 - 2.19 = 0$$

$$V_{GS}^2 - 0.6V_{GS} - 1.55 = 0$$


$$\Rightarrow V_{GS} = 1.58 \text{ V} > 0.8 \quad \text{Take } V_{GS} = 1.58 \text{ V.}$$

$$V_{GS} = \begin{cases} 1.58 \text{ V} & > 0.8 \\ -0.98 \text{ V} & < 0.8 \end{cases} \times$$

$$i_D = (1.58 - 0.8)^2 = 0.61 \text{ mA}$$

$$\Rightarrow V_{DS} = 5 - 0.61(4 + 1) = 1.95 \text{ V} > V_{GS} - 0.8 = 1.58 - 0.8 = 0.78 \text{ V} \quad \text{SAT.}$$

b)

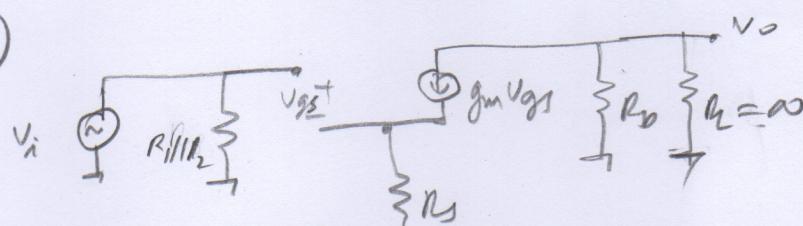

$$V_{GS} = V_i - g_m V_{GS} R_S$$

$$= \frac{V_i}{1 + g_m R_S}$$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$= 2\sqrt{1 \times 0.61} = 1.56 \text{ mA/V}$$

$$V_o = -g_m V_{GS} R_D$$

$$\frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_S} = \frac{-1.56 \times 4}{1 + 1.56 \times 1} = -2.44 \text{ V/V}$$


$$c) \text{ If } R_L \neq \infty \text{ then } \frac{V_o}{V_i} = \frac{-g_m R_D // R_L}{1 + g_m R_S}$$

$$\Rightarrow \frac{R_D // R_L}{R_D} = 0.75 \Rightarrow \frac{R_D R_L}{(R_D + R_L) R_D} = 0.75 \Rightarrow \frac{R_L}{R_D + R_L} = 0.75$$

$$R_L = 0.75 R_D + 0.75 R_L \quad R_L = \frac{0.75 R_D}{0.25} = 3 R_D = 12 \text{ k}\Omega$$

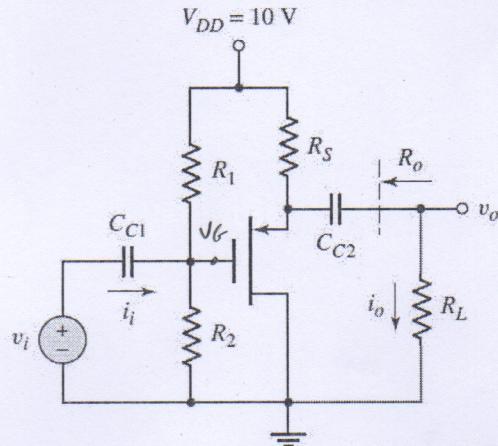Q2. The parameters of the circuit below are $R_S = 4 \text{ k}\Omega$, $R_1 = 850 \text{ k}\Omega$, $R_2 = 350 \text{ k}\Omega$, and $R_L = 4 \text{ k}\Omega$. The transistor parameters are $V_{TP} = -1.2 \text{ V}$, $k_p = 40 \mu\text{A}/\text{V}^2$, $W/L = 80$, and $\lambda = 0.05 \text{ V}^{-1}$.

- (8 points) Determine I_{DQ} and V_{SDQ} . Check the state of the transistor.
- (8 points) Draw the small signal ac equivalent circuit; derive and find the small-signal voltage gain $A_v = v_o/v_i$.
- (4 points) Determine the small-signal ac circuit transconductance gain $A_g = i_o/v_i$.
- (8 points) Find the small-signal ac output resistance R_o . Draw the circuit by which you determine the output resistance.



$$a) V_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{350}{1200} \times 10 = \frac{35}{12} = 2.92 \text{ V.}$$

$$k_p = \frac{40 \mu\text{A}/\text{V}^2}{2} \times 80 = 1600 \mu\text{A}/\text{V}^2 = 1.6 \text{ mA}/\text{V}^2.$$

$$\text{Assume SAT: } i'_D = 1.6 (V_{SG} - 1.2)^2$$

$$V_{SG} = 10 - 1.6 \times 4 - V_G = 10 - 4 \times 2.92 - 2.92$$

$$i'_D = \frac{7.08 - V_{SG}}{4} = 1.77 - 0.25 V_{SG}$$

$$1.77 - 0.25 V_{SG} = 1.6 (V_{SG}^2 - 2.4 V_{SG} + 1.44)$$


$$1.6 V_{SG}^2 - (1.6 \times 2.4 - 0.25) V_{SG} + 1.6 \times 1.44 - 1.77 = 0$$

$$V_{SG} = \begin{cases} 2.08 > 1.2 & \checkmark \\ 0.16 > 1.2 & \times \end{cases} \quad \text{Take } V_{SG} = 2.08 \text{ V.}$$

$$I_{DQ} = 1.77 - 0.25 \times 2.08 = 1.25 \text{ mA.}$$

$$V_{SDQ} = 10 - 4 \times 1.25 = 10 - 5 = 5 \text{ V.}$$
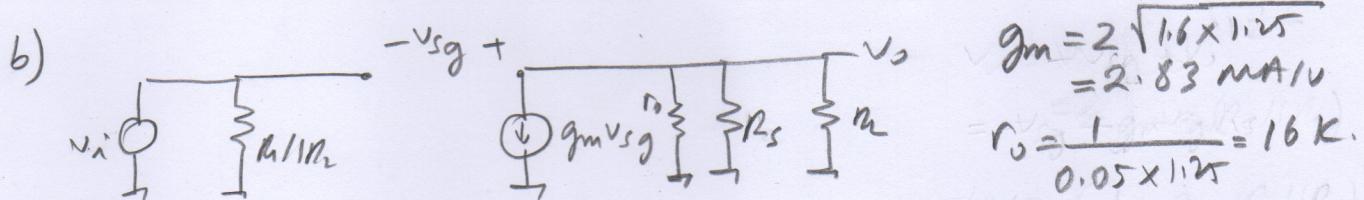
$$= 5 \text{ V} > 2.08 - 1.2 \quad \text{So SAT.}$$




$$\checkmark \text{ Define } R = r_o || R_s || R_L = 16 || 4 || 4 = 16 || 2 = \frac{32}{18} = \frac{16}{9} = 1.78 \text{ k}\Omega.$$

$$A_v = v_o/v_i = -g_m R = -g_m R (v_o - v_i) = \frac{-g_m R v_i}{1 + g_m R}$$


$$A_v = \frac{v_o}{v_i} = \frac{g_m R}{1 + g_m R} = \frac{2.83 \times 1.78}{1 + 2.83 \times 1.78} = 0.83 \text{ V/V.}$$

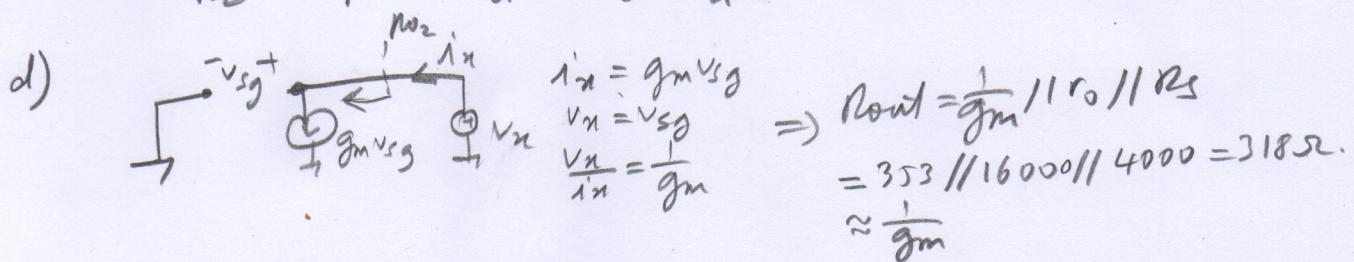c) $I_o = \frac{v_o}{R_L} = \frac{v_o}{4} \quad \frac{i'_D}{v_i} = \frac{i'_D}{v_o} \cdot \frac{v_o}{v_i} = \frac{1}{4} \times 0.83 = 0.208 \text{ mA/V.}$



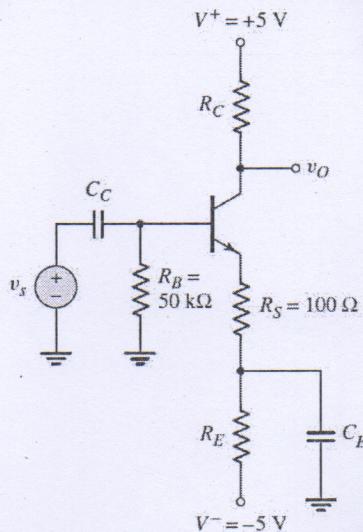Q3. For the circuit below the transistor parameters are $\beta = 100$ and $V_A = \infty$.

- (8 points) Design the circuit such that $I_{CQ} = 0.25$ mA and $V_{CEQ} = 3$ V. Check the state of the transistor. Assume $V_{BE(ON)} = 0.7$ V and $V_{CE(SAT)} = 0.2$ V.
- (8 points) Derive and find the small signal ac input resistance seen by the source v_s .
- (8 points) Derive and find the small signal ac voltage gain $A_v = v_o/v_s$.



$$a) V_{CEQ} = V^+ - R_C \times I_{CQ} - (R_E + r_E) I_{CQ} - V^-$$

$$3 = 5 - 0.25 \times 0.1 + 5 - 0.25 (R_C + R_E)$$

$$R_C + R_E = 4 (10 - 3 - 0.025) = 4 \times 6.975 = 27.9 \text{ k}\Omega$$


$$I_D = \frac{0.25}{100} = \frac{5 - 0.7}{R_B + (\beta + 1)(R_S + R_E)} = \frac{4.3}{50 + 101 \times (0.1 + R_E)}$$

$$0.125 + 25 (0.1 + R_E) = 430 \quad 0.1 + R_E = \frac{417.5}{25} = 16.7 \text{ k}\Omega$$

$$R_E = 16.7 - 0.1 = 16.6 \text{ k}\Omega \Rightarrow R_C = 11.3 \text{ k}\Omega$$

$$V_{CEQ} = 3 \text{ V} > 0.2 \text{ V} \quad F_B > 0 \quad \Rightarrow \text{F.A.}$$

b)

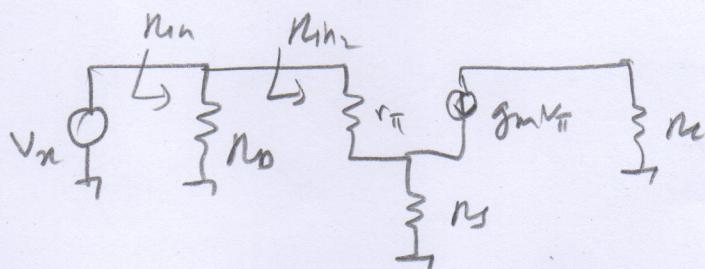

$$r_\pi = \frac{0.026}{0.25} = 10.4 \text{ k}\Omega$$

$$R_{h2} = r_\pi + (\beta + 1) R_S$$

$$= 10.4 + 101 \times 0.1 \\ \cong 20.5 \text{ k}\Omega$$

$$R_{h1} = 50 // 20.5 = 14.5 \text{ k}\Omega$$


c)

$$I_b = \frac{V_{in}}{r_\pi + (\beta + 1) R_S} \quad V_o = -\beta R_C I_b \quad \frac{V_o}{V_{in}} = \frac{-\beta R_C}{r_\pi + (\beta + 1) R_C}$$



$$= \frac{-100 \times 11.3}{20.5} = -56 \text{ V/V}$$

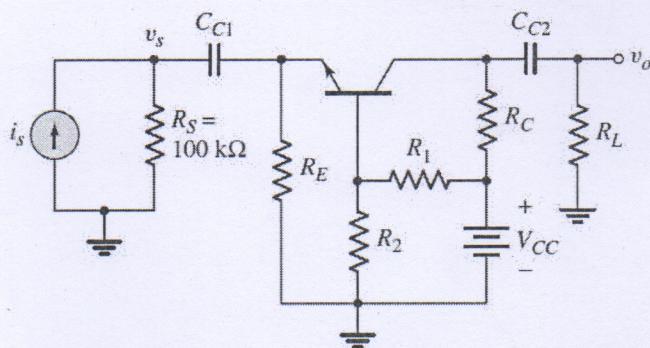Q4. The parameters of the circuit below are $V_{CC} = 9$ V, $R_L = 4 \text{ k}\Omega$, $R_C = 6 \text{ k}\Omega$, $R_E = 3 \text{ k}\Omega$, $R_1 = 150 \text{ k}\Omega$, and $R_2 = 50 \text{ k}\Omega$. The transistor parameters are $\beta = 125$, $V_{BE(\text{ON})} = 0.7$ V, $V_{CE(\text{SAT})} = 0.2$ V, and $V_A = \infty$. The input signal is a current.

- (8 points) Determine Q-point values. Check the state of the transistor.
- (10 points) Determine the small signal ac transresistance function $R_m = v_o/i_s$.
- (6 points) Find the small-signal ac voltage gain $A_v = v_o/v_s$.



a) DC circuit

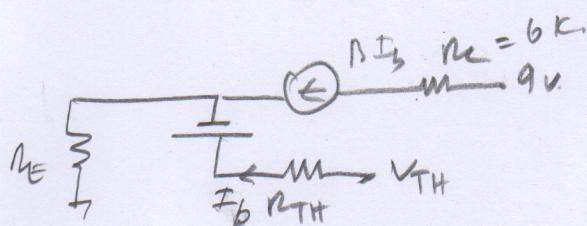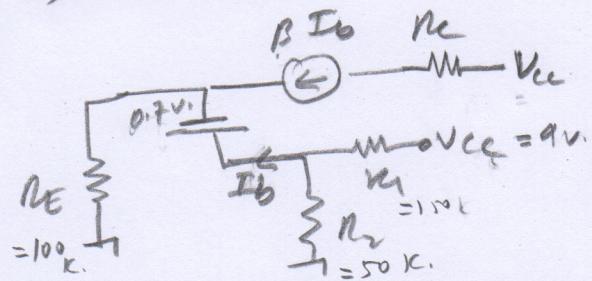

$$V_{TH} = \frac{R_L}{R_L + R_E} \times 9 = 7.25 \text{ V}$$


$$R_{TH} = 50 // 110 = 37.5 \text{ k}\Omega$$

$$V_{TH} = R_{TH} \times I_b + 0.7 + (\beta + 1) I_b \times R_E$$

$$I_b = \frac{2.25 - 0.7}{37.5 + 126 \times 3} = 37 \mu\text{A}$$

$$\Rightarrow I_{EQ} = 0.47 \text{ mA}, \quad I_{EQ} \approx 0.47 \text{ mA}$$
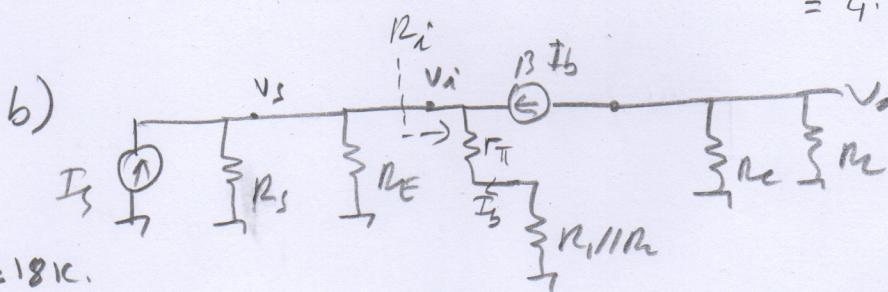
$$V_{CEQ} = 9 - 0.47 \times 6 - 0.47 \times 300 = 4.77 \text{ V} > 0.2 \text{ V} \quad \checkmark \text{ F.A.}$$



$$v_i = -I_b (R_{\pi} + R_1 // R_2)$$

$$i_i = -(\beta + 1) I_b$$

$$R_{\pi} = \frac{V_{\pi}}{I_{\pi}} = \frac{R_{\pi} + R_1 // R_2}{\beta + 1} = \frac{7 + 37.5}{126} = 0.353 \text{ k}\Omega$$

$$V_i = I_s \times R_s // R_E // R_{\pi} \Rightarrow \frac{V_i}{I_s} = R_s // R_E // R_{\pi}$$

$$I_b = \frac{-V_i}{R_{\pi} + R_1 // R_2} \Rightarrow V_o = -\beta I_b R_C // R_L = \beta R_C // R_L \times \frac{V_i}{R_{\pi} + R_1 // R_2}$$

$$\frac{V_o}{I_s} = \frac{V_o}{V_i}, \quad \frac{V_i}{I_s} = \frac{\beta R_C // R_L}{R_{\pi} + R_1 // R_2} \times (R_s // R_E // R_{\pi}) = \frac{125 \times 2.4}{44.5} \times 100 // 3 // 0.353 \approx 2.36 \text{ V/mA}$$

$$c) \frac{V_o}{V_s} \triangleq \frac{V_o}{V_i} = \frac{\beta R_C // R_L}{R_{\pi} + R_1 // R_2} = \frac{125 \times 2.4}{44.5} = 6.74$$