

Name: Tarik Reyhan

Signature: _____

EEE 313 Spring 2012

(Corrected)

Bilkent University

Department of Electrical and Electronics Engineering

EEE 313 Electronic Circuit Design **Midterm Examination #2**

18 April 2012, 17.40 (4 questions, 120 minutes)

- This is a **closed book**, closed notes exam. No cheat sheet allowed.
- All cell-phones should be completely **turned off**.
- Use a calculator for numerical computations. Carry at least **3 significant digits**. Double check your numerical calculations.
- Be sure to write the **units** of all numerical results.
- **Show** all work clearly. Show all the intermediate steps including formulas. **Never, just carry out calculations without formulas and explanation.**
- Please put your **final answer** for each part inside a box for easy identification. Do not give multiple answers, they will not be graded.
- Do not remove the **staple** from the exam sheets or separate pages of the exam. All extra pages must be stamped to your exam.
- You may leave the exam room when you are done. However, please do not leave during the **last five minutes** of the exam.
- At the end of the exam, please stay seated until **all** exam papers are collected.

Useful constants and formulas:

Boltzmann's constant: $86 \times 10^{-6} \text{ eV/K}^\circ$

Electron charge: $1.6 \times 10^{-19} \text{ Coulombs}$

Drain current equation for n-channel MOSFET:

$$I_D = K_n (V_{GS} - V_{TN})^2 \quad \text{for} \quad V_{GS} - V_{TN} \leq V_{DS}$$

$$I_D = K_n (2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2) \quad \text{for} \quad V_{GS} - V_{TN} \geq V_{DS}$$

Drain current equation for p-channel MOSFET:

$$I_D = K_p (V_{SG} + V_{TP})^2 \quad \text{for} \quad V_{SG} + V_{TP} \leq V_{SD}$$

$$I_D = K_p (2(V_{SG} + V_{TP})V_{SD} - V_{SD}^2) \quad \text{for} \quad V_{SG} + V_{TP} \geq V_{SD}$$


Forward active current of BJT is given by:

$$I_C = I_S \left(e^{\frac{V_{BE}}{nV_t}} - 1 \right)$$

Other equations must be deduced by the students.


Please do not write below this line

1. 30 pts.	
2. 20 pts.	
3. 25 pts.	
4. 25 pts.	
Total 100 pts.	

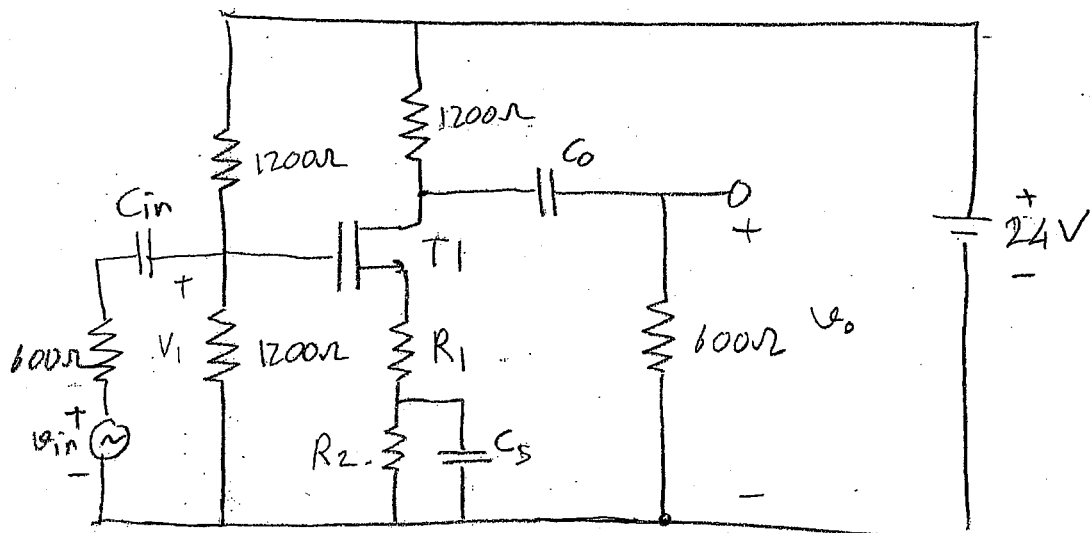

1. (30 points) At the circuit given above, C_{in} , C_o and C_s are very large. $K_n = 1 \times 10^{-2} A/V^2$. $V_{TN} = 2V$
- (7 points) Find the DC bias of the transistor, $R_1 + R_2 = 300\Omega$
 - (7 points) Draw the AC equivalent circuit,
 - (8 points) Find the maximum undistorted peak-to-peak output swing of the circuit assuming that the drain current is equal to 10mA and the transistor is at nonsaturation with $R_1 = 0$ and $R_2 = 300\Omega$.
 - (8 points) Find the maximum undistorted peak-to-peak output swing of the circuit assuming that the drain current is equal to 10mA and the transistor is at nonsaturation with $R_1 = 100\Omega$ and $R_2 = 200\Omega$.

Solution a -)

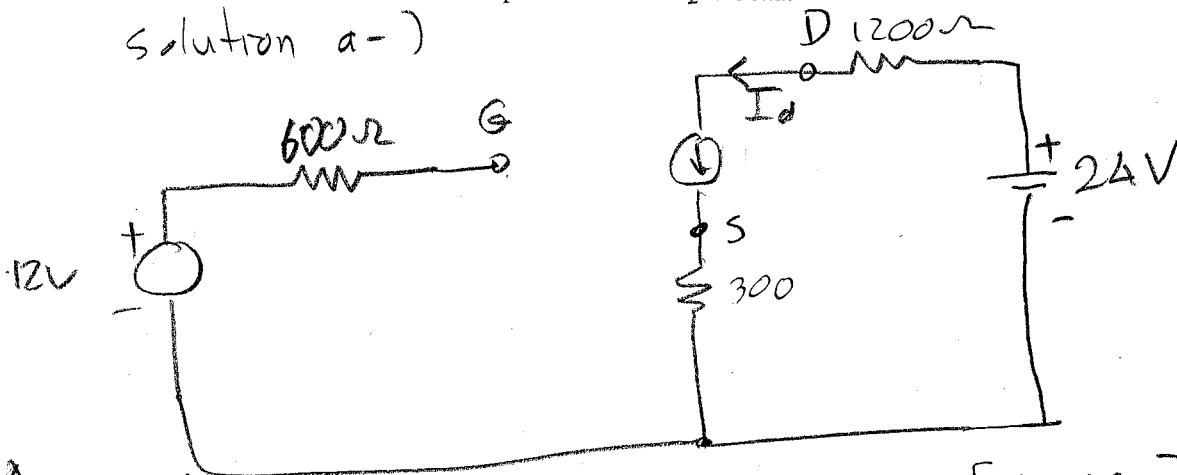

Assume SAT

$$12V = V_{GS} + I_d 300 = V_{GS} + K_n [V_{GS} - V_{TN}]^2$$

$$12V = V_{GS} + 300 \times 10^{-2} [V_{GS}^2 - 4V_{GS} + 4] = V_{GS} + 3V_{GS}^2 - 12V_{GS} + 12$$

$$3V_{GS}^2 - 11V_{GS} = 0 \Rightarrow V_{GS1} = 0 \quad V_{GS2} = \frac{11}{3} = 3.666V$$

$$V_s = 12 - V_{GS} = 12 - 3.666 = 8.333 \text{ V}$$

$$I_D = \frac{8.333 \text{ V}}{300 \Omega} = 27.77 \text{ mA}$$

$$V_{DS} = V_{CC} - I_D [R_S + R_D] = 24 - 27.77 \times 10^{-3} [300 + 1200]$$

$$= -17.66 \text{ V} \Rightarrow \text{non plausible} \Rightarrow \text{not a solution} \Rightarrow$$

Transistor is at non-sat

Assuming non-sat

$$12 \text{ V} = V_{GS} + 300 \text{ k}\Omega \left[2 \frac{V_{TN}}{V_{GS} - 2} V_{DS} - V_{DS}^2 \right]$$

$$24 \text{ V} = (300 + 1200) \text{ k}\Omega \left[2 \frac{V_{TN}}{V_{GS} - 2} V_{DS} - V_{DS}^2 \right] + V_{DS}$$

$$24 = 1500 \times 10^3 \left[2 \frac{V_{TN}}{V_{GS} - 2} V_{DS} - V_{DS}^2 \right] + V_{DS}$$

$$12 = V_{GS} + 3 \left[2 \frac{V_{TN}}{V_{GS} - 2} V_{DS} - V_{DS}^2 \right]$$

$$-60 = 5V_{GS} + 15 \left[2 \frac{V_{TN}}{V_{GS} - 2} V_{DS} - V_{DS}^2 \right]$$

$$24 - 60 = -5V_{GS} + V_{DS}$$

$$-36 = -5V_{GS} + V_{DS} \Rightarrow 5V_{GS} = V_{DS} + 36$$

$$\Rightarrow \boxed{V_{DS} = 5V_{GS} - 36}$$

$$12 = V_{GS} + 3 \left[2 \frac{V_{TN}}{V_{GS} - 2} [5V_{GS} - 36] - [5V_{GS} - 36]^2 \right]$$

$$12 = V_{GS} + 3 \left[2 \frac{V_{TN}}{V_{GS} - 2} [5V_{GS}^2 - 46V_{GS} + 72] - [25V_{GS}^2 - 360V_{GS} + 1296] \right]$$

$$12 = V_{GS} + 3 \left[10 \frac{V_{TN}}{V_{GS} - 2} V_{GS}^2 - 92 \frac{V_{TN}}{V_{GS} - 2} V_{GS} + 144 \frac{V_{TN}}{V_{GS} - 2} - 25V_{GS}^2 + 360V_{GS} - 1296 \right]$$

$$12 = V_{GS} - 45V_{GS}^2 + 804V_{GS} - 3456$$

$$\underbrace{+45V_{GS}^2}_a + \underbrace{805V_{GS}}_b + \underbrace{3468}_c = 0$$

$$V_{GS} = 7.23V, \quad 10.65804V \text{ too large to make } V_{GS} < V_{TN} *$$

$$I_D = 10^{-2} [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2] = 0.015897A = 15.97mA$$

$$V_{DS} = 24 - I_D(300 + 1200) = 24 - 1500I_D = 0.15423V$$


$$V_{DS} = 5V_{GS} - 36 = 0.15423V$$

← solution is correct

$$V_{GS} = 7.23V$$

$$I_D = 15.97mA$$


b-) The AC equivalent circuit

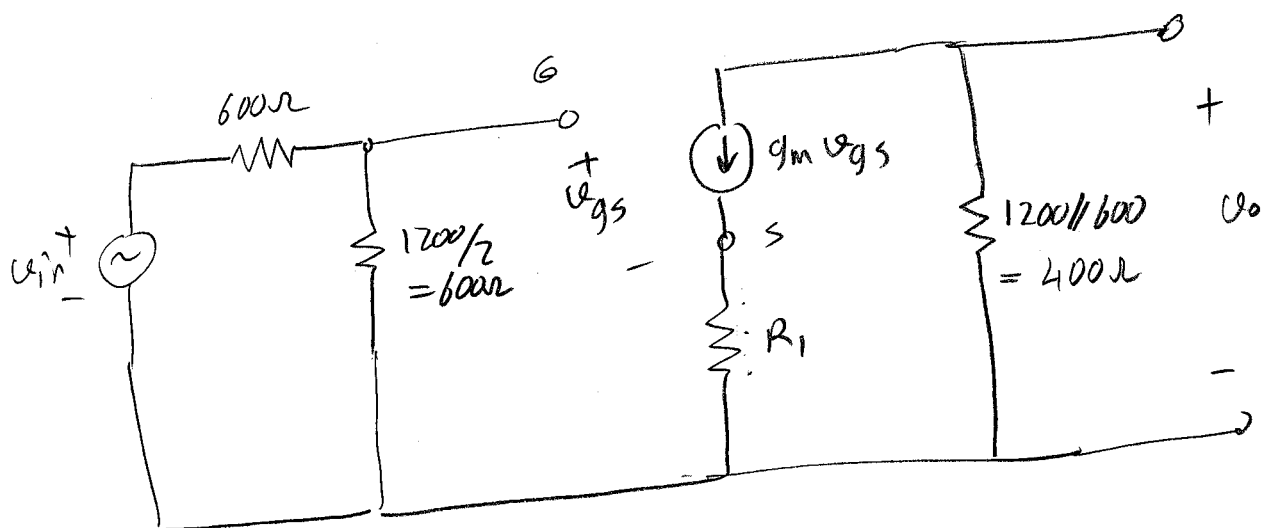

$$g_m = \frac{d}{dV_{GS}} \left\{ K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2] \right\} = 10^{-2} [2V_{DS}]$$

$$g_m = 2 \times 10^{-2} \times 0.15423 = 0.0030846S = 3.08 \times 10^{-3}S$$

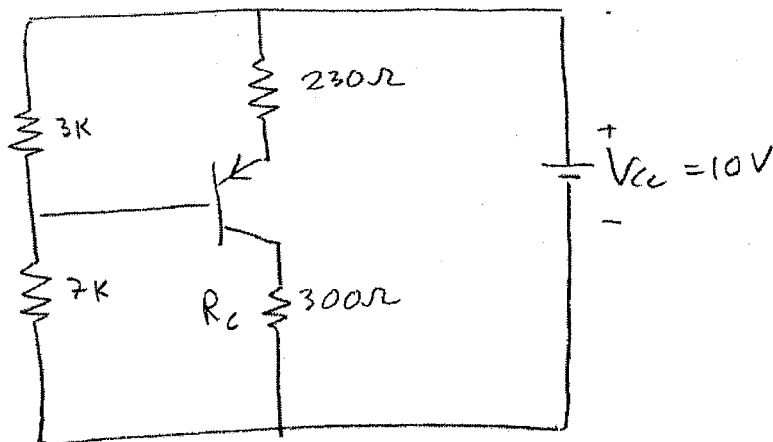
c-) & d-) are cancelled because of misspelling of "saturation" as "nonsaturation"



2. (20 points) At the circuit given above, $\beta=99$, $V_{BE\text{SAT}}=0.7\text{Volts}$ and $V_{CE\text{SAT}}=0.3\text{Volts}$. Please answer the following:

- (10 points) Find the bias (Voltages and currents of the transistor) of the transistor and verify it.
- (10 points) What should be the value of the collector resistor (R_c) in order to bias the transistor at just the borderline of saturation?

a-) Assuming forward active

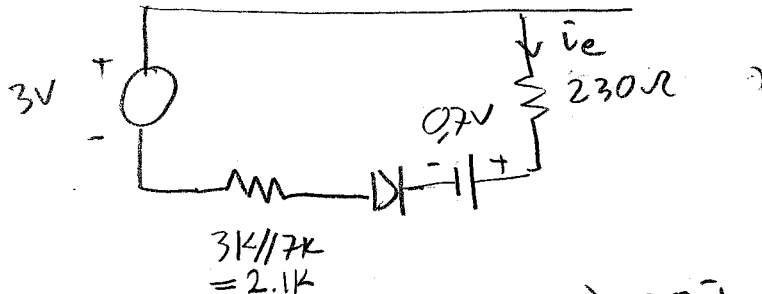

$$3V = i_b 2100 + 0.7 + (99+1) 230 i_b \Rightarrow$$

$$\frac{2.3V}{(23000 + 2100)\Omega} = i_b = \frac{2.3V}{25100\Omega} = 9.16 \times 10^{-5} A = 9.16 \mu A$$


$$i_c = 99 i_b = 9.07 \text{ mA} \quad i_e = (99+1) i_b = 9.16 \text{ mA}$$

$$V_{EC} = V_{CC} - I_c (230 + 300) = 10 - 9.1 \times 10^{-3} \times 530 = 5.14 V$$

$$V_{EC} = V_{EC\text{SAT}} = 0.3 = 10V - I_c (230 + R) \Rightarrow$$

$$\frac{10 - 0.3 V}{I_c} = 230 + R \Rightarrow \frac{9.7}{9.1 \times 10^{-3}} = 1065.9 = 230 + R \Rightarrow$$

$$R = 1066 - 230 = 836 \Omega$$

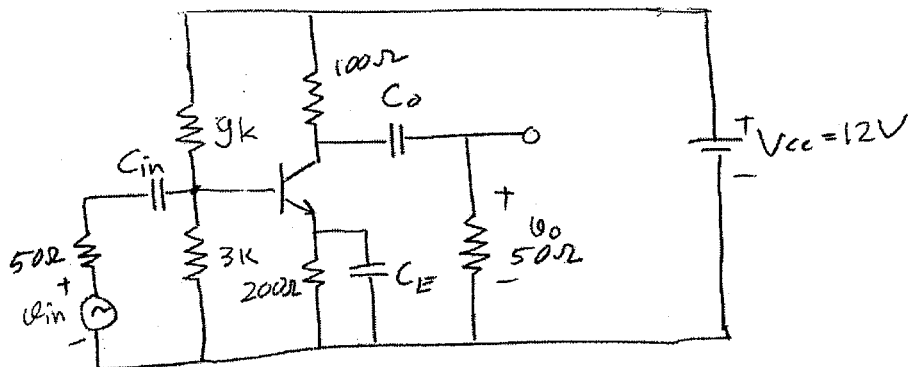

3. (25 points) At the circuit given above, C_{in} , C_o and C_E are very large and $\beta=79$, $V_{BESAT}=0.6V$ and $V_{CESAT}=0.2V$. Please answer the following:

- (7 points) Find the bias of the transistor,
- (8 points) Find the voltage gain of the circuit defined as V_o/V_{in} assuming that the quiescent collector current is equal to $10.5mA$,
- (10 points) Find the output undistorted voltage swing of the circuit assuming that the quiescent collector current is equal to $10.5mA$,

a-)

$$12 \times \frac{3}{9+3} = 3V$$

$$\frac{9 \times 3}{12} = \frac{9}{4} = 2.25k$$

$$V_{CE} = 12V - (10.5 \times 10^{-3})(100 + 200) = 8.84V$$

$$I_B = \frac{3 - 0.6}{2250 + 80 \times 200} = 1.315 \times 10^{-4} A = 131.5 \mu A$$

$$I_C = 79 I_B = 10.4 mA$$

$$I_E = 80 I_B = 10.5 mA$$

b-)

$$g_m = \frac{10.4 mA}{26.6 mV} = 0.3918$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{79}{0.391} = 202.05 \Omega$$

$$100 // 50 \Omega = \frac{100}{3} = 33.33 \Omega$$


$$2.25k // 202k = 185 \Omega$$

$$\frac{V_o}{V_{in}} = \frac{-185}{185+50} \cdot 0.391 \times 33.33 = -10.26 = A_v$$

(-)

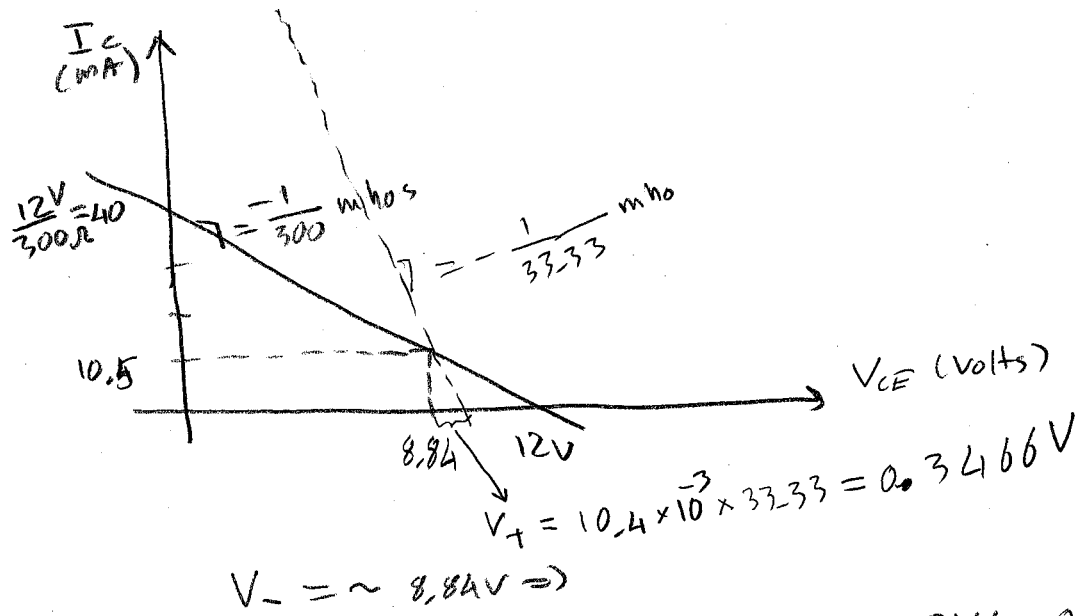

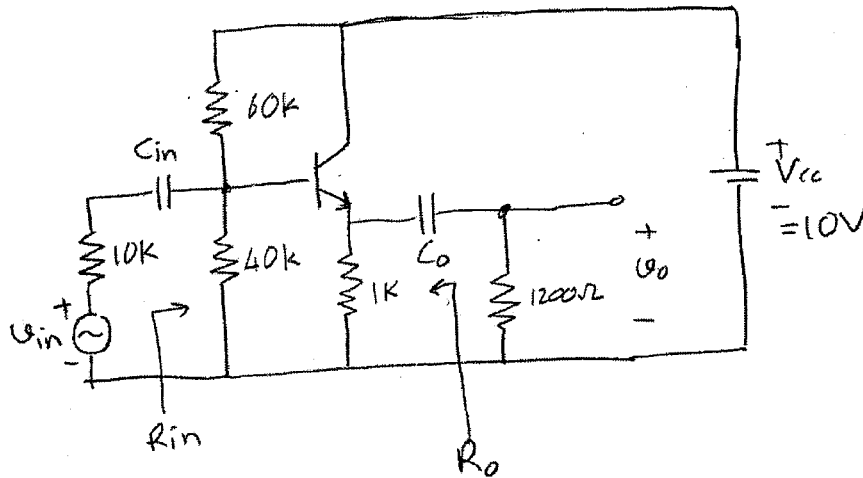
$$V_{P-P \text{ swing}} = 2 \min\{V_-, V_+\} = 2 \times 0.3466 = 0.693V$$



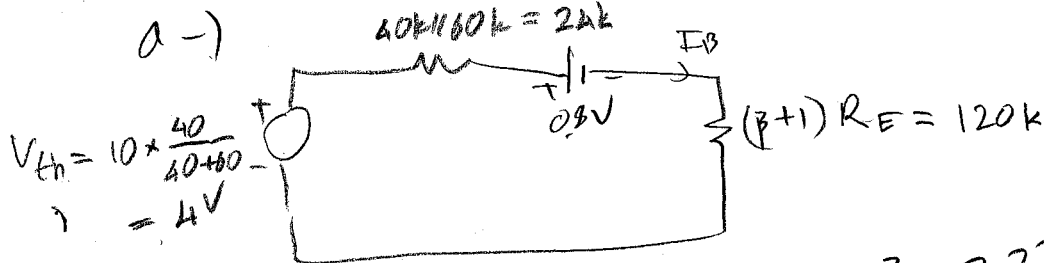4. (25 points) At the circuit given above, C_{in} and C_o are very large and $\beta=119$, $V_{BESAT}=0.8\text{Volts}$ and $V_{CESAT}=0.4\text{Volts}$. Please answer the following:

- (7 points) Find the DC bias of the transistor,
- (8 points) Find the voltage gain of the amplifier defined as V_o/V_{in} assuming that C_{in} and C_o are very large and the collector current is equal to 3mA.
- (10points) Find the input and output impedances of the circuit as shown above assuming that C_{in} and C_o are very large and the collector current is equal to 3mA.




$$I_B = (4\text{V} - 0.8\text{V}) / ((120 + 24) \times 10^3) = 2.22 \times 10^{-5} \text{A} = 22.2 \mu\text{A}$$

$$I_C = \beta I_B = 119 \times 22.2 \mu\text{A} = 2.644 \text{mA}$$

$$I_E = (\beta + 1) I_B = 2.666 \text{mA}$$

$$V_{CE} = V_{CC} - I_E R_E = 10 - 2.666 \text{mA} \times 1000 = 7.33 \text{V}$$

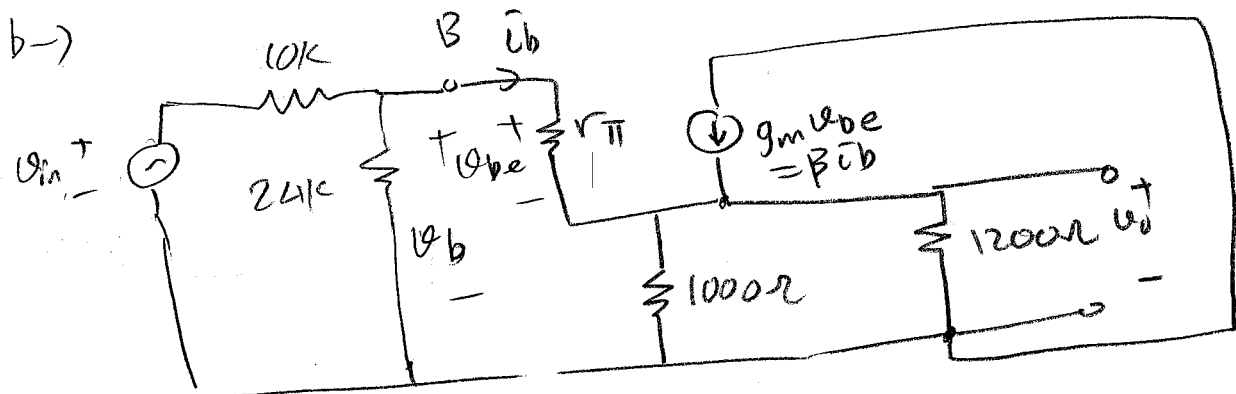

EE313-MT1-2012-04-17-1008

$$R_{L1} \parallel R_L = 545.5 \Omega$$

$$g_m = \frac{3.6 \text{ mA}}{26.6 \text{ mV}} = 0.1128 \text{ S}$$

$$r_{\pi} = \frac{119}{0.1128} = 1055 \Omega$$

Tarik Reyhan

$$V_b = V_{in} \cdot \frac{((\beta+1)(R_c \parallel R_L) + r_{\pi}) \parallel 24k}{((\beta+1)(R_c \parallel R_L) + r_{\pi}) \parallel 24k + 10k}$$

$$[(\beta+1)R_c \parallel R_L + r_{\pi}] = 545.4 \times 120 + 1055 = 66509 \Omega$$

$$[(\beta+1)(R_c \parallel R_L + r_{\pi})] \parallel 24000 = 17636 \Omega \Rightarrow$$

$$V_b = \frac{17636}{17636 + 10000} V_{in} = 0.638 V_{in}$$

$$V_o = V_b \cdot \frac{(R_L \parallel R_c)(\beta+1)}{(R_L \parallel R_c)(\beta+1) + r_{\pi}} = \frac{R_L \parallel R_c}{R_L \parallel R_c + \frac{r_{\pi}}{\beta+1}}$$


$$V_o = V_b \cdot \frac{R_L \parallel R_c}{R_L \parallel R_c + \frac{\beta}{g_m(\beta+1)}} = \frac{R_L \parallel R_c}{R_L \parallel R_c + \frac{1}{g_m}} = \frac{545.4}{545.4 + \frac{1}{0.1158}}$$

$$\frac{V_o}{V_b} = \frac{545.4}{545.4 + 8.6} = \frac{545.4}{554} = 0.984$$

$$\frac{V_o}{V_{in}} = \frac{V_o}{V_b} \cdot \frac{V_b}{V_{in}} = 0.984 \times 0.638 = 0.625$$

Input impedance

Drawing the AC equivalent circuit again

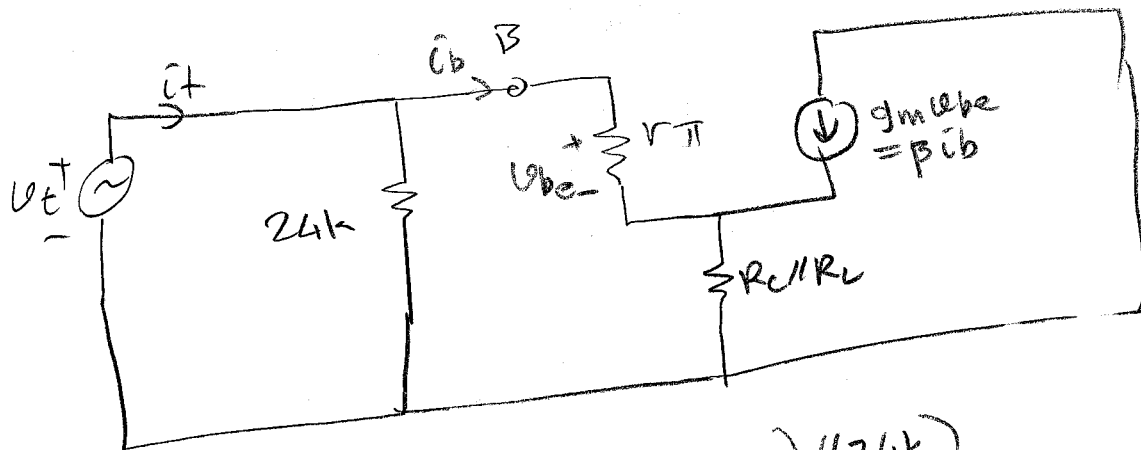


$$R_{in} = \frac{v_t}{i_t} = (R_C \parallel R_L)(\beta + 1) + r_{\pi} \parallel 24k$$

$$= \left[(545.5 \times 120 + 1150) \parallel 24000 \right]$$

$$(R_C \parallel R_L)(\beta + 1) + 1150 = 65460 + 1150 = 66610$$

$$R_{in} = 66610 \parallel 24000 = 17643 \Omega$$

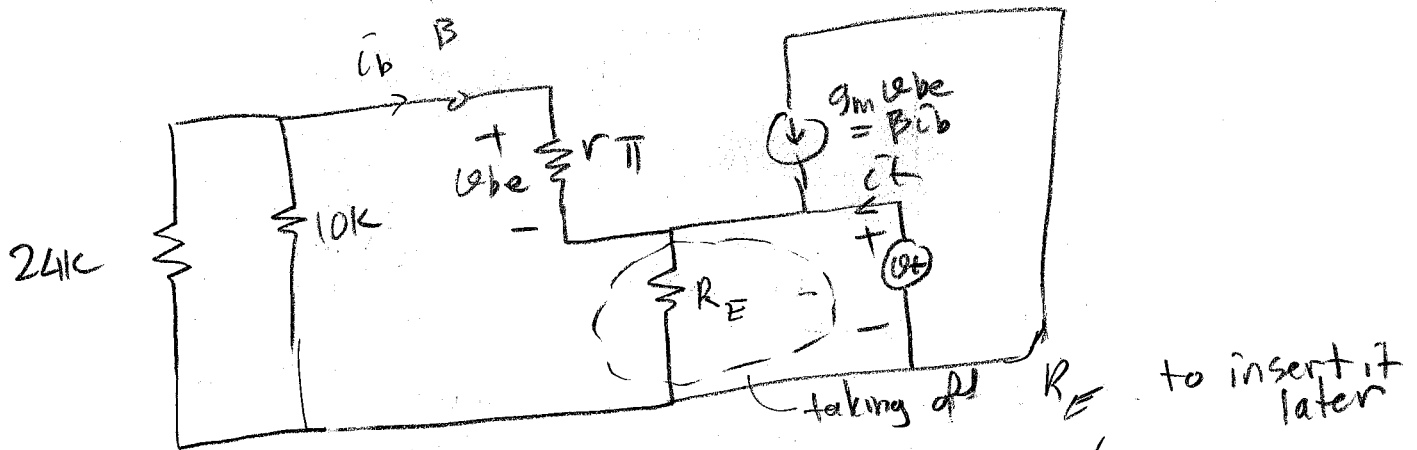c-) Output impedance
Shorting the i/p source, the AC equivalent circuit becomes



$$i_t' = -(i_b + \beta i_b) = -(\beta + 1)i_b \quad i_b' = -\frac{v_t'}{r_{\pi} + (24k \parallel 10k)}$$

$$i_b' = -\frac{v_t'}{1055 + 7059} = -\frac{v_t'}{8114 \Omega} \Rightarrow v_t' = -8114 i_b$$

$$\frac{v_t'}{i_t'} = -\frac{8114 i_b}{120 i_b} = 67.6 \Omega$$

adding R_E in parallel R_o becomes

$$R_o = 67.6 \Omega \parallel 1000 \Omega = 63.32 \Omega$$