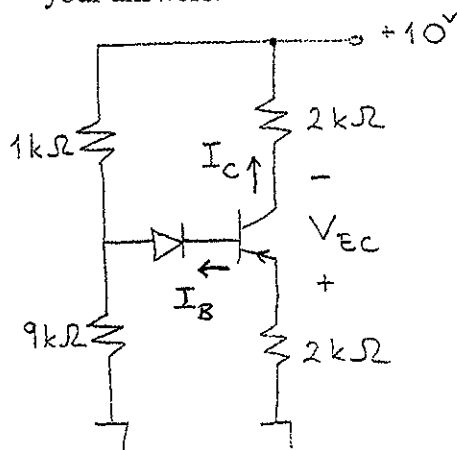


In the following two questions, show all your work and put your answer in the designated boxes.

n-MOSFET	$ V_{Th} = 1V$	$K_n = 1mA/V^2$				
p-MOSFET	$ V_{Tp} = 2V$	$K_p = 0.5mA/V^2$				
nnp-BJT	$\beta_F = 149$	$\beta_R = 10$	$n = 1$	$V_A \rightarrow \infty$	$V_{BE(ON)} = 0.7V$	$V_{CE(SAT)} = 0.2V$
pnnp-BJT	$\beta_F = 99$	$\beta_R = 4$	$n = 1$	$V_A \rightarrow \infty$	$V_{EB(ON)} = 1V$	$V_{EC(SAT)} = 0.2V$
Diode	$V_f = 0.6V$	$n = 1$				
Zener diode	$V_z = 0.5V$	$V_z = 5V$	$n = 1$			

Q1. (20 points)


- a. (5 points) Determine the states of the diode and the transistor, and find I_C and V_{EC} . Justify your answers.



Diode state	OFF
Transistor state	OFF
I_C	0 mA
V_{EC}	-10 V


Base current + is positive always
Diode opposes the current \Rightarrow OFF
Transistor also OFF

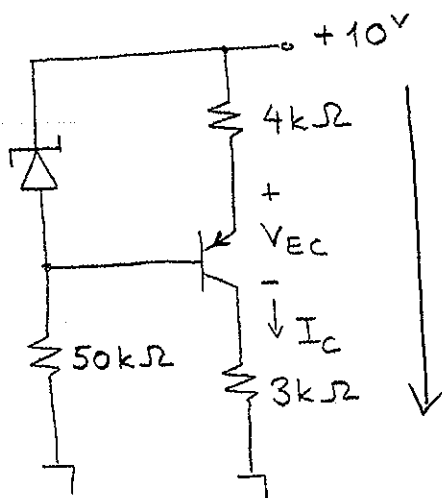- b. (5 points) Determine the states of the diode and the transistor, and find I_C and V_{EC} . Justify your answers.



Diode state	BREAKDOWN
Transistor state	FORWARD ACTIVE
I_C	0.99 mA
V_{EC}	3.03 V

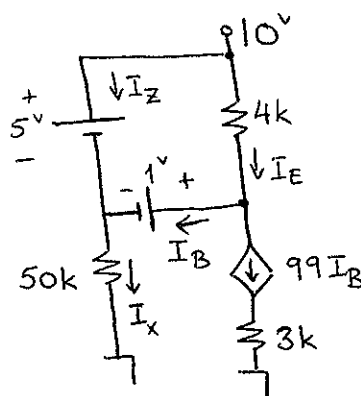assume pnp is in F. ACT and the zener in BRKDOWN



$$I_E = \frac{10 - 6}{4k\Omega} = 1mA$$


$$I_B = \frac{1mA}{\beta + 1} = 10\mu A \quad I_C = 990\mu A$$

$$I_x = \frac{5V}{50k\Omega} = 100\mu A$$

$$V_{EC} = 6V - 3k\Omega \cdot I_C$$


$$V_{EC} = 3.03V > V_{EC(SAT)}$$

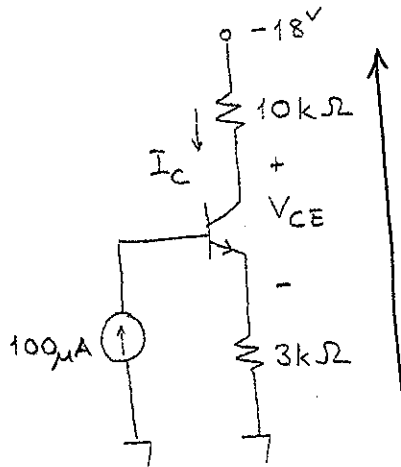- c. (5 points) Determine the state of the transistor, and find I_C and V_{CE} . Justify your answers.



Transistor state	REVACT
I_C	-1.1mA
V_{CE}	-4V

assume REVACT

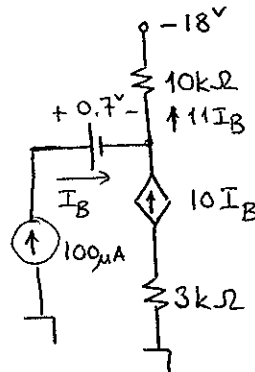

$$I_B = 100\mu\text{A}$$

$$18\text{V} - 0\text{V} = 10 \cdot I_B \cdot 3\text{k}\Omega + V_{CE} + 11I_B \cdot 10\text{k}\Omega$$


$$V_{CE} = -4\text{V}$$

$$V_{EC} = 4\text{V} > V_{EC\text{SAT}}$$


$$I_C = -11I_B = -1.1\text{mA}$$

- d. (5 points) Determine the state of the transistor, and find I_E and I_B . Justify your answers.

Transistor state	REVACT
I_E	$-459.57\mu\text{A}$
I_B	$45.957\mu\text{A}$

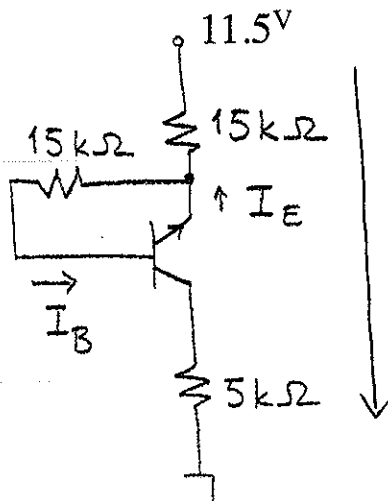

assume REVACT

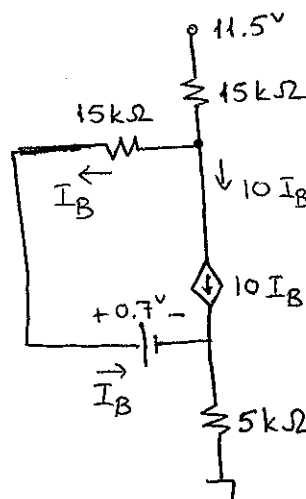

$$11.5\text{V} = 15\text{k} \cdot 11I_B + 15\text{k} \cdot I_B + 0.7 + 5\text{k} \cdot 11I_B$$


$$I_B = 45.957\mu\text{A}$$

$$I_E = -10 \cdot I_B = -459.57\mu\text{A}$$

$$V_{EC} = 15\text{k}I_B + 0.7\text{V}$$

$$V_{EC} = 1.389\text{V} > V_{EC\text{(SAT)}}$$

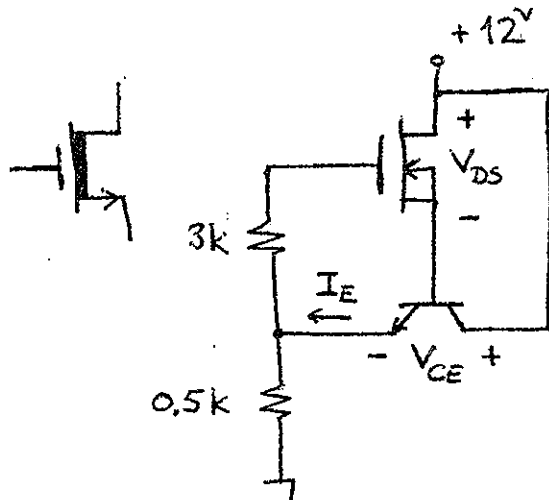b. (10 points) Determine the following currents and voltages, justify your answer.



V_{DS}	$4.55V$
V_{CE}	$5.25V$
I_E	$13.5mA$

n-ch depletion mosfet


$$V_T = -1V \quad K_n = 1mA/V^2$$

npn BJT $\beta = 149$ $V_{BE_{ON}} = 0.7V$

$$V_{CE_{SAT}} = 0.2V$$

+1

assume nMOS SAT
nBJT F.ACT

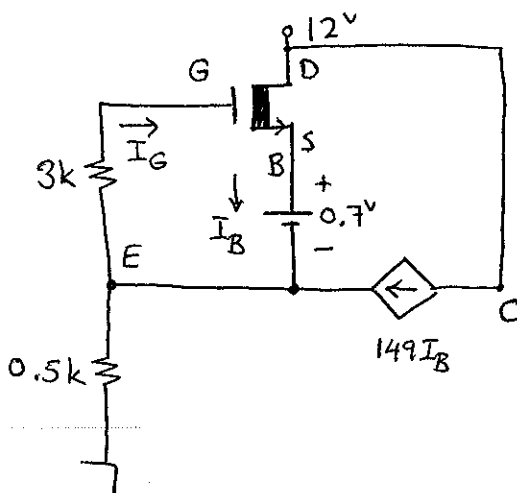

$$I_G = 0 \Rightarrow V_G = V_E$$

+1

$$V_{GS} = V_{ES} = -0.7V + 1$$

$$I_B = I_D = K_n (V_{GS} - (-1))^2 = 90\mu A$$

+2

$$V_E = (\beta + 1)I_B \cdot 0.5k = 6.75V$$

$$I_E = (\beta + 1)I_B = 13.5mA$$

+1

$$V_D = V_C = 12V$$

$$V_{CE} = 5.25V > V_{CE_{SAT}} \quad \text{BJT F.ACT}$$

+1

$$V_{DS} = 12V - (V_E + 0.7V) = 4.55V > V_{GS} - V_{Th}$$

$$4.55V > 0.3V$$

nMOS SAT

+1