

Pop Quiz 1

Section 2 - Time: 50 min

Show your work for full credit. Please read the questions carefully!

n-channel MOSFET

$$i_D = K_n (v_{GS} - V_{Th})^2$$

SAT

$$i_D = K_n [2(v_{GS} - V_{Th})v_{DS} - v_{DS}^2]$$

NON-SAT

p-channel MOSFET



$$i_D = K_p (v_{SG} + V_{Tp})^2$$

SAT

$$i_D = K_p [2(v_{SG} + V_{Tp})v_{SD} - v_{SD}^2]$$

NON-SAT

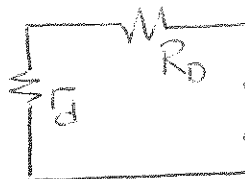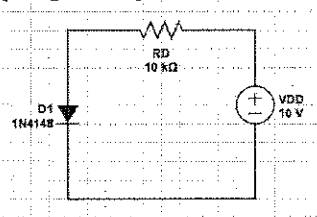1. (20 points) Draw the small signal ac equivalent of the following circuit.



$$g_m = \frac{V_T}{I_{DQ}}$$

2. (40 points) What are the operating states of the transistors below? Justify your answer. For each, express the value of I_{DS} and V_{DS} .

$V_{Th}=2V, K_n=1mA/V^2$	$V_{Th}=2V, K_n=1mA/V^2$
State: OFF	State: SAT
$I_{DS} = 0 mA$	$I_{DS} = 1 mA$
$V_{DS} = 20V$	$V_{DS} = 17V$

$$V_G = 10V$$

$$V_S = 9V$$

$$V_{GS} = 1V < V_{Th}$$

$$\Rightarrow \text{OFF}$$

$$I_D = 0$$

$$V_{DS} = 20V$$

$$V_G = 6V$$

$$V_D = 30V - 10k \cdot 1mA = 20V$$

$$I_D = 1mA$$

assume SAT

$$1mA = \frac{1mA}{V^2} (6V - V_S - 2V)^2$$


$$\Rightarrow V_S = 3V$$

$$V_{DS} = 17V \geq V_{GS} - V_{Th}$$

$$17V \geq 3V - 2V$$

SAT OK.

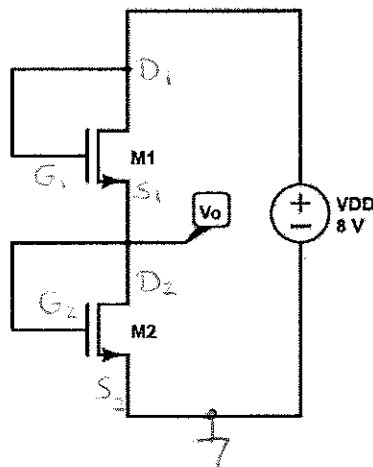3. (40 points) In the circuit shown below, the field effect transistors have threshold voltages, $V_{TH} = 1V$. The transistors' conductance parameters are $K_{n1} = 4K_{n2} = 4mA/V^2$. Determine V_{GS1} , V_{GS2} , V_O , I_D . Show your work!



(5 points)

$$V_{GS1} = V_{DS1} \quad I_{D1} = I_{D2}$$

$$V_{GS2} = V_{DS2}$$

$$V_{DS1} + V_{DS2} = 8V \quad (*) \quad (5 \text{ points})$$

if T/R conducting they must be in SAT state because $V_{DS} \geq V_{GS} - V_{TH}$

assume M_1 and M_2 in SAT

$$I_{D1} = I_{D2} \quad (KCL) \quad (5 \text{ points})$$

$$K_{n1} (V_{GS1} - V_{TH})^2 = K_{n2} (V_{GS2} - V_{TH})^2 \quad (5 \text{ points})$$

$$4K_{n2} (V_{DS1} - 1V)^2 = K_{n2} (V_{DS2} - 1)^2$$

$$2(V_{DS1} - 1) = (V_{DS2} - 1)$$

$$2V_{DS1} - 1 = V_{DS2} \quad (5 \text{ points})$$

from (*) $V_{DS1} + V_{DS2} = 8V \quad (10 \text{ points})$

$$3V_{DS1} = 9V \Rightarrow V_{DS1} = 3V \Rightarrow V_{DS2} = 5V$$

$$V_{GS1} = 3V \quad V_{GS2} = 5V$$

$$\Rightarrow V_O = 5V$$

$$I_{D1} = I_{D2} = \frac{4mA}{V^2} (3V - 1V)^2 = 16mA \quad (5 \text{ points})$$