

25-11-2017  
BILKENT UNIVERSITY  
Department of Electrical and Electronics Engineering  
EEE313 Electronic Circuit Design  
Midterm Exam II  
SOLUTION

Surname: \_\_\_\_\_

Name: \_\_\_\_\_


ID-Number: \_\_\_\_\_

Signature: \_\_\_\_\_

Duration is 110 minutes. Solve all 4 questions. Show all your work.  
No books or notes.

Q1 (25 points)	
Q2 (25 points)	
Q3 (25 points)	
Q4 (25 points)	
Total (100 points)	

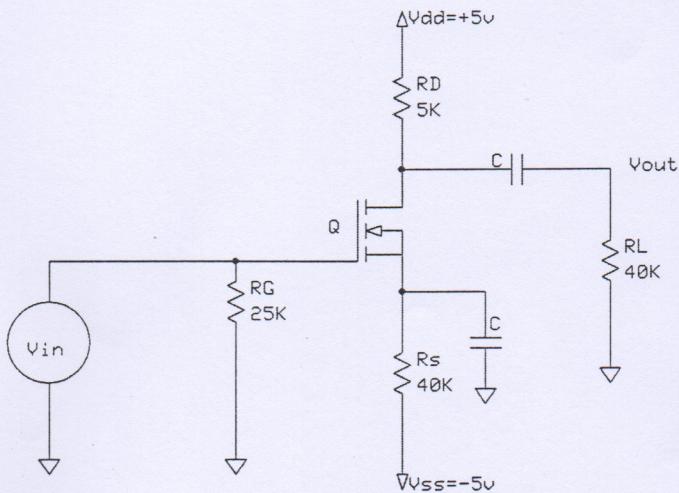Q1. In the circuit shown below, the NMOS transistor has parameters  $V_{TN}=0.8$  V,  $K_n=0.85$  mA/V<sup>2</sup> and  $\lambda=0.02$  V<sup>-1</sup>. Find the small signal voltage gain. Draw the small signal equivalent circuit and derive your results.



DC analysis  $V_G = 0 \quad V_{GS} = 0 - I_0 \times R_s - (-5) = 5 - I_0 \cdot 40 = 5 - 40 I_0$

Assume TR is SAT:  $I_0 = 0.85 (V_{GS} - 0.8)^2$

$$I_{DSQ} = \frac{5 - 1.137}{40} = 0.0966 \text{ mA}$$

$$\begin{aligned} V_{DSQ} &= 5 - I_{DSQ} \times 5 - I_{DSQ} \times 40 + 5 \\ &= 10 - 0.0966 \times 45 = 5.65 \text{ V} \\ &> 1.137 - 0.8 \quad \checkmark \end{aligned}$$

$$\frac{5 - V_{GS}}{40} = 0.85 (V_{GS}^2 - 1.6 V_{GS} + 0.64)$$

$$5 - V_{GS} = 34 V_{GS}^2 - 54.4 V_{GS} + 21.76$$


$$34 V_{GS}^2 - 53.6 V_{GS} + 16.76 = 0$$

$$V_{GS} = \begin{cases} 1.137 \text{ V} > 0.8 \quad \checkmark \\ 0.4335 \text{ V} < 0.8 \times \end{cases}$$

$$V_{GS} = 1.137 \text{ V}$$

$\therefore T_N$  is SAT.

AC analysis

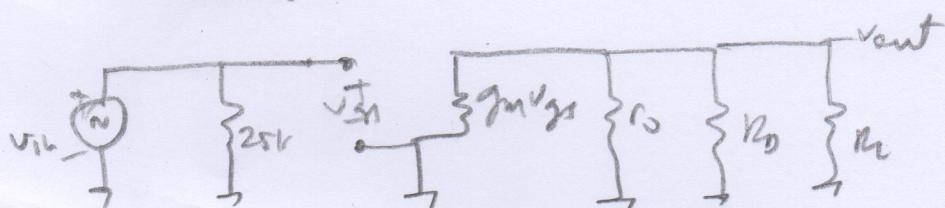

$$g_m = 2 \sqrt{0.85 \times 0.0966} = 0.573 \text{ mA/V}$$

$$r_o = \frac{1}{0.02 \times 0.0966} = 517.6 \text{ k}\Omega$$

$$V_{out} = -g_m V_{GS} \times (R_o || R_D || R_L)$$

$$V_{GS} = V_{in}$$


$$\begin{aligned} \Rightarrow A_v &= -g_m (R_o || R_D || R_L) = -0.573 \times (517.6 || 5 || 40) \\ &= -0.573 \times (517.6 || 4.44) \\ &= -0.573 \times 4.44 \\ &= -2.52 \end{aligned}$$

Q2. In the circuit shown below, the NMOS transistor has parameters  $V_{TN}=0.8$  V,  $k_n=0.1$  mA/V<sup>2</sup>,  $W/L=20$  and  $\lambda=0.02$  V<sup>-1</sup>. Find the small signal voltage gain, the input impedance  $R_{in}$ , and the output impedance  $R_{out}$ . Draw the small signal equivalent circuit and derive your results.

$$K_N = \frac{0.1}{2} \times 20 = 1 \text{ mA/V}^2$$

$$g_m = 2 \sqrt{1 \times 4} = 4 \text{ mA/V}$$

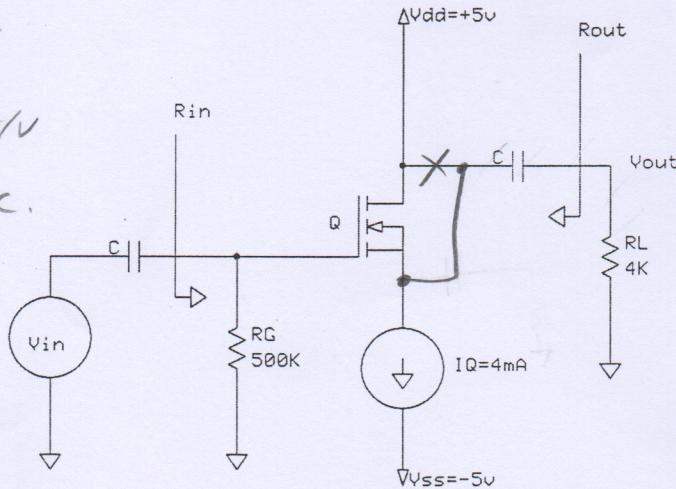
$$r_o = \frac{1}{0.02 \times 4} = \frac{1}{0.08} = 12.5 \text{ k}\Omega$$



$$\frac{1}{g_m} = \frac{1}{4} = 0.25$$

$$\frac{0.25 \times 12.5}{0.25 + 12.5} = \frac{3.125}{12.75}$$


$$R_h = R_G = 500 \text{ k}\Omega$$

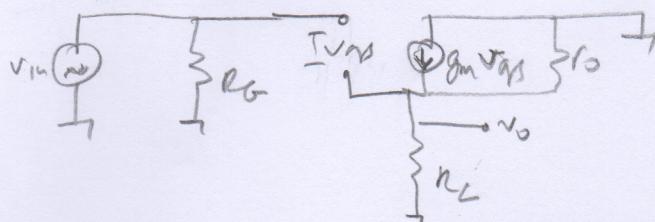

$$V_d = (g_m V_{gs} - \frac{V_o}{r_o}) R_L \Rightarrow V_o (1 + \frac{R_L}{r_o}) = g_m V_{gs} R_L \quad V_o = \frac{g_m V_{gs}}{\frac{1}{R_L} + \frac{1}{r_o}}$$

$$V_{ih} = V_{gs} + V_o \Rightarrow V_{ih} = V_{gs} + \frac{g_m V_{gs}}{\frac{1}{R_L} + \frac{1}{r_o}} = V_{gs} \left( 1 + \frac{g_m}{\frac{1}{R_L} + \frac{1}{r_o}} \right)$$
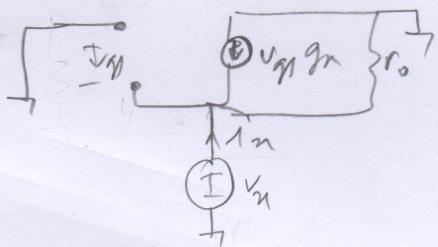
$$\frac{V_o}{V_{in}} = \frac{\frac{g_m}{\frac{1}{R_L} + \frac{1}{r_o}}}{1 + \frac{g_m}{\frac{1}{R_L} + \frac{1}{r_o}}} = \frac{g_m}{\frac{1}{R_L} + \frac{1}{r_o} + g_m} = \frac{4}{\frac{1}{12.5} + \frac{1}{4} + 4} = \frac{4}{4.33} = 0.92$$



$$V_x = -V_{gs}$$

$$i_n = -V_{gs} g_m + \frac{V_x}{r_o} = +V_x g_m + \frac{V_x}{r_o}$$

$$= V_x \left( \frac{1}{g_m} + \frac{1}{r_o} \right)$$


$$\frac{V_x}{V_{in}} = \frac{1}{g_m} // R_o$$

$$= \frac{1}{4} // 12.5 = \frac{\frac{1}{4}}{\frac{1}{4} + 12.5} = \frac{12.5}{1 + 4 \times 12.5} = \frac{12.5}{51}$$

$$= 0.245 \text{ k}\Omega$$

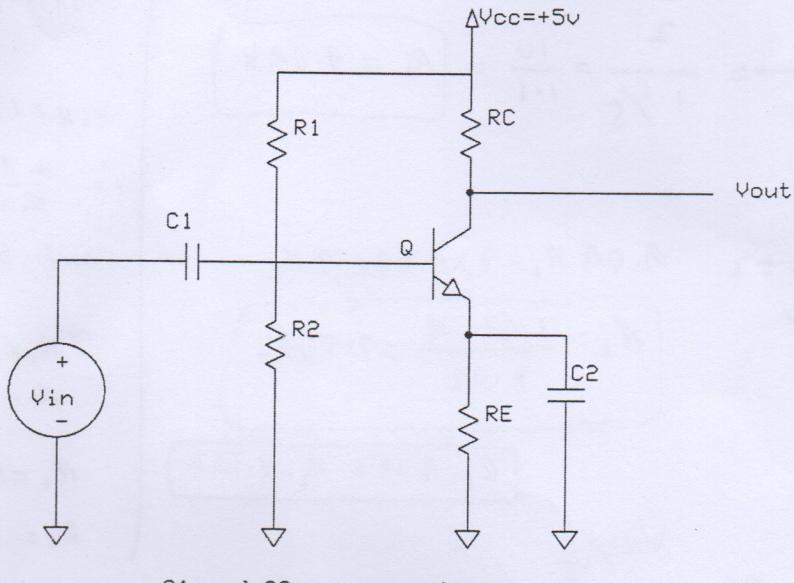Q3. Design the below Common Emitter (CE) stage, i.e. find the values of components such that  $I_{CQ}=1$  mA, voltage drop across  $R_E$  resistor is 400 mV, small signal AC voltage gain magnitude is 20, and small signal AC input impedance is 2 Kohm. Check and verify the state of the transistor.

- (18p)  
(7p)
- Assume for the transistor that  $\beta=100$ ,  $V_{BE(ON)}=0.7V$ ,  $V_{CE(SAT)}=0.2$  V and  $V_A=\infty$
  - Assume for the transistor that  $\beta=100$ ,  $I_S=5 \times 10^{-16}$  A, and  $V_A=\infty$



C1 and C2 are very large

(3p)

a)  $V_{RE} = I_{CQ} \left( \frac{\beta+1}{\beta} \right) R_E = 1 \times \frac{101}{100} \times R_E \quad R_E = \frac{100}{101} \times 0.4 = 0.396 \text{ k} = 396 \Omega$


check TR sat

$$r_T = \frac{V_T}{I_{BSA}} = \frac{0.026}{1/101} = 2.626 \text{ k} \Omega \quad (1p)$$

$$V_{CE} = 5 - 1 \times 0.4 \text{ V} = 4.6 \text{ V}$$

$$= 4.08 > 0.02 \checkmark$$

(2p)

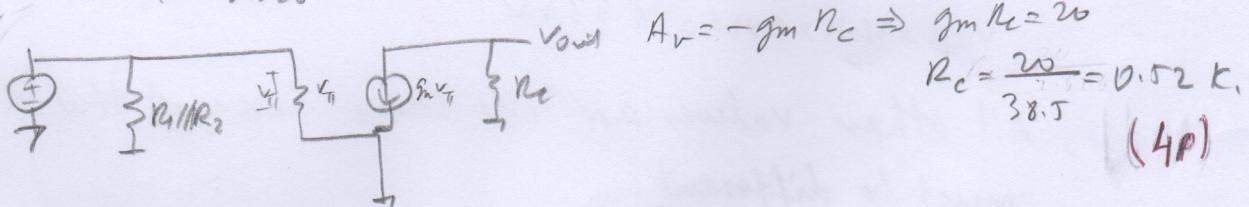

$$R_C = \frac{20}{38.5} = 0.52 \text{ k}, \quad (4p)$$

If  $I_B$  is not considered then  
(3p)

If considered but  $R_{in} = 2k$   
is taken  
(4p)

$$I_B = \frac{1}{100} = 0.01 \text{ mA} \quad V_B = 0.4 + 0.7 = 1.1 \text{ V}$$

$$V_{IB} = 1.1 = 5 - R_1 I_B \quad I_B = \frac{1.1}{R_1} = \frac{1}{100} = 0.01 \text{ mA} \quad I_B = \frac{1.1}{R_1} + 0.01$$

$$1.1 = 5 - R_1 \left( \frac{1.1}{R_1} + 0.01 \right) = 5 - 1.1 \times \frac{R_1}{R_1} - 0.01 R_1 \Rightarrow 3.9 = 1.1 \frac{R_1}{R_1} + 0.01 R_1$$

$$R_{in} = R_1 \parallel R_2 \parallel r_T = 2 \text{ k}$$

$$3.9 = 1.1 \left( \frac{R_1}{8.67} - 1 \right) + 0.01 R_1$$

$$\frac{(R_1 \parallel R_2) \times 2.6}{R_1 + R_2} = 2 \quad 2.6 \left( \frac{R_1}{R_1 + R_2} \right) = 2 \left( \frac{R_1}{R_1 + R_2} \right) + 5.1$$

$$1.1 - 5 = \left( \frac{1.1}{8.67} + 0.01 \right) R_1 \Rightarrow R_1 = 36.5 \text{ k}$$

$$R_1 \parallel R_2 + 2.6 = 0.6 \left( \frac{R_1}{R_1 + R_2} \right) = 5.1$$

$$\frac{36.5 R_2}{36.5 + R_2} = 8.67 \quad 36.5 R_2 = 8.67 R_2 + 36.5 \times 8.67$$

$$R_1 \parallel R_2 = 8.67 \text{ k} \quad R_1 = 8.67 \text{ k}$$

$$R_2 = 8.67 \text{ k}$$

$$\frac{R_1 R_2}{R_1 + R_2} = 8.67 \quad \frac{R_1}{R_1 + 1} = 8.67 \quad \frac{R_1^2}{R_1 + 1} = \frac{R_1}{8.67} - 1$$


(7p)\*

$R_2 = 11.37 \text{ k}$



Q4. In the circuit shown below (for parts a,b,c assume that  $\beta=100$ ,  $V_{BE(ON)}=0.7V$ ,  $V_{CE(SAT)}=0.2 V$  and  $V_A=\infty$ ),

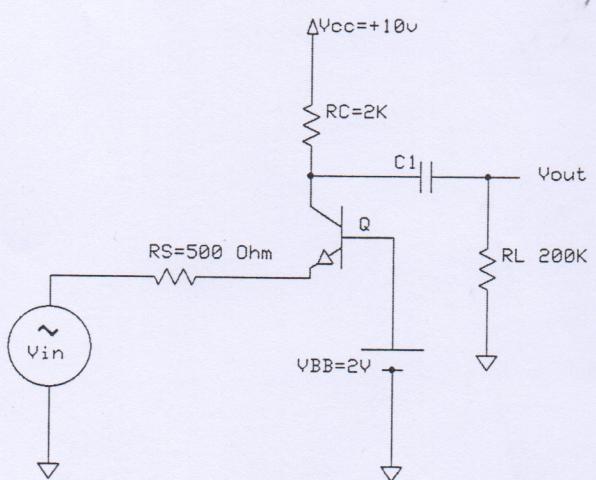- (5) a) Find the quiescent voltage and current values ( $I_{CQ}$  and  $V_{CEQ}$ ), verify transistor state.
- (7) b) Find small signal ac input impedance.
- (6) c) Find the small signal voltage gain.
- (7) d) Find the small signal ac output impedance if  $\beta=100$ ,  $V_{BE(ON)}=0.7V$ ,  $V_{CE(SAT)}=0.2 V$  and  $V_A=100 V$ .




$$a) 2 = 0.7 + I_c \times 0.15 \quad I_c = \frac{1.3}{0.15} = 2.6 \text{ mA. (2p)}$$

$$I_e = \frac{100}{101} \times 2.6 = 2.57 \text{ mA.}$$

$$V_{CEQ} = 10 - 2 \times 2.57 - (2 - 0.7) = 8.7 - 5.14 = 3.56 \text{ V. } > 0.2 \Rightarrow \text{SAT.}$$

b)

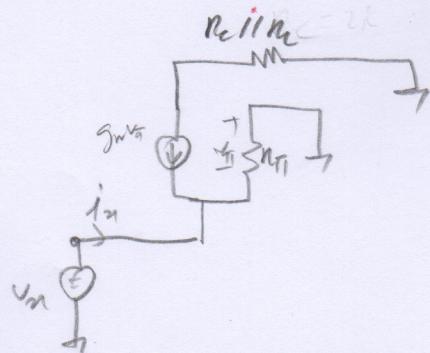


$$r_{\pi} = \frac{V_T}{I_{CQ}} = \frac{0.026 \times 101}{2.6} = 1.0 \text{ k}\Omega$$

$$i_m = \frac{V_{in}}{r_{\pi}} - g_m V_{pi} = \frac{V_{in}}{r_{\pi}} + g_m v_{in}$$

$$R_{in} = \frac{1}{g_m r_{\pi}} = \frac{\frac{1}{g_m} r_{\pi}}{1 + g_m} = \frac{r_{\pi}}{1 + \beta} = \frac{1.0}{101} = 10.52 \text{ }\Omega$$

c)

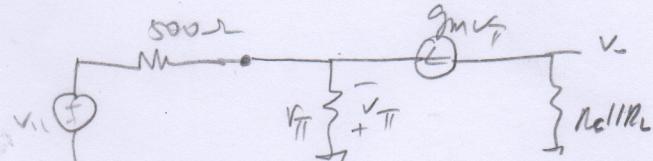


$$v_o = -g_m R_c / r_{\pi} v_{pi}$$

$$-v_{pi} = \frac{10}{510} \times v_{in} \quad v_{pi} = \frac{v_{in} \times 10}{510}$$

$$v_o = \frac{10}{510} \times g_m \times R_c / r_{\pi} = \frac{10}{510} \times \frac{100}{r_{\pi}} \times 2/1000 = 3.84 \text{ (6p)}$$

d)

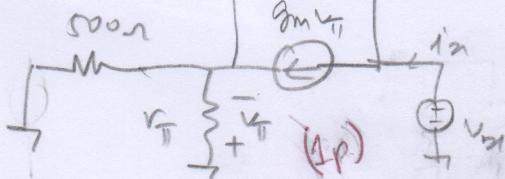

$$v_{pi} = (i_m - g_m V_{pi}) r_o + i_m (R_s / r_{\pi}) (2p)$$

$$\text{since } v_{pi} = -i_m (R_s / r_{\pi})$$

$$v_{in} = (i_m + g_m (R_s / r_{\pi}) i_m) r_o + i_m (R_s / r_{\pi})$$

$$R_{out} = R_s / (1 + g_m (R_s / r_{\pi})) + R_s / r_{\pi} = 1325 \text{ }\Omega + 0.334 \approx 1325 \text{ }\Omega$$

Table 3.1 Summary of the MOSFET current-voltage relationships

NMOS	PMOS
Nonsaturation region ( $v_{DS} < v_{DS}(\text{sat})$ )	Nonsaturation region ( $v_{SD} < v_{SD}(\text{sat})$ )
$i_D = K_n[2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$	$i_D = K_p[2(v_{SG} + V_{TP})v_{SD} - v_{SD}^2]$
Saturation region ( $v_{DS} > v_{DS}(\text{sat})$ )	Saturation region ( $v_{SD} > v_{SD}(\text{sat})$ )
$i_D = K_n(v_{GS} - V_{TN})^2$	$i_D = K_p(v_{SG} + V_{TP})^2$
Transition point	Transition point
$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$	$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$
Enhancement mode	Enhancement mode
$V_{TN} > 0$	$V_{TP} < 0$
Depletion mode	Depletion mode
$V_{TN} < 0$	$V_{TP} > 0$

npn transistor	pnp transistor	
$i_C = I_S e^{v_{BE}/V_T}$	$i_C = I_S e^{v_{EB}/V_T}$	$i_E = i_C + i_B$
$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T}$	$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{EB}/V_T}$	$\alpha = \frac{\beta}{\beta+1}$
$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{BE}/V_T}$	$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{EB}/V_T}$	$\beta = \frac{\alpha}{1-\alpha}$

$$i_C = I_S e^{v_{BE}/V_T} (1 + v_{CE}/V_A)$$

$$r_\pi \equiv \frac{v_{be}}{i_b} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$

$L=1/V_A$   
 $V_T=26 \text{ mV}$