 


20-5-2021

BILKENT UNIVERSITY Department of Electrical and Electronics Engineering
EEE313 Electronic Circuit Design Final Exam
4 questions 150 minutes


PART-1, 2 QUESTIONS 75 MINUTES

- **Instructions:**
- Calculators without extensive memory are allowed
- Clearly explain all your answers in order to receive credit
- Put a box around your final answer
- Cheat sheets are not allowed
- Indicate the units for your final answers
- Write your name and student ID on the bottom of every page
- Mail your pdf solutions to eee313exam@bilkent.edu.tr with your student ID number as subject
- Also upload your pdf solutions to Moodle



 Q1. (20 points) For the buffered regulator shown above, $V_{Z0} = 6\text{V}$ and $R_1 = 0.5\text{k}\Omega$. The DC voltage source V_S may be between 9V and 12V . The load resistor R_L may be between 50Ω and 100Ω . I_Z must be greater than 0.1mA for the Zener to be in the Zener region, and the maximum allowable power dissipation in the Zener is 66mW .

- Find the range of acceptable β of the transistor so that the Zener current remains within acceptable limits under all conditions stated above for V_S and R_L (assuming the transistor is Forward Active.).
- For the β range found above find the maximum value of R_C so that the transistor remains in the Forward Active state.
- If the load resistor is accidentally shorted ($R_L \rightarrow 0$), how much current goes through R_C ? Take R_C as the maximum value found in part b. Assume I_Z is negligible if $V_Z < V_{Z0}$.



Q2. (30 points) The parameters of the transistor in the circuit above are $K_p = 1\text{ mA/V}^2$, $V_{TP} = -1.5\text{ V}$, and $\lambda = 0$. The other circuit component values are $R_S = 200\Omega$, $R_1 = 1.2\text{k}\Omega$, $R_D = 1.2\text{k}\Omega$, $R_L = 50\text{k}\Omega$, $C_{C1} = 4.7\mu\text{F}$, $C_{C2} = 1\mu\text{F}$, $C_{gs} = 10\text{pF}$, and $C_{gd} = 4\text{pF}$. v_{in} is a small-signal ac source.


- Determine the quiescent current and voltage values of the transistor. Verify the state of the transistor.
- Determine the small-signal midband gain $A_{MB} = v_{out}/v_{in}$.
- Find the -3dB lower cut-off frequency f_L of this amplifier.
- Find the -3dB upper cut-off frequency f_H of this amplifier.

20-5-2021

BILKENT UNIVERSITY Department of Electrical and Electronics Engineering
EEE313 Electronic Circuit Design Final Exam
4 questions 150 minutes

PART-2, 2 QUESTIONS 75 MINUTES

- **Instructions:**
- Calculators without extensive memory are allowed
- Clearly explain all your answers in order to receive credit
- Put a box around your final answer
- Cheat sheets are not allowed
- Indicate the units for your final answers
- Write your name and student ID on the bottom of every page
- Mail your pdf solutions to eee313exam@bilkent.edu.tr with your student ID number as subject
- Also upload your pdf solutions to Moodle

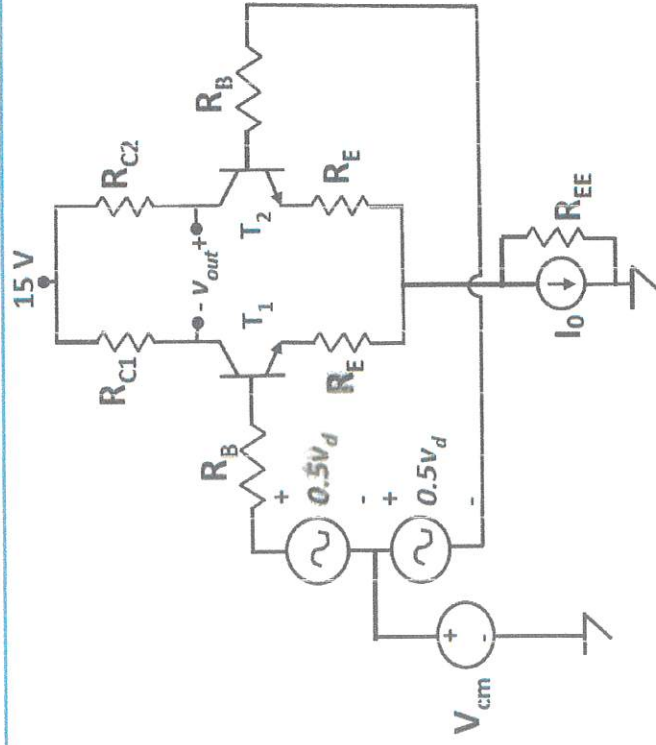

For T1 and T2

$$\beta = 100, V_A = \infty,$$

$$V_{BE}(\text{ON}) = 0.7\text{V}$$

$$V_{CE}(\text{SAT}) = 0.2\text{V}$$

$$V_T = 0.026\text{V}$$

$$R_{C1} = R_{C2} = 10\text{k}\Omega$$

$$R_E = 150\Omega$$

$$R_B = 5\text{k}\Omega$$

$$R_{EE} = 200\text{k}\Omega$$

$$I_0 = 1\text{mA}$$

Q3. (30 points) In the above diff amp $V_{cm} = V_Q + v_{cm}$ where $V_Q = 5\text{V}$, v_{cm} is the small-signal common-mode input voltage, and v_d is the small-signal differential input voltage.


a) For when the small input signals are zero (i.e. $v_{cm} = v_d = 0$), find the collector currents, small signal transistor parameters, and verify the states of the transistors. Note: Do not ignore the base currents and the current on R_{EE} .

b) Derive and find the small signal differential gain v_{out}/v_d .

c) Derive and find the worst-case common mode small-signal gain v_{out}/v_{cm} if R_{C1} and R_{C2} are accurate to $\pm 1\%$.

d) Derive and find the small-signal common mode input resistance R_{icm}

 e) Derive and find the small-signal differential input resistance R_{id}



Q4. (20 points) In the above voltage buffer, the **nnpn**

BJT has the parameters $V_{BE}(\text{ON}) = 0.7\text{V}$, $V_{CE}(\text{SAT}) = 0.2\text{V}$, $\beta = 100$, $V_A = \infty$, and the **depletion mode nMOS** transistor has the parameters $K_n = 0.2\text{mA/V}^2$, $\lambda = 0$, and $V_{TN} = -1.8\text{V}$. Take $V_T = 0.026\text{V}$.

a) For $R_L = \infty$, find the range of V_{in} so that both

transistors are active i.e. F.A. for the BJT and SAT for the nMOS.

b) If V_{out} is a sinusoidal with peak voltage of 2V , find the minimum value of R_L for which the condition that both transistors are active is not violated.

c) For $R_L = 500\Omega$ derive and find the small signal gain v_{out}/v_{in} of this buffer for $V_{in} = 0.7\text{V} + v_{in}$ where v_{in} and v_{out} are a small signal.