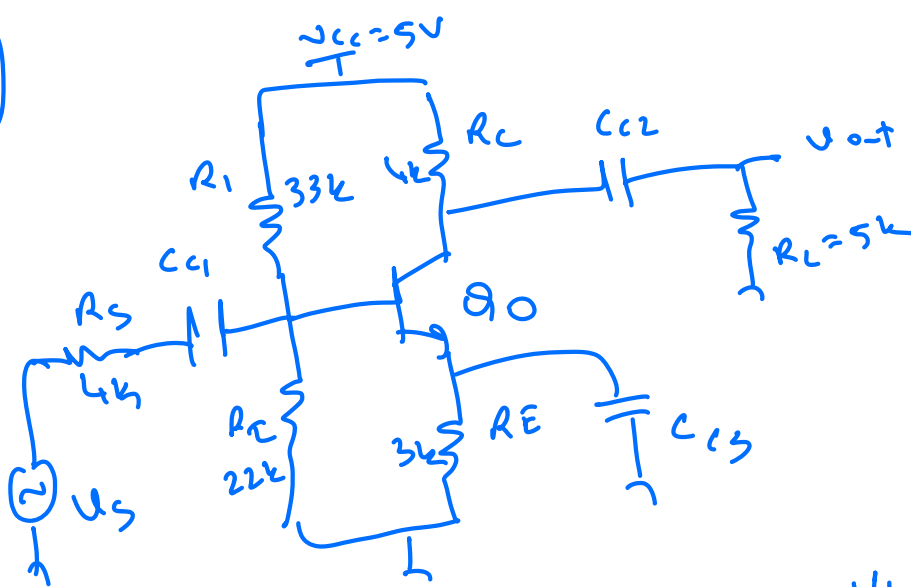


1)




$$V_{BE(0V)} = 0,7V$$

$$V_{CE(sat)} = 0,2V$$

$$\beta_o = 100$$

$$r_o = 200k$$

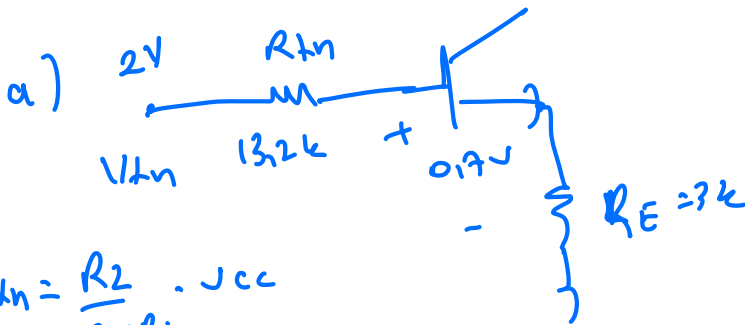

$$V_{th} = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$$

$$V_{th} = \frac{2}{5} \cdot 5 = 2V$$

$$R_{th} = R_1 || R_2 = 33 || 22 = 13,2k$$

$$V_{th} = R_{th} \cdot I_B + 0,7V + (\beta + 1) I_B R_E$$

$$2 = 13,2 I_B + 0,7 + 101 I_B \cdot 3$$

$$1,3 = 316,2 I_B$$

$$I_B = 4,1 \mu A$$


$$I_C = 0,41 mA$$

$$I_E = 0,415 mA$$

$$V_{CE} = 5 - 4 \cdot 0,41 - 3 \cdot 0,415$$

$$V_{CE} = 2,115V > 0,2V \quad \text{f-A. } \checkmark$$

b)

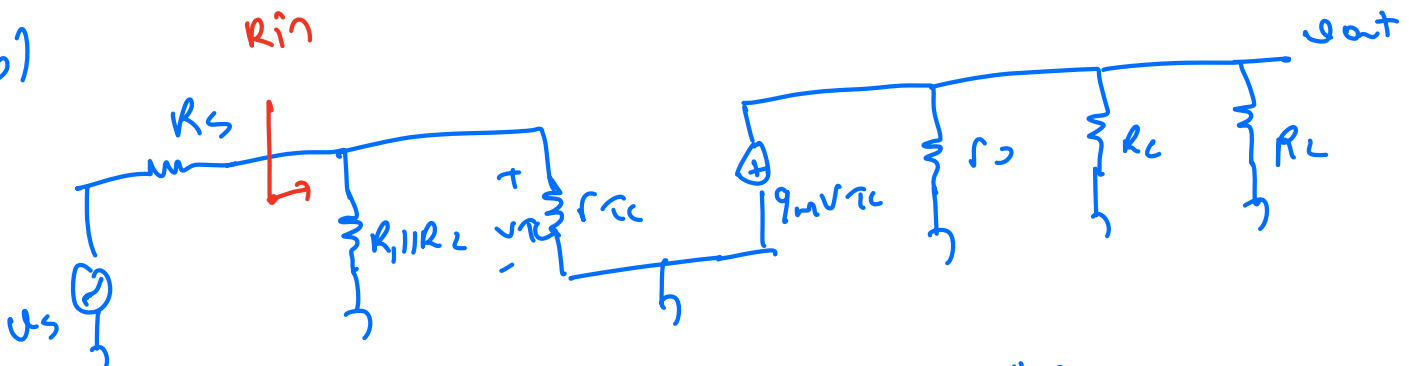

$$g_m = \frac{I_C}{V_T} = \frac{0,41}{0,025} = 16,4 mA/V$$

$$r_a = \frac{\beta}{g_m} = \frac{100}{16,4} = 6,1 k\Omega$$

$$R_{in} = R_1 || R_2 || r_{ic}$$

$$R_{in} = 13,2k || 6,1k = 4,17k\Omega$$

$$V_{\pi} = \frac{R_{in}}{R_{in} + R_s} \cdot u_s$$

$$\frac{u_{out}}{u_s} = A_v = -\frac{R_{in}}{R_{in} + R_s} \cdot g_m (r_o \parallel R_C \parallel R_L)$$

$$u_{out} = -g_m V_{\pi} (r_o \parallel R_C \parallel R_L)$$


$$A_v = -\frac{4.17}{4.17 + 4} \cdot (164) \cdot (200 \parallel 445)$$

midband gain

(capacitors have no effect)

$$A_v = -18.4 \frac{V}{V}$$

C.)

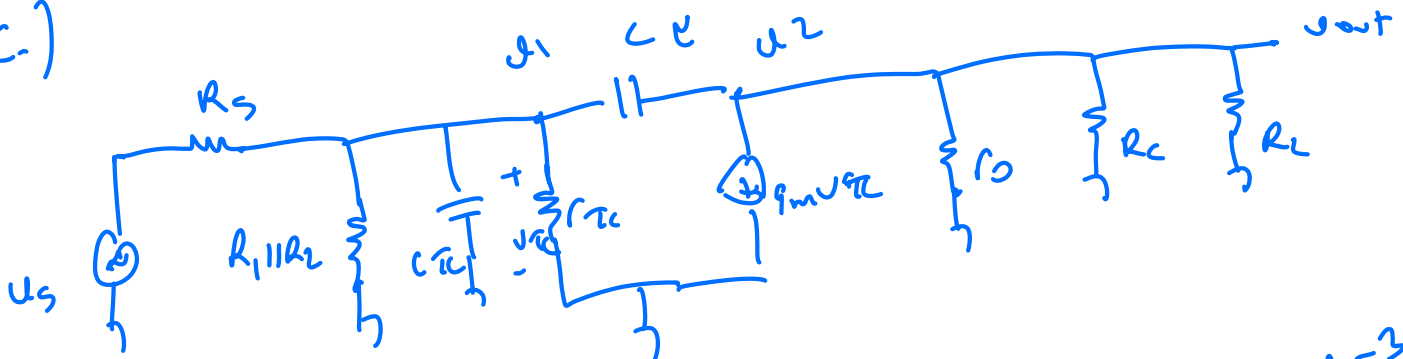

from lecture notes $f_T = \frac{g_m}{2\pi (C_{\pi} + C_C)}$


$$\Rightarrow 700 \cdot 10^6 = \frac{164 \cdot 10^{-3}}{2\pi (C_{\pi} + C_C)}$$

$$C_{\pi} + C_C = 373 \text{ pF}$$

$$C_C = 1 \text{ pF} \leftarrow \text{given}$$

$$C_{\pi} = 273 \text{ pF}$$

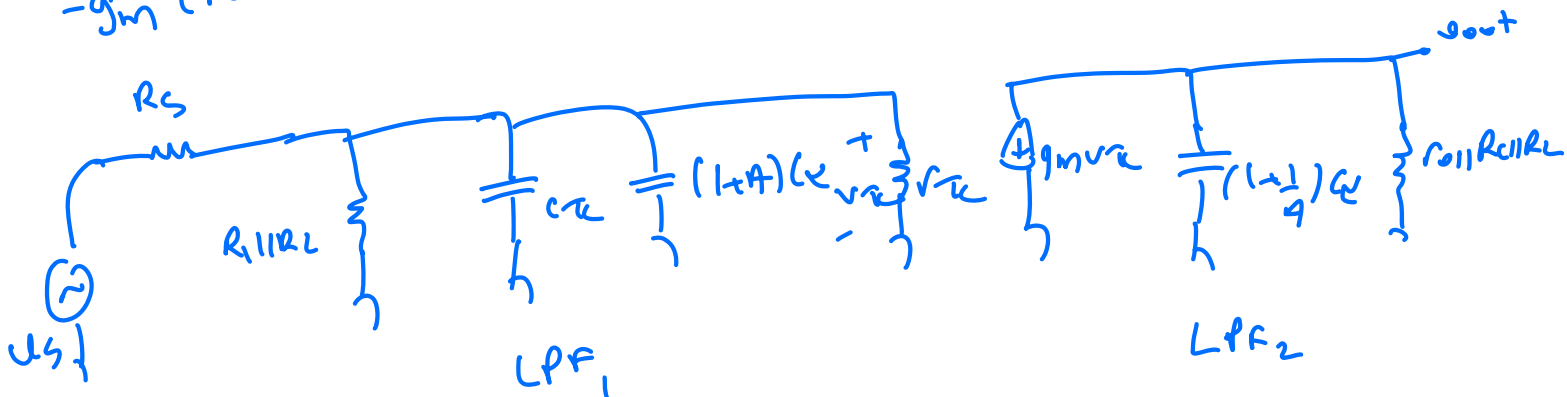gain from u_1 to u_2
 $-g_m (r_o \parallel R_C \parallel R_L) = -36 \frac{V}{V} = -A$



$$C_T = C_{\pi} + (1+A)C_C = 273 + 37.1 = 39.73 \text{ pF}$$

$$(1 + \frac{1}{36})C_C \sim 1 \text{ pF}$$

There is a LPF @ the input side and $\rightarrow \frac{1}{1+j\frac{f}{f_{c1}}}$
 There " " " " output side. $\hookrightarrow \frac{1}{1+j\frac{f}{f_{c2}}}$

$$f_{c1} = \frac{1}{2\pi C_T (R_S \parallel \underbrace{R_{i1} \parallel R_{i2} \parallel r_{\pi}}_{R_{in}})} = \frac{1}{2\pi \cdot 39.73 \cdot 10^{-12} \cdot (4 \parallel 4 \parallel 2k)}$$


$$f_{c1} = \frac{1}{2\pi \cdot 39.73 \cdot 10^{-12} \cdot 2.04 \cdot 10^3} = 1.96 \text{ MHz}$$

$$f_{c2} = \frac{1}{2\pi C_L (r_o \parallel R_C \parallel R_L)} = \frac{1}{2\pi \cdot 1 \cdot 10^{-12} \cdot 2.2k} = 72.3 \text{ MHz}$$

$$f_H = f_{c1} = 1.96 \text{ MHz}$$

The input side dominates the response because of the miller effect.

2)

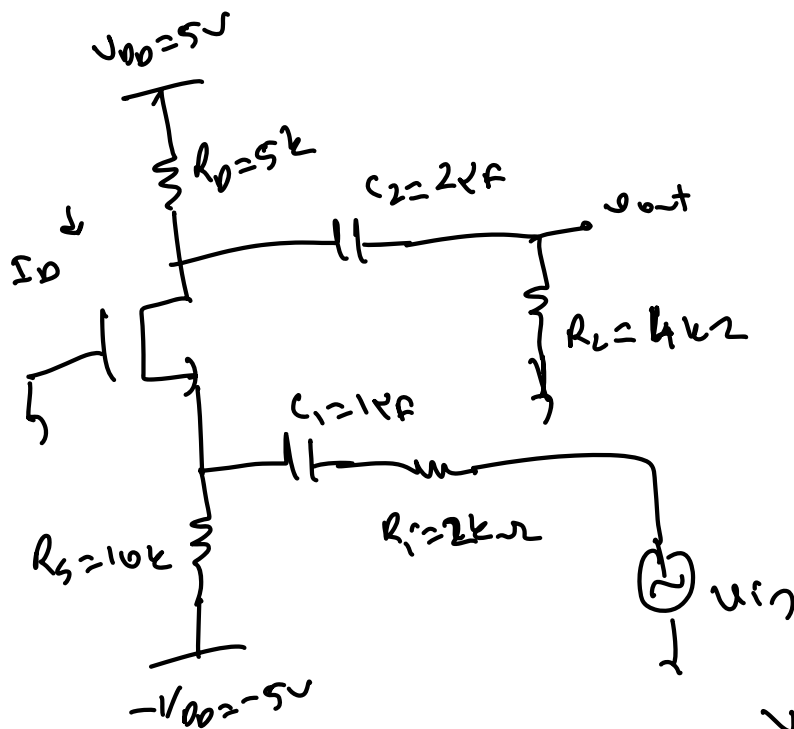

$$V_{TN} = 1V$$

$$K_N = 2 \frac{mA}{V^2}$$

$$\lambda = 0$$

$$C_{gs} = 12 pF$$

$$C_{gd} = 3 pF$$

a) $V_G = 0V$

$$V_S = -5 + 10I_D$$

$$V_D = 5 - 5I_D$$

$$V_{GS} = 5 - 10I_D$$

$$V_{GS} = 1.4V$$

$$V_{DS} = 10 - 15I_D$$

$$V_{DS} = 4.16V$$

$$I_D = 2 \cdot (0 - (-5 + 10I_D) - 1)^2$$

$$I_D = 2 \cdot (4 - 10I_D)^2$$

$$I_D = 2 \cdot 2^2 \cdot (2 - 5I_D)^2$$

$$I_D = 8 \cdot (4 - 20I_D + 25I_D^2)$$

$$0.125I_D = 4 - 20I_D + 25I_D^2$$

$$I_D = 0.145 mA \times V_{GS} < V_{th}$$

$$I_D = 0.36 mA$$

$$V_{DS} > V_{GS} - V_{TN} \quad \text{SAT}$$


$$4.16 \quad 1.4 \quad -1$$

$$g_m = 2\sqrt{K_N I_D}$$

$$g_m = 2\sqrt{2 \cdot 0.36}$$

$$g_m = 1.7 \frac{mA}{V}$$

b)

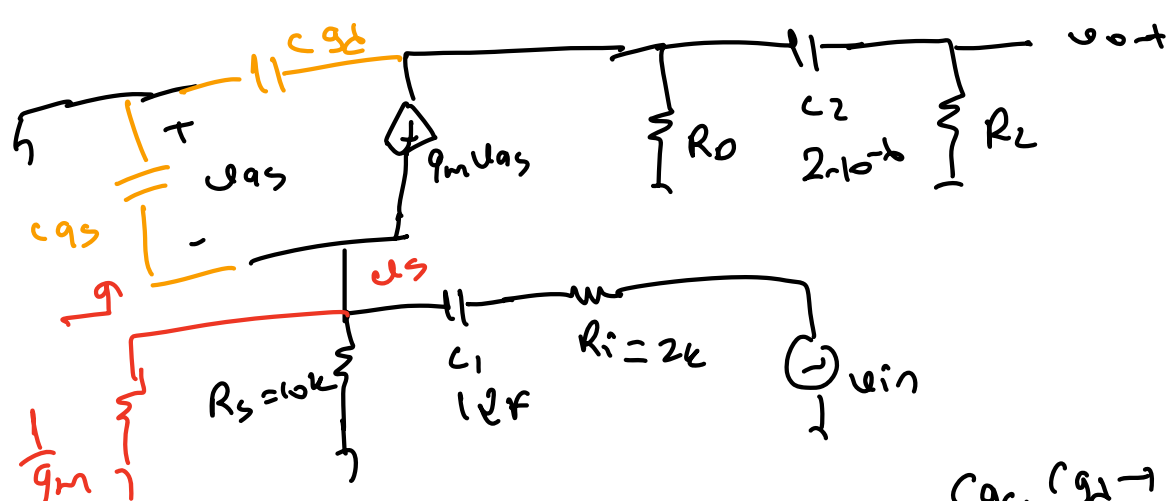

for mid band gain $C_1, C_2 \rightarrow$ short ckt. $C_{gs}, C_{gd} \rightarrow$ open ckt.

$$u_s = \frac{\frac{1}{g_m} \parallel R_s}{\frac{1}{g_m} \parallel R_s + R_i} \cdot u_{in}$$

$$u_{gs} = u_g - u_s$$

$$u_{gs} = -u_s$$

or you can write a KCL @ the source.

$$u_{out} = -g_m u_{gs} (R_o \parallel R_L)$$

$$A_v = \frac{u_{out}}{u_{in}} = g_m \cdot \frac{\frac{1}{g_m} \parallel R_s}{\frac{1}{g_m} \parallel R_s + R_i} \cdot (R_o \parallel R_L)$$

$$A_v = 1.7 \cdot \frac{0.59 \parallel 10}{0.59 \parallel 10 + 2} \cdot (5 \parallel 4) \Rightarrow \boxed{A_v = 0.82 \frac{V}{V}}$$

c) f_L is determined by C_1 and C_2 .

$$f_{LC1} = \frac{1}{2\pi C_1 \left(\frac{1}{g_m} \parallel R_s + R_i \right)} = \frac{1}{2\pi \cdot 10^{-6} \cdot (0.59 \parallel 10 + 2)k}$$

$$f_{LC1} = 62 \text{ Hz}$$

R seen by C_1
(kill u_{in})

the form is for low freq.

$$A_o = \frac{j \frac{1}{f_{LC1}}}{1 + j \frac{1}{f_{LC1}}} \cdot \frac{j \frac{1}{f_{LC2}}}{1 + j \frac{1}{f_{LC2}}}$$

$$f_{Lc2} = \frac{1}{2\pi C_2 (R_0 + R_L)} = \frac{1}{2\pi \cdot 2 \cdot 10^{-6} \cdot (9k)} = 8.8k Hz$$


$f_L = 62 Hz$ \rightarrow R seen by C_2

d) f_H is determined by C_{gs} and C_{gd}
 R seen by C_{gs} $(\frac{1}{g_m} \parallel R_S \parallel R_i)$, C_{gs} is from source to gnd.
 R seen by C_{gd} $(R_D \parallel R_L)$, C_{gd} is from drain to gnd.


$$f_{Hc_{gs}} = \frac{1}{2\pi C_{gs} (\frac{1}{g_m} \parallel R_S \parallel R_i)} = \frac{1}{2\pi \cdot 12 \cdot 10^{-12} \cdot (0.59 \parallel 10 \parallel 2)k} = 30.1 mHz$$

$$f_{Hc_{gd}} = \frac{1}{2\pi C_{gd} (R_D \parallel R_L)} = \frac{1}{2\pi \cdot 3 \cdot 10^{-12} \cdot (4 \parallel 5)k} = 23.9 mHz$$

$$f_H = 23.9 mHz$$

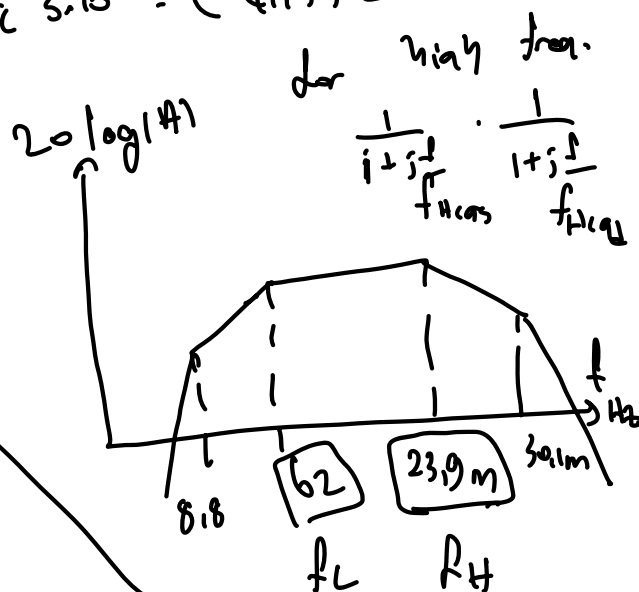

3)

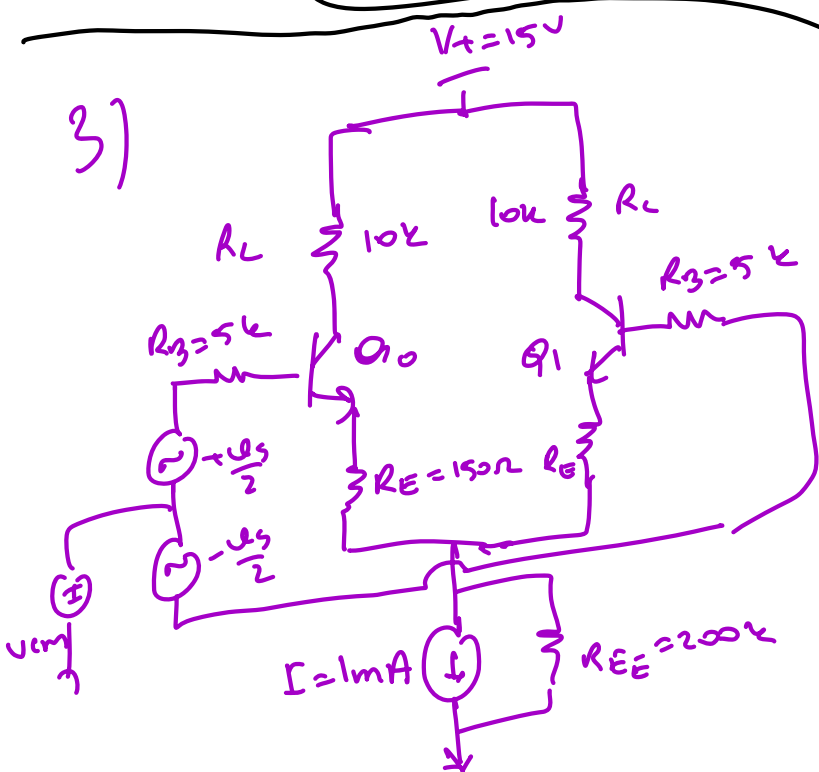

$$\beta = 100$$

$$V_A = \infty$$

$$V_{BE}(on) = 0.7V$$

a) input differential Resistance, R_{id} .

Let's find DC operating point 1st.

$$I_{E0} = I_{E1} = \frac{1\text{mA}}{2} = 0,5\text{mA} \quad \beta \text{ large enough} \quad I_C = I_E$$

$$I_B = \frac{0,5}{100} = 5\mu\text{A}$$

$$V_B = -5 \cdot 5\mu\text{A} = -0,025\text{V} \sim 0$$

$$V_C = 15 - 10 \cdot 0,5 = 10\text{V}$$

$$V_E = -0,1\text{V}$$

$$V_{CE} = 10,7\text{V} \sim 0,2\text{V F.A.} \checkmark$$


$$g_m = \frac{I_C}{V_T} = \frac{0,5}{0,026} = 19,2\text{mA/V} \quad r_{\pi} = \frac{\beta}{g_m} = 5,2\text{k}\Omega$$

$$R_{id} = (R_B + r_{\pi} + (\beta+1)R_E) \times 2$$

$$R_{id} = (5 + 5,2 + 101 \cdot 0,15) \times 2 \Rightarrow R_{id} = 50,7\text{k}\Omega$$

b) Differential half ckt.

S.S. model.

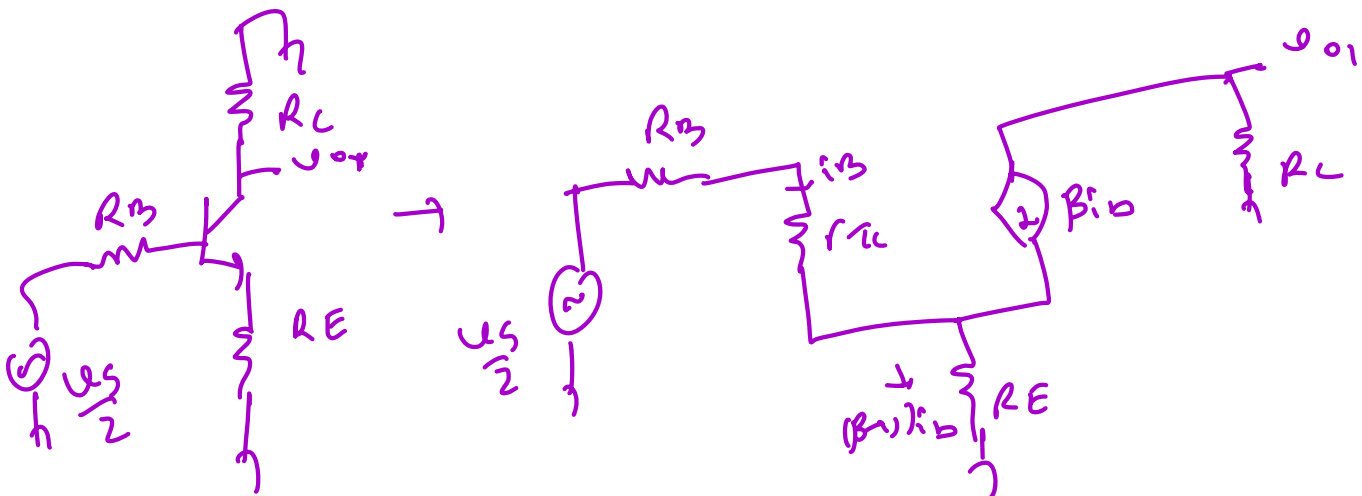

$$u_{o1} = -\beta i_b R_C$$


$$\frac{u_{s1}}{2} = (R_B + r_{\pi}) i_b + (\beta+1) i_b R_E \Rightarrow \frac{u_{o1}}{\frac{u_{s1}}{2}} = \frac{-\beta R_C}{(R_B + r_{\pi}) + (\beta+1) R_E}$$

$$\frac{U_{o1}}{U_s} = \frac{-\beta R_c}{2 \cdot [R_B + r_{\pi} + (\beta+1)R_E]}$$

$$\frac{U_{o2} - U_{o1}}{U_s} = A_{dm} = \frac{\beta R_c}{R_B + r_{\pi} + (\beta+1)R_E} = \frac{100 \cdot 10}{5 + 5.2 + 101 \cdot 0.15}$$

$$A_{dm} = 39.5 \frac{V}{V}$$

c) the common mode gain.

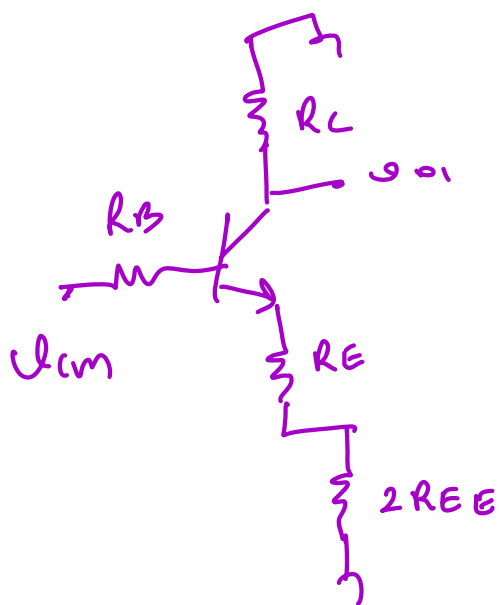

the S.S. model is the same as (b)

with $R_E \rightarrow R_E + 2R_{EE}$

$$\frac{U_{o1}}{U_{cm}} = \frac{-\beta R_c}{(R_B + r_{\pi}) + (\beta+1) \cdot (R_E + 2R_{EE})}$$

$$\frac{U_{o2}}{U_{cm}} = \frac{-\beta R_c}{(R_B + r_{\pi}) + (\beta+1) (R_E + 2R_{EE})}$$

Ideally if everything matches $A_{cm} = \frac{U_{o2} - U_{o1}}{U_{cm}} = 0$

U_{cm} has the same gain in both branches.

$R_c \rightarrow \pm 10\%$

worst case $\rightarrow 1.01 R_c$
 $\rightarrow 0.99 R_c$

$$\frac{U_{o2} - U_{o1}}{U_{cm}} = \frac{\beta \cdot 0.02 \cdot R_c}{(R_B + r_{\pi}) + (\beta+1) (R_E + 2R_{EE})}$$


← absolute value.

$$A_{cm} \approx \frac{100 \cdot 102 \cdot 10}{(5 + 5.2) + 101 \cdot 10.15 + 400} = \boxed{4.9 \cdot 10^{-4}} \text{ worst case.}$$

$$d) CMRR = \frac{A_{dm}}{A_{cm}} = \frac{39.5}{4.9 \cdot 10^{-4}} = 79840$$

$$CMRR = 20 \log(79840) = \boxed{98 \text{ dB}}$$

e) common mode input resistance R_{ic}

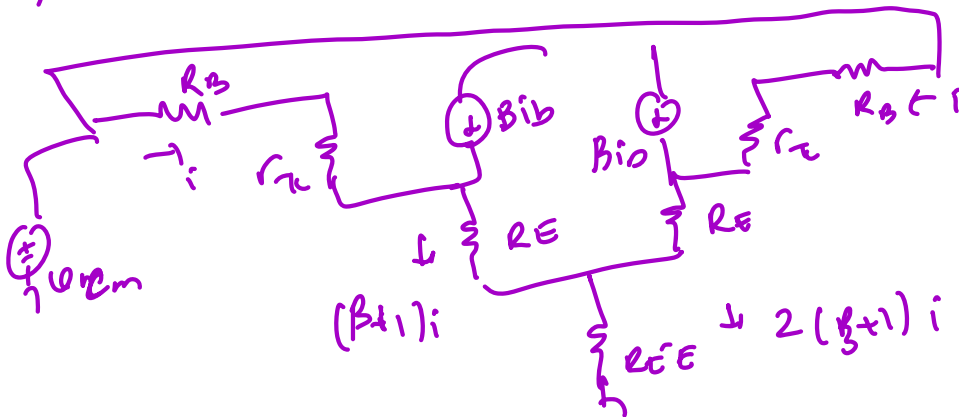


$$U_{cm} = i(R_B + r_{\pi}) + (\beta+1)i R_E + 2(\beta+1)i R_{EE}$$

$$R_{icm} = \frac{U_{cm}}{2i} = \frac{1}{2} [R_B + r_{\pi} + (\beta+1)R_E] + (\beta+1)R_{EE} \quad \leftarrow \text{dominates}$$

$$R_{icm} = \frac{1}{2} [5 + 5.2 + 101 \cdot 0.15] + 101 \cdot 200 \Omega$$

$$\boxed{R_{icm} = 20.2 \text{ m}\Omega}$$

4)

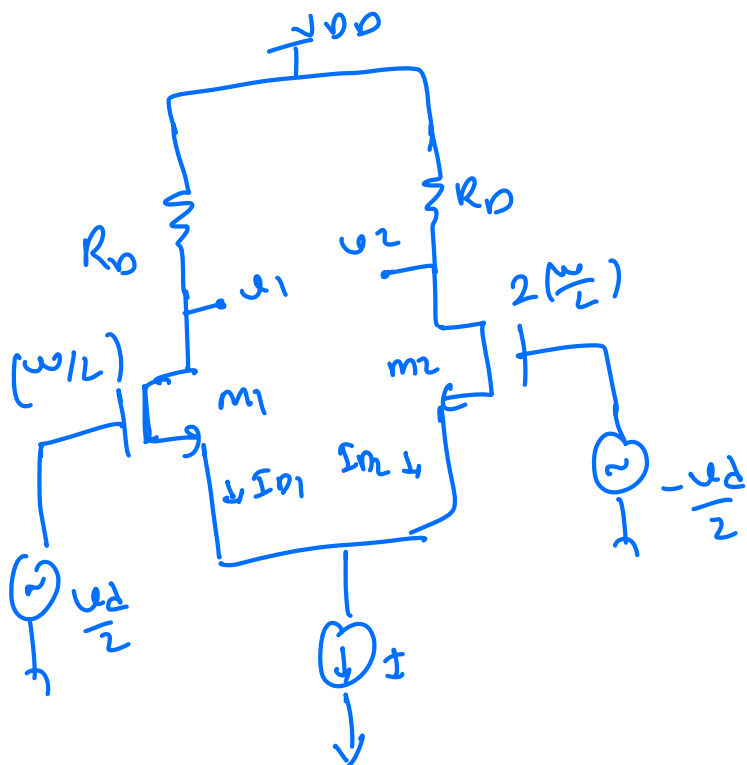

The DC bias on the gate of m_1 and m_2 are same.

m_1 - m_2 have same V_{GS}

then $I_{D2} = 2I_{D1}$


$$I_{D1} = \frac{I}{3}$$

$$K_N = \frac{K_N'}{2} \left(\frac{W}{L} \right)$$

$$I_{D2} = \frac{2I}{3}$$

$$g_{m1} = 2\sqrt{K_{N1} I_{D1}} \quad g_{m2} = 2\sqrt{K_{N2} I_{D2}} = 2g_{m1} \quad \begin{matrix} K_{N2} = 2K_{N1} \\ I_{D2} = 2I_{D1} \end{matrix}$$

S.S. model:

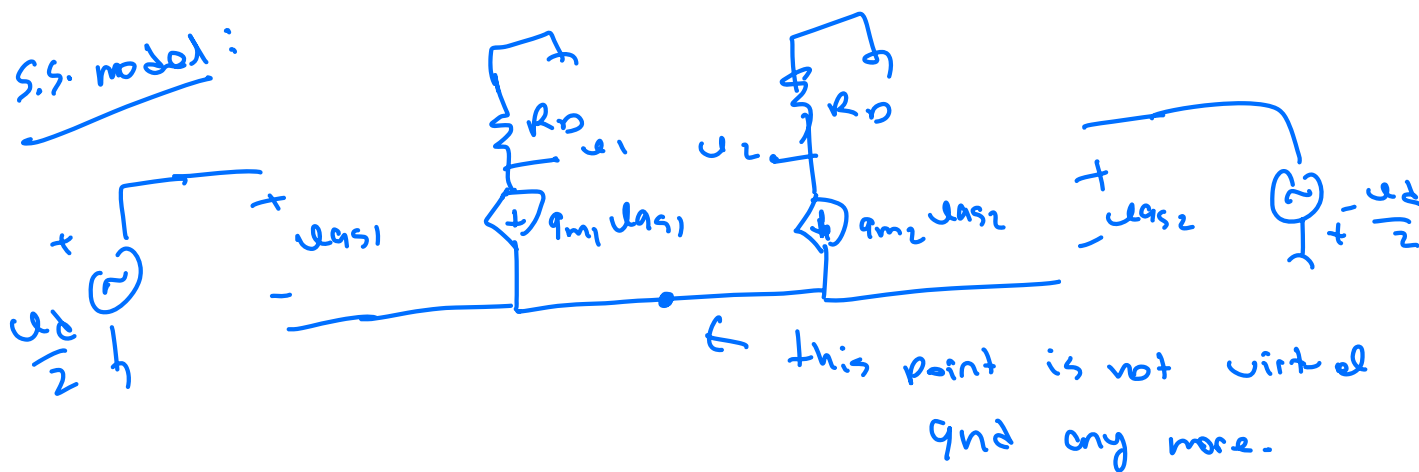

$$g_{m1} v_{gs1} + g_{m2} v_{gs2} = 0$$

$$g_{m1} v_{gs1} + 2g_{m1} v_{gs2} = 0$$

$$v_{gs2} = -\frac{1}{2} v_{gs1}$$

$$-\frac{v_{d1}}{2} + v_{gs1} - v_{gs2} - \frac{v_d}{2} = 0$$

$$v_{gs1} - v_{gs2} = v_d$$

$$v_{gs1} + \frac{1}{2} v_{gs1} = v_d$$

$$v_{gs1} = \frac{2}{3} v_d$$

$$v_{gs2} = -\frac{1}{3} v_d$$

$$v_1 = -g_{m1} v_{gs1} R_0$$

$$v_2 = -g_{m2} v_{gs2} R_0$$

for m_1 - m_2 matched operation.

$$v_{gs1} = \frac{v_d}{2}$$

$$v_{gs2} = -\frac{v_d}{2}$$


$$v_2 - v_1 = R_D (g_{m1} v_{ds1} - g_{m2} v_{ds2})$$

$$v_2 - v_1 = R_D \left(g_{m1} \frac{2}{3} v_d + 2g_{m1} \frac{v_d}{3} \right)$$

$$v_2 - v_1 = \frac{4}{3} g_{m1} R_D v_d$$

$$A_{dm} = \frac{v_2 - v_1}{v_d} = \frac{4}{3} g_{m1} R_D$$

5)

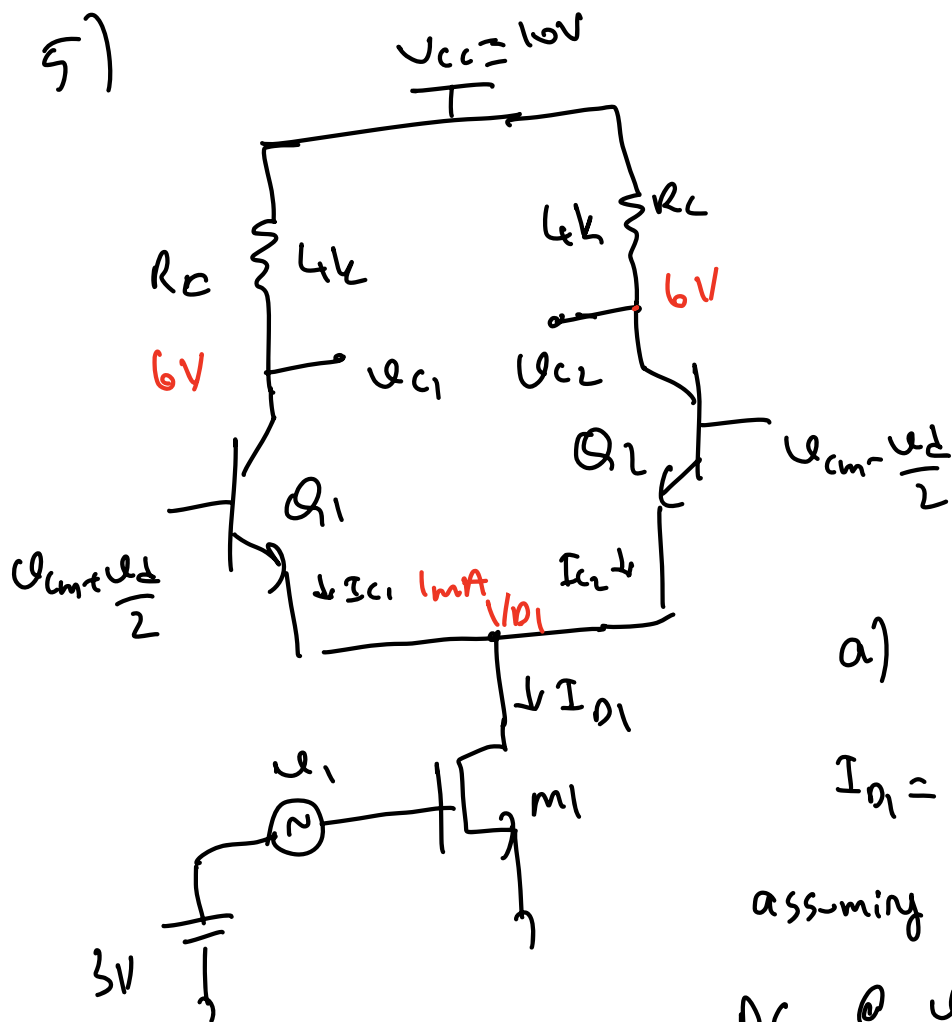

$$\beta = 100$$

$$K_N = 0.5 \frac{\text{mA}}{\text{V}^2}$$

$$V_{TN} = 1\text{V}$$

a) the range of V_{cm}

$$I_{D1} = 0.5 (3 - 1)^2 = 2\text{mA}$$

assuming large β $I_{C1} = I_{E2} = 1\text{mA}$

DC @ v_{c1} and $v_{c2} = 6\text{V}$

$$V_{D1} = V_E = V_{cm} - 0.7$$

for M_1 to stay in sat. $V_{DS} > V_{GS} - V_{TN}$

$$V_{DS} > 2V$$

$$V_{CM} - 0.7 > 2V \Rightarrow V_{CM} > 2.7V$$

for Q_1 and Q_2 to stay in F.A.

$$V_{CE} > 0.2V, V_{CE} \text{ (SAT)}$$

$$2.7V < V_{CM} < 6.5V$$

$$V_C - V_E > 0.2V$$

$$6 - (V_{CM} - 0.7) > 0.2V, V_{CM} < 6.5V$$

this is equ. to B-C diode off. condition.

b) $v_1 = 0.1 \cos(\omega_1 t)$
 $v_2 = 0.001 \cos(\omega_2 t)$ } $\omega_2 \gg \omega_1$ in this case this ckt is an Analog multiplier.

$$i_{D1} = I_{D1} + i_{AC}$$

$0.1 < 0.3V$ so we can treat v_1 as small signal.

$$i_{AC} = g_{m1} \cdot v_1 \quad g_{m1} = \frac{2\sqrt{k_N I_{D1}}}{V} = \frac{2\sqrt{0.5 \cdot 2}}{V} = \frac{2\sqrt{1}}{V}$$

$$i_{AC} = 2 \cdot 0.1 \cos(\omega_1 t) = 0.2 \cos(\omega_1 t) \text{ mA}$$

OR. $i_{D1} = (3 + 0.1 \cos(\omega_1 t) - 1)^2 = \left[2^2 + 4 \cdot 0.1 \cos(\omega_1 t) + 0.01 \cos^2(\omega_1 t) \right]$ ignore this.

$$= 2 + 0.2 \cos(\omega_1 t) \text{ mA}$$

$$i_{D1} = 2 + 0.2 \cos(\omega_1 t) \text{ mA}$$

i_{Q1} splits into Q_1 and Q_2 equally.

$$i_{C1} = i_{C2} = 1 + 0.1 \cos \omega_1 t \text{ mA}$$

$$g_{m1} = g_{m2} = \frac{i_C}{V_T} = \frac{1 + 0.1 \cos \omega_1 t}{0.026} = [38.5 + 3.85 \cos \omega_1 t] \frac{\text{mA}}{\text{V}}$$

$$V_{out} = V_{C2} - V_{C1} = g_m R_C V_d \quad \leftarrow \text{differential operation.}$$

$$V_{out} = [38.5 + 3.85 \cos \omega_1 t] \cdot 4 \cdot 0.001 \cos \omega_2 t$$

$$V_{out} = 0.154 \cos \omega_2 t + 0.015 (\cos \omega_1 t) \cdot (\cos \omega_2 t)$$

@ ω_2 freq

@ $\omega_1 + \omega_2$ freq.
 $\omega_2 - \omega_1$


signals are
mixed. or
multiplied.

* the component @ ω_2 freq. is large in this case.

This is a single balanced multiplier, a double balanced multiplier cancels the ω_2 component.

$$c) V_1 = 0 \text{ and } V_{out} = V_{C2}, \quad \beta = 100, \quad r_o = \frac{1}{\lambda I_D} = \frac{1}{0.02 \cdot 2} = 25 \text{ k}\Omega$$


diff. gain

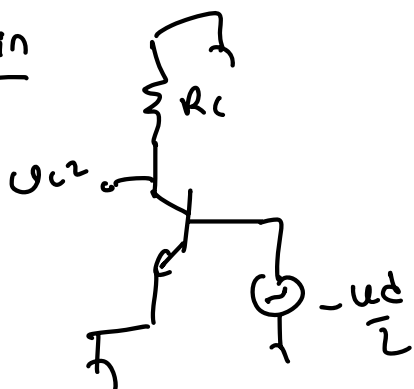

$$V_{C2} = -g_m R_C \cdot \frac{V_d}{2}$$

$$A_{dm} = \frac{V_{C2}}{V_d} = \frac{g_m R_C}{2} = \frac{38.5 \cdot 4}{2} = 77$$

Common mode gain

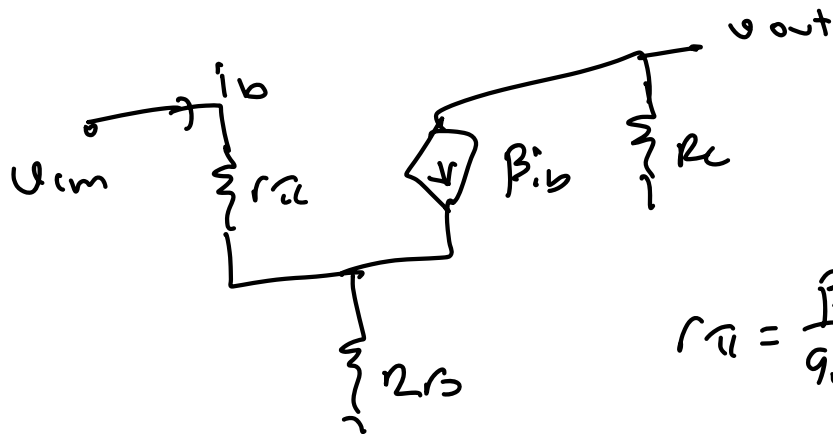

$$r_{\pi} = \frac{\beta}{g_m} = 2.6 \text{ k}\Omega$$

$$v_{cm} = i_b r_{\pi} + (\beta + 1) i_b 2r_o$$

$$v_{out} = -\beta i_b R_C$$

$$A_{cm} = \frac{v_{out}}{v_{cm}} = \frac{-\beta R_C}{r_{\pi} + (\beta + 1) 2r_o} = \frac{-100 \cdot 4}{2.6 + 101 \cdot 50}$$

$$A_{cm} = -0.08$$

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{77}{0.08} = 972 \Rightarrow CMRR = 20 \log_{10}(972)$$

$$CMRR = 59.8 \text{ dB}$$