

Name: _____

Section: _____

Signature: _____

EEE 313 Fall 2013

Bilkent University
Department of Electrical and Electronics Engineering
EEE 313 Electronic Circuit Design

Midterm 1

1 November 2013, 18:00
(4 questions, 120 minutes)

- This is a **closed book**, closed notes exam. No cheat sheet allowed.
- All cell-phones should be completely **turned off**.
- Use a calculator for numerical computations. Carry at least **4 significant digits** during calculations. Your final answer should be at least **3 significant digits**.
- Be sure to write the **units** of all numerical results.
- **Show** all work clearly.
- Please put your **final answer** for each part inside a box for easy identification. Do not give multiple answers, they will not be graded.
- Do not remove the **staple** from the exam sheets or separate pages of the exam. All extra pages must be stamped to your exam.
- You may leave the exam room when you are done. However, please do not leave during the **last five minutes** of the exam.
- At the end of the exam, please stay seated until **all** exam papers are collected.

FET equations:

n-channel MOSFET

$$i_D = K_n (v_{GS} - V_{Tn})^2 \quad \text{SAT}$$

$$i_D = K_n [2(v_{GS} - V_{Tn})v_{DS} - v_{DS}^2] \quad \text{NON-SAT}$$

p-channel MOSFET

$$i_D = K_p (v_{SG} + V_{Tp})^2 \quad \text{SAT}$$

$$i_D = K_p [2(v_{SG} + V_{Tp})v_{SD} - v_{SD}^2] \quad \text{NON-SAT}$$

n-channel JFET


$$i_D = \frac{I_{DSS}}{V_p^2} (v_{GS} - V_p)^2 \quad \text{SAT}$$

$$i_D = \frac{I_{DSS}}{V_p^2} [2(v_{GS} - V_p)v_{DS} - v_{DS}^2] \quad \text{NON-SAT}$$


Please do not write below this line


1. 25 pts.	
2. 30 pts.	
3. 25 pts.	
4. 20 pts.	
Total 100 pts.	

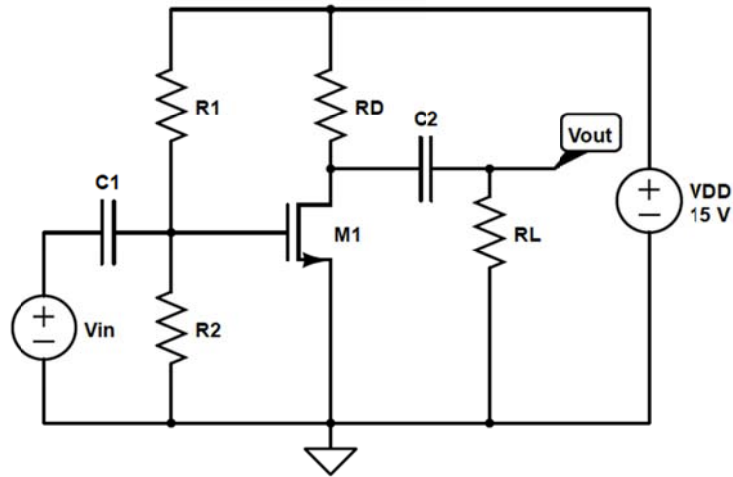- 1) (25 points) Design the common source circuit below using an n-channel MOSFET. The quiescent values are to be $I_{DQ} = 25 \text{ mA}$ and $V_{GSQ} = 7 \text{ V}$. The transconductance is $g_m = 10 \text{ mA/V}$. Let $R_L = 1 \text{ k}\Omega$, $R_I = 1 \text{ k}\Omega$, $A_v = v_{out}/v_{in} = -5$, and $R_{in} = 56 \text{ k}\Omega$. Find:
- (6 points) R_1 and R_2
 - (6 points) R_D
 - (7 points) K_n
 - (6 points) V_{in}



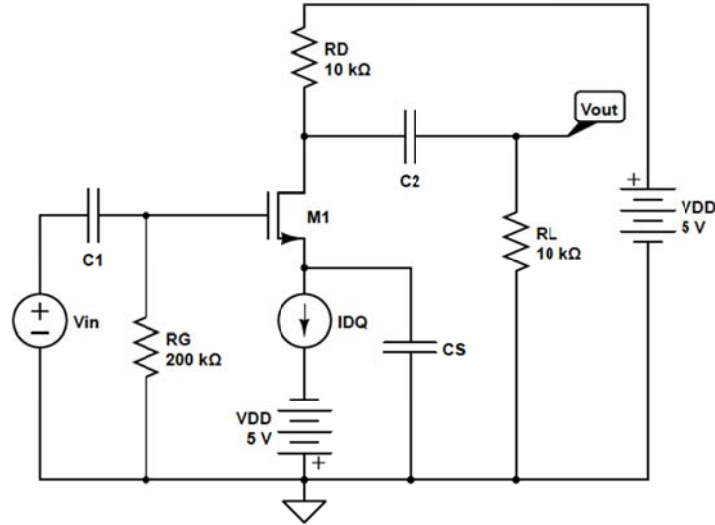2. (30 points) The transistor in the common-source amplifier has parameters threshold voltage, $V_{TN} = 1V$, conductance parameter, $K_n = 0.5mA/V^2$ and Early voltage, $V_A = 100V$. Be careful about the polarities of voltage sources.
- (20 points) Determine I_{DQ} to achieve the maximum undistorted peak-to-peak output swing in the output voltage.
 - (10 points) Find the small-signal voltage gain.




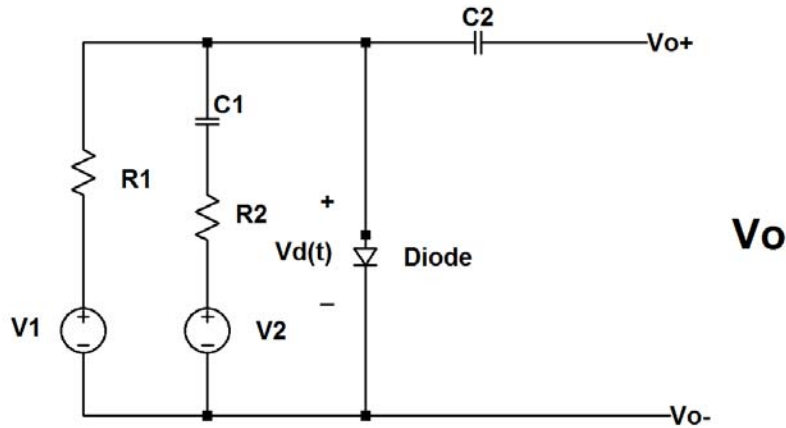

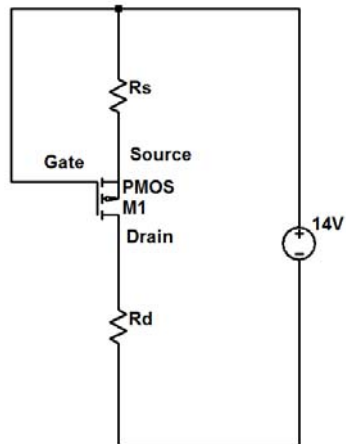3. (25 points) At the circuit given above, the diode $V_\gamma = 0.6$ Volts. The value of the resistor R_2 is 15Ω . $V_1 = 10$ Volts, $R_1 = 2\text{k}\Omega$ and C_2 is very large. $V_2(t)$ is equal to $0.02\cos(1000t)$ Volts. The diode is at room temperature and the ideality factor $n=1$.

Answer the following:

- (6 points) Find the DC current, I_{DQ} , through the diode,
- (6 points) Draw the AC equivalent circuit,
- (7 points) Calculate and plot $v_o(t)$ including the right timing of the waveform.
- (6 points) Do we expect to see an undistorted or distorted sinusoidal wave over the diode? Please state the reason behind your answer.



4. (20 points) At the depletion-mode p-channel MOSFET circuit given above, $V_{TP}=3$ Volts and $K_p=5 \times 10^{-3} \text{ A/V}^2$. $R_d=6 \text{ k}\Omega$ and $R_s=3 \text{ k}\Omega$
- (15 points) Find the bias of the transistor,
 - (5 points) Verify the solution.

