
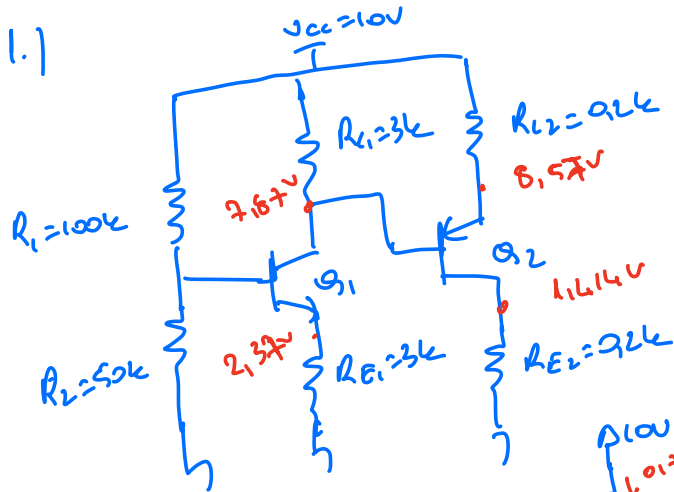


1.]

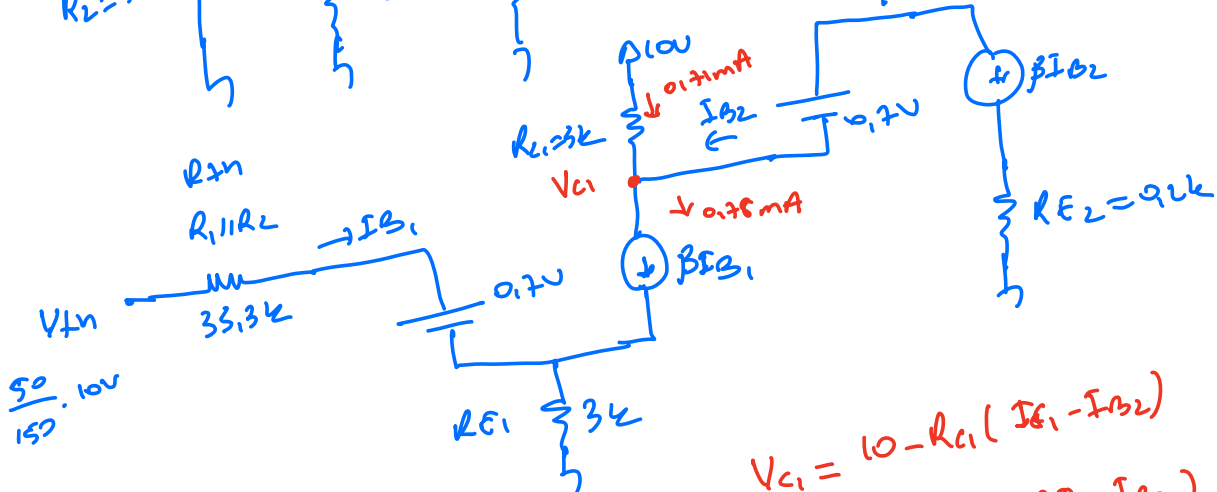

R_{C2} and R_{E2} labeling should be swapped for $Q2$, values are the same. Doesn't affect the result.



$$V_{tn} = R_{tn} \cdot I_{B1} + 0.7V + (\beta + 1) I_{B1} \cdot R_{E1}$$

$$3.33 = 33.3 I_{B1} + 0.7V + 303 I_{B1}$$

$$2.63 = 336.3 I_{B1}$$

$$I_{B1} = 7.82 \mu A$$

$$I_{C1} = 0.78 mA$$

$$I_{E1} = 0.79 mA$$

$$V_{C1} = 10 - R_{C1} (I_{B1} - I_{B2})$$

$$V_{C1} = 10 - 3 \cdot (0.78 - I_{B2}) \quad (1)$$

$$V_{C1} = 10 - R_{C2} (\beta + 1) I_{B2} - 0.7V$$

$$V_{C1} = 10 - 0.2 \cdot 10 \cdot I_{B2} - 0.7$$

$$V_{C1} = 9.3 - 2.0 I_{B2} \quad (2)$$

$$(1) = (2)$$

$$V_{C1} = 10 - 3 \cdot 0.71$$

$$V_{C1} = 7.87V$$

$$V_{E1} = 3 \cdot 0.79$$

$$V_{E1} = 2.37V$$

$$V_{CE1} = 5.5V > 0.2V$$

F.A. ✓

$Q2$ ($7.15V$, $7.07mA$)

$$V_{E2} = 10 - 0.2 \cdot 7.14$$

$$V_{E2} = 8.57V$$

or $V_{C1} + 0.7V$

$$V_{C2} = 0.2 \cdot 7.07$$

$$V_{C2} = 1.414V$$

$$V_{EC2} = 7.15V > 0.2V$$

F.A. ✓

$$7.166 + 3 I_{B2} = 9.3 - 2.0 I_{B2}$$



$$23.2 I_{B2} = 1.64$$

$$I_{B2} = 7.07 \mu A$$

$$I_{C2} = 7.07 mA$$

$$I_{E2} = 7.14 mA$$

2.)

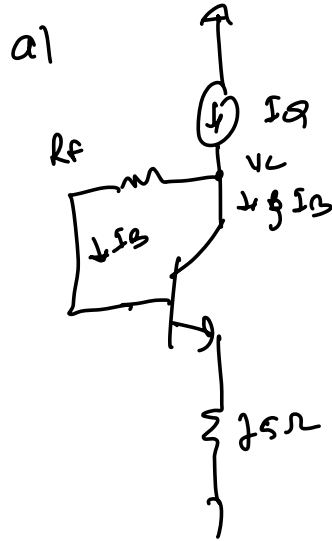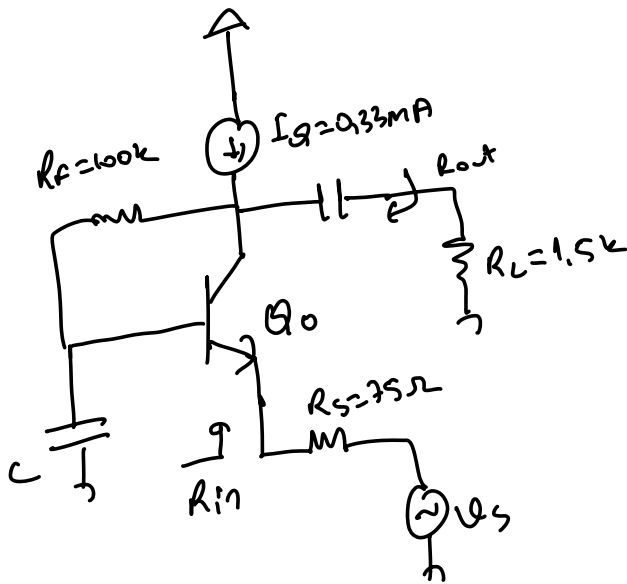

note that

$$V_{CE} = R_F I_B + 0.7$$


$$V_{CE} = 100k \cdot \frac{0.33}{101} + 0.7 = 1.027V$$

$$V_{CE} > 0.2V \quad \text{F.A.} \checkmark$$

$$V_E = 0.075 \cdot 0.33$$

$$V_E = 0.025V$$
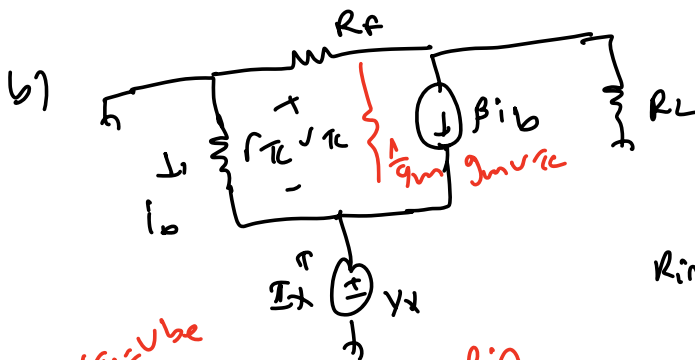
$$r_{\pi} = \frac{\beta \cdot V_T}{I_C} = \frac{100 \cdot 0.026}{0.327} = 7.95k \quad g_m = \frac{\beta}{r_{\pi}} = 12.6 \frac{mA}{V}$$



$v_{ce} = v_{be}$
in class

$$\text{or } \left(\frac{1}{g_m} \parallel r_{\pi} \right) = r_{in}$$

$$v_{be} = -v_e$$

$$g_m v_{be} = -g_m v_e$$


used v_{ce} instead of v_{be} in the solutions

$$r_{in} = \frac{V_T}{I_T} = \frac{r_{\pi}}{\beta + 1} = \frac{7.95k}{101}$$

$$r_{in} = r_e = 78.7\Omega$$

R_F has no effect

Small signal.

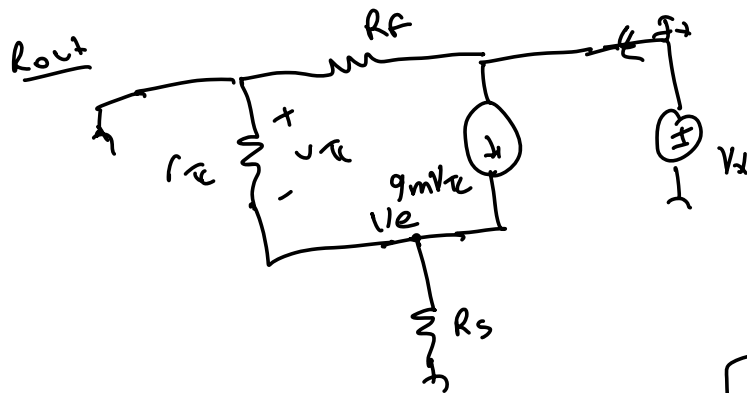

$$I_e = g_m V_{\pi} (R_S \parallel r_{\pi})$$

$$I_e = -V_{\pi}$$


$$-V_{\pi} = g_m V_{\pi} (R_S \parallel r_{\pi})$$

$$V_{\pi} = 0 \text{ or } g_m (-)$$

$$V_{\pi} = 0 \quad \times$$

$$\frac{V_x}{I_x} = R_F = 100k = R_{out}$$

c) Now $r_o = 100k$.

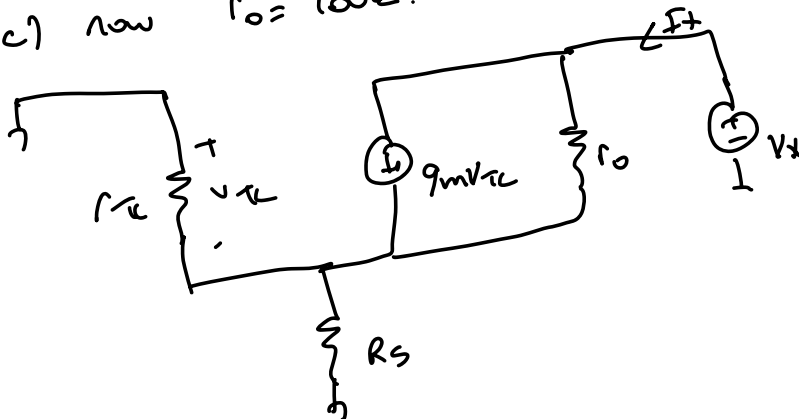

note that R_F is from V_{out} to gnd

so $R_{out} = R_F \parallel R_{out1}$

will add R_F @ the end.

$$V_x = (I_x - g_m V_{\pi}) r_o + I_x (R_S \parallel r_{\pi})$$

$$I_e = -V_{\pi} = I_x (R_S \parallel r_{\pi})$$

$$V_x = [I_x + g_m I_x (R_S \parallel r_{\pi})] r_o + I_x (R_S \parallel r_{\pi})$$

$$\frac{V_x}{I_x} = R_{out1} = [1 + g_m (R_S \parallel r_{\pi})] r_o + R_S \parallel r_{\pi}$$

$$R_{out1} = [1 + 12.6 (0.075 \parallel 7.95)] r_o + 0.075 \parallel 7.95$$


$$R_{out1} = 1945 r_o + 0.075$$

$$R_{out1} = 194.5k$$

$$R_{out} = 194.5 \parallel R_F$$

$$R_{out} = 194.5 \parallel 100$$

$$R_{out} = 66k$$

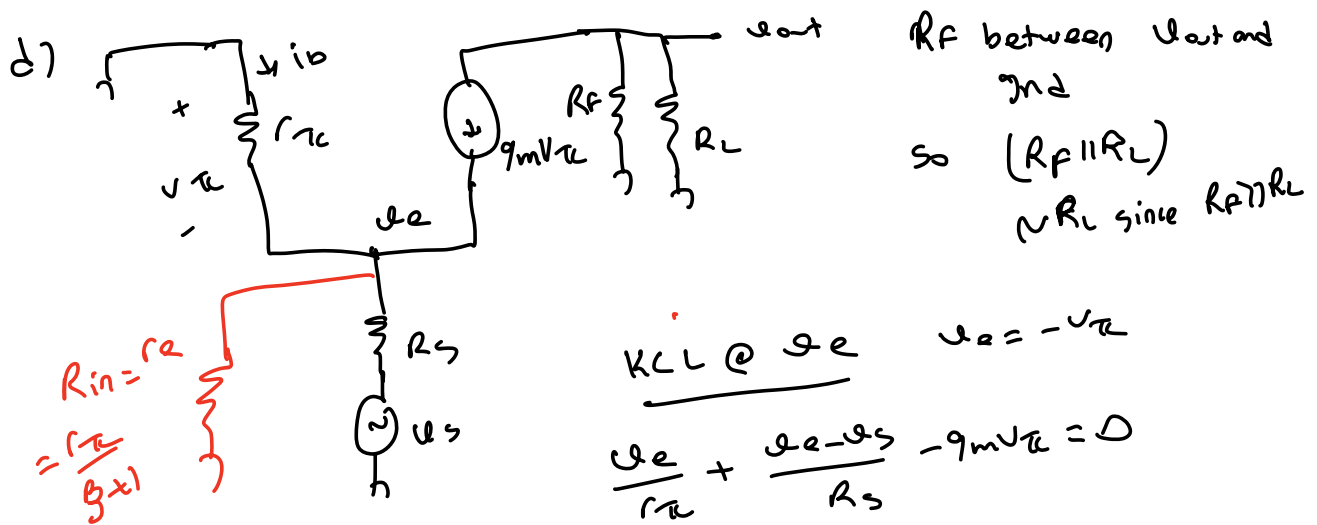

$$\frac{v_S}{R_S} = -v_{\pi} \left(\frac{1}{r_{\pi}} + \frac{1}{R_S} + g_m \right)$$

$$v_{\pi} = -\frac{v_S}{R_S} \cdot \left(r_{\pi} || R_S || \frac{1}{g_m} \right)$$

$$v_{out} = -g_m v_{\pi} (R_L || R_F)$$

$$\frac{v_{out}}{v_S} = \frac{g_m (R_L || R_F)}{R_S} \cdot \left(r_{\pi} || R_S || \frac{1}{g_m} \right)$$

$$r_{\pi} || \frac{1}{g_m} = \frac{\frac{r_{\pi}}{g_m}}{\frac{r_{\pi}}{g_m} + 1} = \frac{r_{\pi}}{\beta + 1}$$

$$\frac{v_{out}}{v_S} = \frac{g_m (R_L || R_F)}{R_S} \cdot \left(\frac{r_{\pi}}{\beta + 1} || R_S \right) = \frac{12.6 \cdot (100 || 1.5)}{0.075} \cdot \left(\frac{0.0381}{0.075} \right)$$

$$\frac{v_{out}}{v_S} = \frac{12.6 \cdot (100 || 1.5)}{g_m (R_F || R_L)} \cdot \frac{78}{78 + 75} = 9.5 \checkmark$$

$\rightarrow \frac{R_{in}}{R_{in} + R_S}$


preferred method

or $v_e = \frac{R_{in}}{R_{in} + R_S} \cdot v_S = -v_{\pi}$ $R_{in} = R_e = \frac{r_{\pi}}{\beta + 1}$


$$v_{out} = -g_m v_{\pi} (R_F || R_L)$$

$$\frac{v_{out}}{v_S} = \frac{R_{in}}{R_{in} + R_S} \cdot g_m (R_F || R_L) \leftarrow \text{same result as the KCL}$$

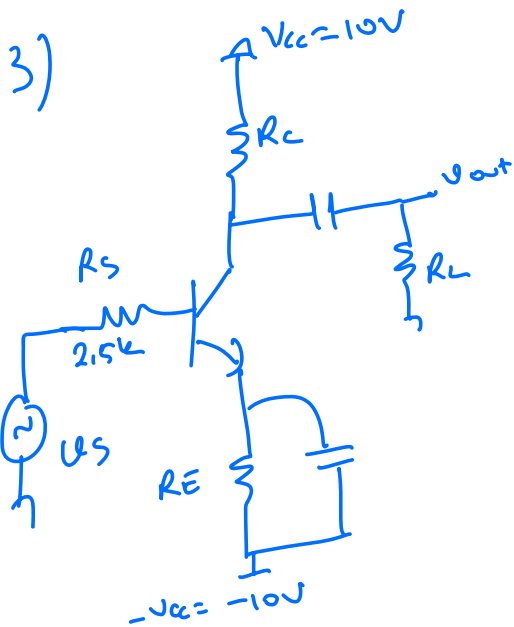we can write v_{π} by looking @ the input resistance, (R_{in})



a) $U_s = 0$ $i_e = 0.5 \text{ mA}$

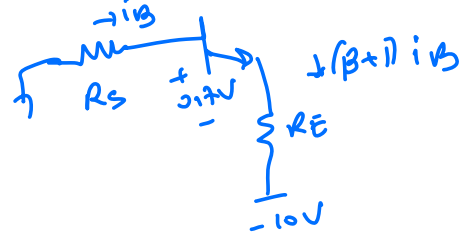

$$R_s i_b + 0.7 \text{ V} + (\beta + 1) i_b \cdot R_E - 10 = 0$$

$$i_e = (\beta + 1) i_b = 0.5 \text{ mA}$$

$$i_b = \frac{0.5}{101} = 4.95 \mu\text{A}$$

$$2.5 \cdot 4.95 \cdot 10^{-3} + 0.7 + 0.5 R_E = 10$$

$$R_E = 18.58 \text{ k}\Omega$$

b) $V_C = V_{CC} - i_C R_C$

$$5 = 10 - 0.5 \cdot \frac{100}{101} \cdot R_C$$


$$R_C = 10.1 \text{ k}\Omega$$

$$V_C = 5 \text{ V}$$

$$V_E = 18.58 \cdot 0.5 - 10$$

$V_{CE} = 0.12 \text{ V}$
F.A.L ✓

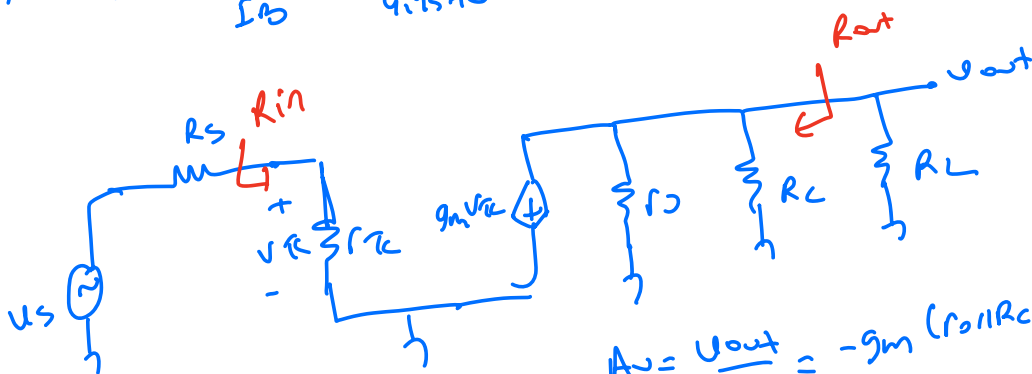c) $r_\pi = \frac{V_T}{I_B} = \frac{0.026}{4.95 \cdot 10^{-3}} = 5.3 \text{ k}\Omega$ $g_m = \frac{\beta}{r_\pi} = 19 \text{ mA/V}$



$$v_{out} = -g_m v_{be} (r_o \parallel R_C \parallel R_L) = A_v \cdot \frac{v_{in}}{r_{in} + R_s}$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o \parallel R_C \parallel R_L) \cdot \frac{r_\pi}{r_\pi + R_s}$$

$$A_v = -19 \cdot (200 \parallel 10 \parallel 10.1) \cdot \frac{5.3}{5.3 + 2.5}$$

$$A_v = -19 \cdot 4.9 \cdot 0.68$$


$$A_v = -63.3 \frac{\text{V}}{\text{V}}$$

d) $R_{in} = R_{ic}$
 $R_{in} = 5.3 \text{ k}\Omega$

for R_{out} find v_{in}
 $v_{in} = 0$

$$R_{out} = r_o \parallel R_L = 200 \parallel 10.1$$

$$R_{out} = 9.6 \text{ k}\Omega$$

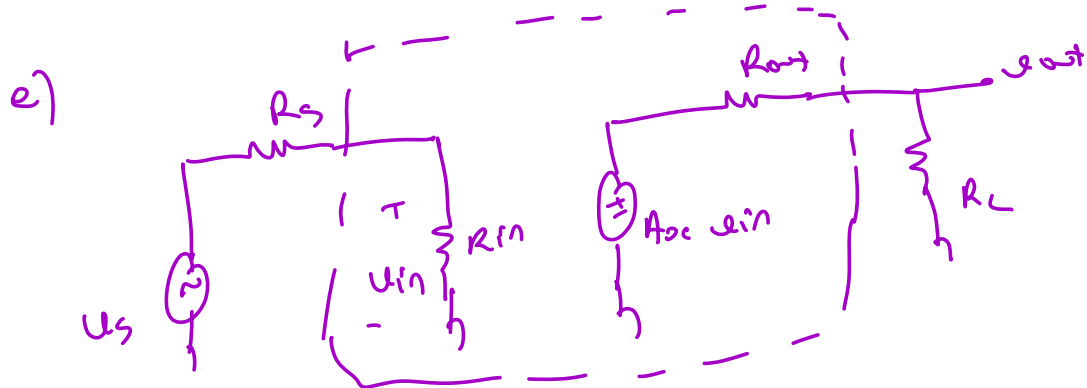

R_s and R_L are handled separately


for A_{oc} $R_L \rightarrow \infty$

$$R_s = 0 \quad R_{out} = 9.6 \text{ k}\Omega$$

$$A_{oc} = -g_m (r_o \parallel R_L) = -19. (200 \parallel 10.1) = -19.966$$

$$A_{oc} = -162.4 \frac{\text{V}}{\text{V}}$$

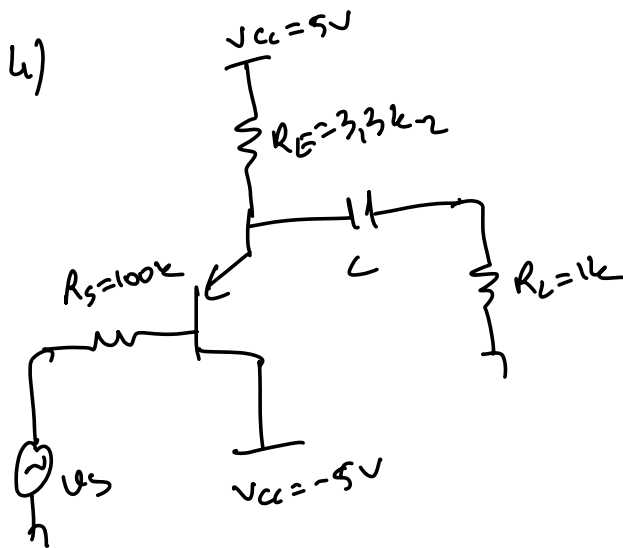
$$\frac{v_{out}}{v_s} = \frac{R_{in}}{R_{in} + R_s} \cdot A_{oc} \cdot \frac{R_L}{R_L + R_{out}} \quad \text{gives the same answer as in (c)}$$



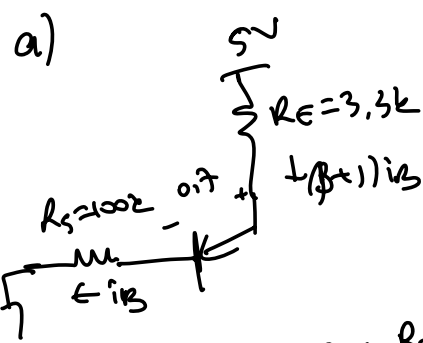b) $r_{\pi} = \frac{V_T}{I_B} = \frac{0.026}{9.92 \cdot 10^{-3}} = 2.6k\Omega$


$g_m = \frac{\beta}{r_{\pi}} = 38.2 \text{ mA/V}$

Note that this is a common collector amplifier.



$5 = (\beta+1)I_B \cdot R_E + 0.7 + R_S I_B$
 $5 = 101 I_B \cdot 3.3 + 0.7 + 100 I_B$
 $4.3V = 433.3 I_B$

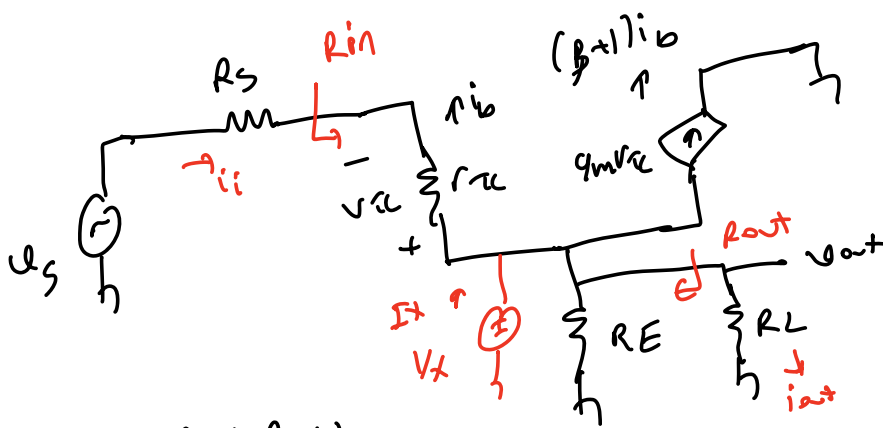$I_B = 9.92 \mu A$
 $I_E = (\beta+1) \cdot I_B = 1 \text{ mA}$



$R_{in} = r_{\pi} + (\beta+1) \cdot (R_E \parallel R_L)$
 RE and RL reflected to the base

$R_{in} = 2.6 + 101 \cdot (3.3 \parallel 1)$
 $R_{in} = 80.1k$

$R_{out} = R_E \parallel R_{out1}$
 and V_S .

$I_x = (\beta+1) I_B$
 $V_x = I_B (r_{\pi} + R_S)$


$\frac{V_x}{I_x} = R_{out1} = \frac{r_{\pi} + R_S}{\beta+1}$

$R_{out1} = 3.3 \parallel \frac{2.6 + 100}{101}$

$R_{out1} = 0.776k$
 $R_{out} = 776\Omega$

Small R_{out}

Large R_{in}
 Common collector.

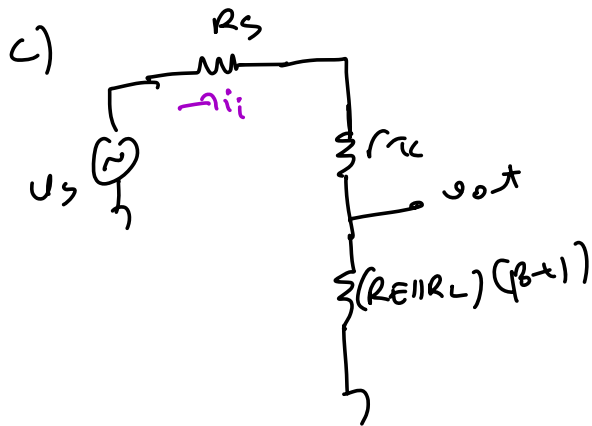

The current through $R_E \parallel R_L$ is $(\beta+1) i_b$ when reflected to the base $(\beta+1) (R_E \parallel R_L)$ since the current in the base is i_b .

$$A_v = \frac{u_{out}}{u_s} = \frac{(\beta+1) \cdot (R_E \parallel R_L)}{(\beta+1) \cdot (R_E \parallel R_L) + r_{\pi} + R_s}$$

$$A_v = \frac{101 \cdot (3.3 \parallel 1)}{101 \cdot (3.3 \parallel 1) + 26 + 100} = \frac{101 \cdot 0.767}{101 \cdot 0.767 + 26 + 100}$$

$$A_v = 0.43 \frac{V}{V}$$



d) $i_{out} = \frac{u_{out}}{R_L}$ $i_i = \frac{u_s}{R_s + r_{\pi} + (\beta+1) R_E \parallel R_L}$

$$\frac{i_{out}}{i_i} = \frac{u_{out}}{u_s} \cdot \frac{R_s + r_{\pi} + (\beta+1) \cdot R_E \parallel R_L}{R_L} = \frac{u_{out}}{u_s} \cdot \frac{R_s + R_{in}}{R_L}$$

$$\frac{i_{out}}{i_i} = 0.43 \cdot \frac{100 + 691}{1} = 77.44 \frac{A}{A}$$

or simply. $i_c = (\beta+1) i_b$, there will be a current division @ the output $\frac{R_E}{R_E + R_L}$ so $\frac{i_{out}}{i_{in}} = (\beta+1) \cdot \frac{R_E}{R_E + R_L} = 101 \cdot \frac{3.3}{3.3+1}$

$$A_i = 77.5$$

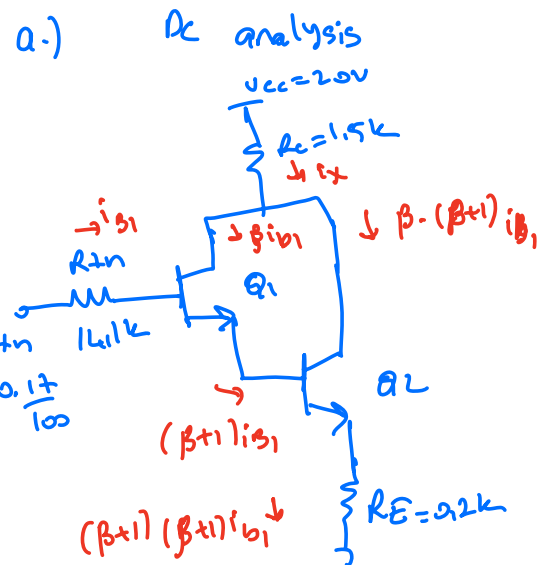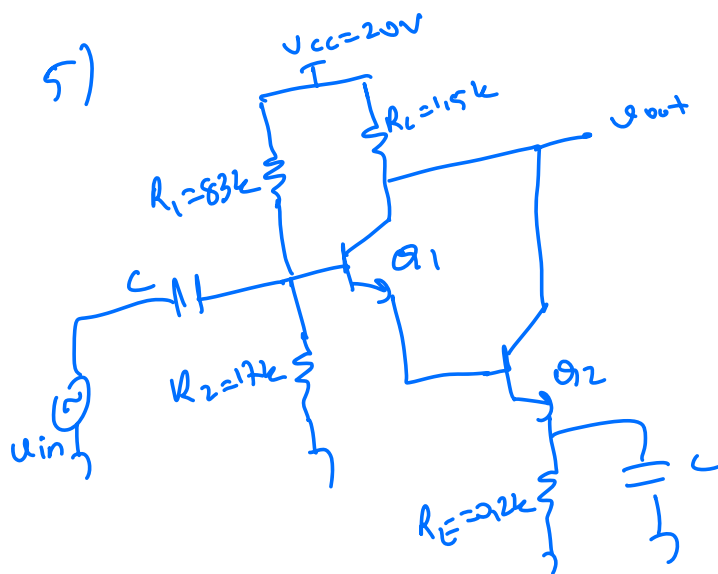

$$i_{B2} = (\beta+1)i_{B1}$$

$$i_{E2} = (\beta+1)i_{B2} = (\beta+1)^2 i_{B1}$$

$$V_{th} = R_{th}i_{B1} + \frac{0.7}{V_{BE1}} + \frac{0.7}{V_{BE2}} + (\beta+1)^2 i_{B1} \cdot R_E$$

$$3.14 = 14.1 i_{B1} + 0.7 + (101)^2 i_{B1} \cdot 0.022$$

$$2 = 2054.3 i_{B1}$$

$$i_{B1} = 0.97 \mu A$$

$$i_{E1} = i_{B2} = (\beta+1)i_{B1} = 0.1 \text{ mA}$$

$$i_{E2} = 9.93 \text{ mA}$$

$$i_x = \beta i_{B1} + \beta \cdot (\beta+1)i_{B1}$$

$$i_x = 0.097 + 9.83$$

$$i_x = 9.93 \text{ mA}$$

$$V_C \text{ for both } V_C = 20 - 15 \cdot 9.93$$

$$V_C = 5.1 \text{ V}$$

$$V_{E2} = 1.99 \text{ V}$$

$$V_{E1} = V_{E2} + 0.7$$

$$V_{E1} = 2.69 \text{ V}$$

This configuration is known as Darlington pair.

Q2 currents are β times Q1 currents.

$$V_{CE2} = 3.11 \text{ V}$$

$$I_{C2} = 9.83 \text{ mA}$$

$$V_{CE1} = 2.61 \text{ V}$$


$$I_{C1} = 0.097 \text{ mA}$$

$$V_{CE1}, V_{CE2} > 0.2 \text{ V}$$

both P.A.V

$$b) \quad r_{\pi 1} = \frac{V_T}{I_{B1}} = \frac{26 \text{ mV}}{0,97 \cdot 10^{-3}} = 26,8 \text{ k} \quad g_{m1} = \frac{\beta}{r_{\pi 1}} = 3,73 \text{ mA/V}$$
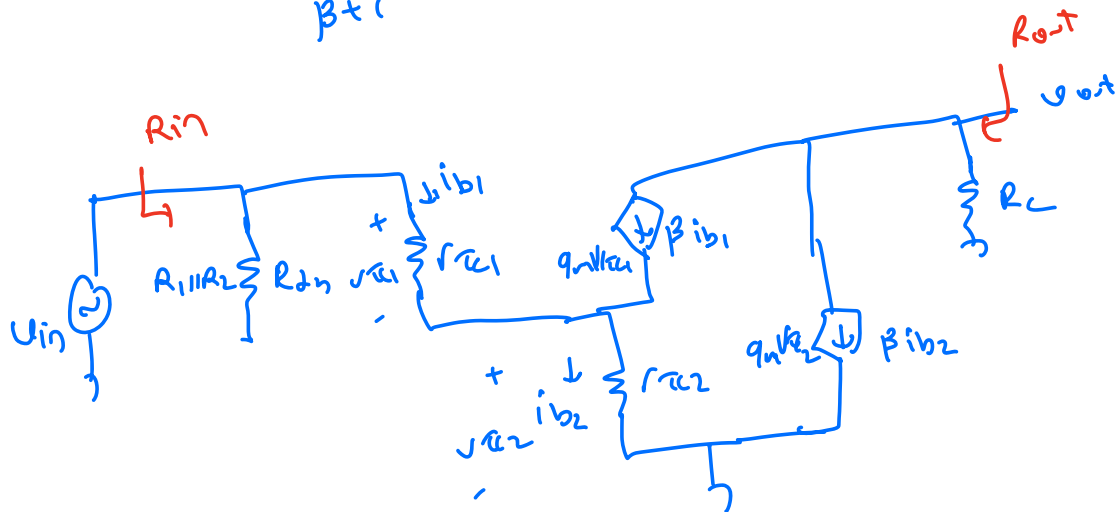
$$r_{\pi 2} = \frac{r_{\pi 1}}{\beta + 1} = 0,27 \text{ k} \quad g_{m2} = 376,9 \text{ mA/V}$$



$$i_{b2} = (\beta + 1) i_{b1}$$

$$u_{out} = [\beta i_{b1} + (\beta + 1) \beta i_{b1}] \cdot R_C$$

$$\frac{u_{out}}{u_{in}} = - \frac{\beta (\beta + 2) R_C}{2 r_{\pi 1}}$$

$$u_{in} = i_{b1} r_{\pi 1} + i_{b2} r_{\pi 2}$$

$$\frac{u_{out}}{u_{in}} = - \frac{100 \cdot 102 \cdot 1,5}{2 \cdot 26,8}$$

$$u_{in} = i_{b1} r_{\pi 1} + (\beta + 1) i_{b1} r_{\pi 2}$$

$$u_{in} = 2 i_{b1} r_{\pi 1}$$

$$A_v = -285,4 \frac{V}{V}$$

c) R_{in}



$$R_{in} = R_{B1} \parallel r_{\pi 1} + (\beta + 1) r_{\pi 2}$$


$$R_{in} = R_{B1} \parallel 2 r_{\pi 1}$$

$$R_{in} = 11,1 \parallel 2 \cdot 26,8$$

$$R_{in} = 11,2 \text{ k}$$


for R_{out} and u_{in} $u_{\pi 1} = u_{\pi 2} = 0$

$$R_{out} = R_C = 1,5 \text{ k} \Omega$$

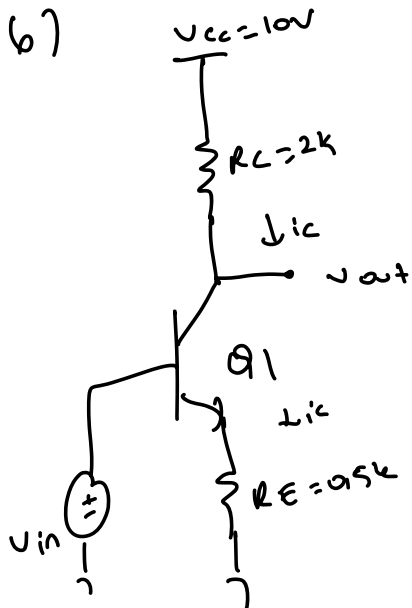

$\beta \rightarrow \text{large}$ implies $i_c = i_e$ (ignore base current)

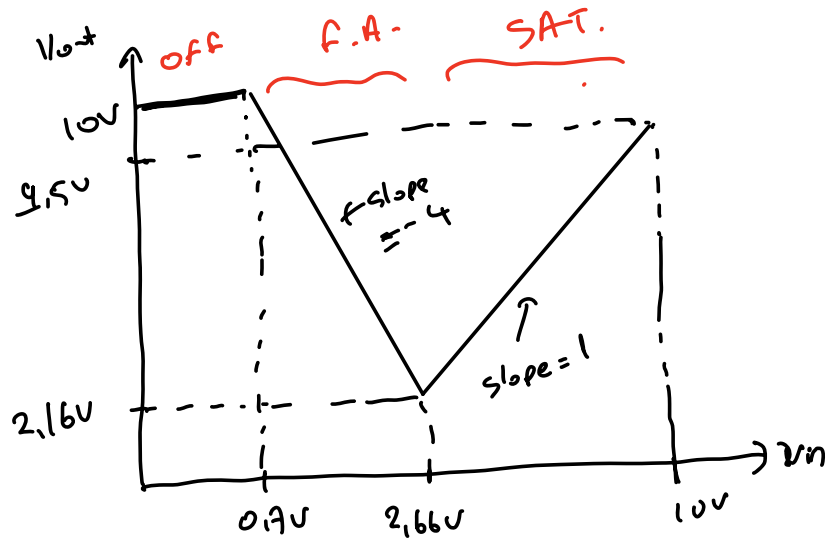$V_{BE(\text{on})} = 0.7V$, $V_{CE(\text{SAT})} = 0.2V$



for $V_{in} < 0.7V$ Q_1 is off $i_c = 0$ $V_{out} = 10 - i_c R_C = 10V$
 (BE and BC junctions are off)

$V_{in} > 0.7V$ Assume forward active

$$i_c = \frac{V_{in} - 0.7}{R_E} \quad V_{out} = V_{CC} - R_C \cdot \frac{V_{in} - 0.7}{R_E} = 10 - 4 \cdot (V_{in} - 0.7)$$

$V_{out} = 12.8 - 4V_{in}$, V_{out} drops linearly with V_{in} .

when $V_{CE} = 0.2V$ Q_1 enters into SAT.

$$V_{CE} = V_{out} - V_C = 12.8 - 4V_{in} - (V_{in} - 0.7) = 0.2$$


$$13.5 - 5V_{in} = 0.2, \quad 5V_{in} = 13.3$$

$$V_{in} = 2.66V$$

$$V_{out} = 2.16V$$

note that $V_{BC} = 0.5V$
 BC junction is on
 at this point.

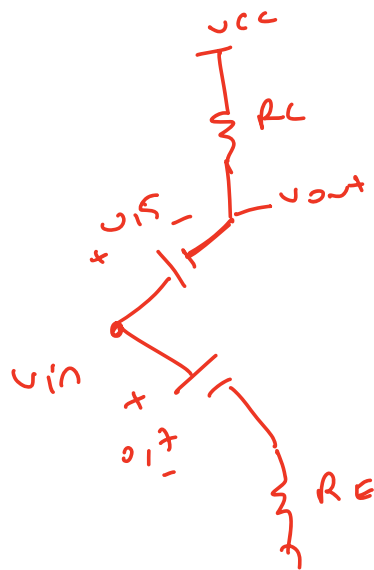once B-E junction is ON. or Q_1 is in SAT.



$V_{out} = V_{in} - 0.5V$ from this point on. ($V_{in} > 2.66V$)

there will be a constant $0.5V$ difference between

V_{in} and V_{out}