

Please submit your solutions to Moodle by Tuesday, 17.10.2023, 23:55.


Homework #1

1. Draw the cross section of a n channel enhancement MOSFET and explain the I_D - V_{DS} relation for

- $V_{GS} < V_{th}$
- $V_{GS} > V_{th}$, and for small V_{DS} voltages
- $V_{GS} > V_{th}$, and for large V_{DS} voltages

You need to explain why there is no current flowing from Gate, Drain, and Source terminals to the substrate.

2.

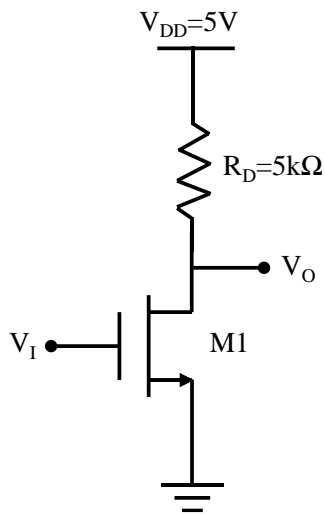


For the circuit on the left $V_{th}=1V$, and $K_N=0.2mA/V^2$

Find and plot V_O vs V_I for $0 < V_I < 5V$.

You don't have to calculate V_O for all the V_I values, but your plot should reflect the actual behavior. Label the states of M1 in your plot. Find the value of V_I when the M1 state changes from TRIODE to SATURATION.

It is not required but you can write a program to plot V_O vs V_I for all values of V_I .

3.

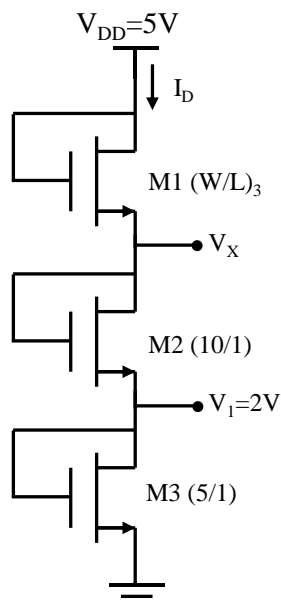


For the circuit on the left $k_N'/2=100\mu A/V^2$, $V_{th}=1V$ for all transistors.

(W/L) ratio of M2 and M3, and $V_I=2V$ are given.

Find V_X , $(W/L)_3$, and I_D .

Verify the transistor states.

4.

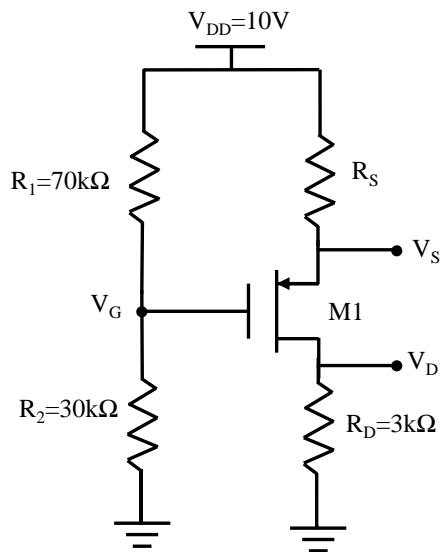


For the pMOS circuit on the left, $K_p=0.25\text{mA/V}^2$, and $V_{tp}=-1\text{V}$

Find the Q point (V_{SD} , I_D) for

- a. $R_S=5\text{k}\Omega$
- b. $R_S=1\text{k}\Omega$

Verify the transistor state for both cases.


5.

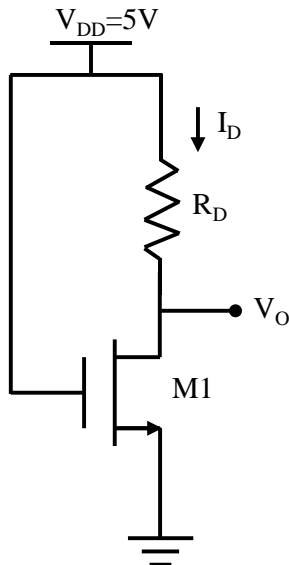

For the nMOS circuit on the left, $K_N=0.2\text{mA/V}^2$, and $V_{th}=1.5\text{V}$

- a. Write the condition in terms of I_D and other circuit parameter for M1 to stay in SATURATION (no numerical values here). Explain the state of M1 as I increase the value of R_D using the load line approach.
- b. Find the range of R_D to keep M1 in SATURATION.

6.

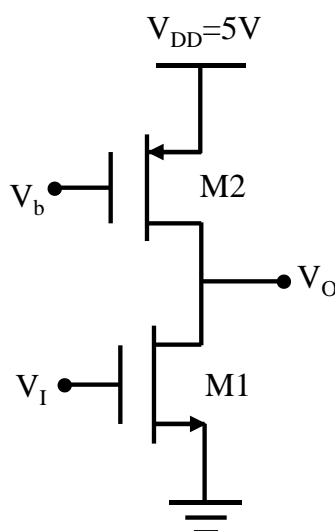

For the circuit on the left, $K_N=K_P$, $V_{tn}=1\text{V}$, $V_{tp}=-1\text{V}$

Find the range of bias voltage V_b , to keep M1 in SATURATION and M2 in TRIODE for

- a. $V_I=2\text{V}$
- b. $V_I=3\text{V}$