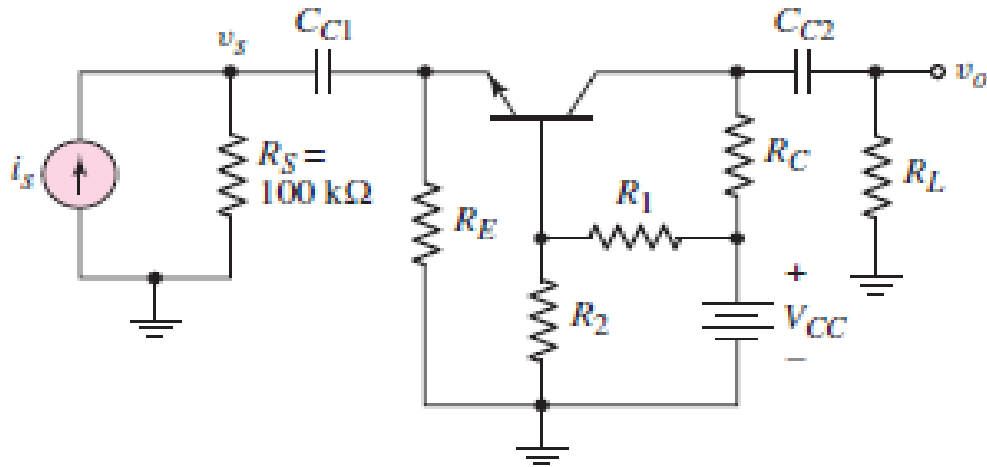


24-4-2021

BILKENT UNIVERSITY Department of Electrical and Electronics Engineering
EEE313 Electronic Circuit Design MidTerm Exam #2
3 questions 120 minutes

Part-1 One question 40 minutes

- **Instructions:**
- Calculators without extensive memory are allowed
- Clearly explain all your answers in order to receive credit
- Put a box around your final answer
- Cheat sheets are not allowed
- Indicate the units for your final answers
- Write your name and student ID on the bottom of every page
- Mail your pdf solutions to eee313exam@bilkent.edu.tr with your student ID number as subject
- Also upload your pdf solutions to Moodle



Q1. (35 points)

The parameters of the shown amplifier are $V_{CC} = 9V$, $R_L = 4k\Omega$, $R_C = 6k\Omega$, $R_E = 3k\Omega$, $R_1 = 150k\Omega$, $R_2 = 50k\Omega$, $C_{C1} = 1\mu F$, and $C_{C2} = 1\mu F$. The transistor parameters are $\beta = 125$, $V_{BE(ON)} = 0.7V$, $V_{CE(SAT)} = 0.2V$, $V_A = \infty$, and $V_T = 0.026V$. The input signal is a small-signal ac current source.

- Derive and numerically determine the Q-point values of I_C and V_{CE} . Verify the state of the transistor.
- Derive and numerically determine the small-signal ac midband transresistance function $R_m = v_o / i_s$.
- Derive and numerically determine the small-signal ac midband voltage gain $A_v = v_o / v_s$.
- Derive and numerically determine the small-signal ac midband input impedance R_{in} of the amplifier. Note that R_s is part of the source.
- Derive and numerically determine the -3dB lower cut-off frequency f_L .