
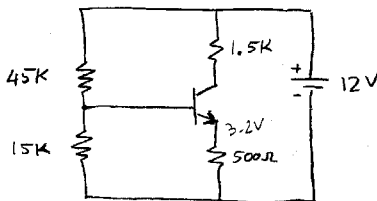


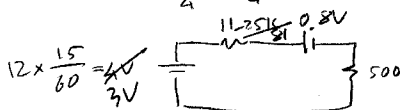1. (18 points) For the circuit given below $\beta=80$, $V_{BE(ON)}=V_T=0.8\text{ V}$ and $V_{CE(sat)}=0.4\text{ V}$. Please find the bias (all voltages and currents) of the transistor.



$$\frac{15 \times 3}{4} = \frac{45}{4} = 11.25\text{ K}$$



$$V_{CE} = 12\text{ V} - 2\text{ K} \times 5\text{ mA} = 2\text{ V}$$

$$V_{CE} = 12\text{ V} - 6.88\text{ V} = 5.11\text{ V}$$


$$I_E = \frac{3\text{ V} - 0.8\text{ V}}{500 + \frac{11250}{81}} = \frac{2.2\text{ V}}{638.9\Omega}$$

$$I_E = 5\text{ mA} \approx I_C = 3.44\text{ mA}$$

$$I_B = \frac{1.44\text{ mA}}{81} = 61.8\mu\text{A}$$

$$I_B = \frac{3.44}{81} = 42.5\mu\text{A}$$

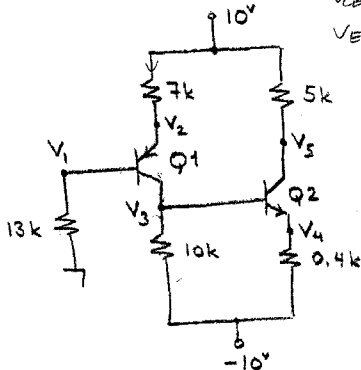
2. (20 points) For the circuit given below $\beta_1=100$, $\beta_2=19$, $V_{EB(ON)1}=1V$ and $V_{EB(ON)2}=1V$. Find the node voltages V_1 , V_2 , V_3 , V_4 and V_5 .



$$V_{CE\text{SAT}} = 0V$$



$$V_{EC\text{SAT}} = 0V$$

Assume Q_1 is active and Q_2 is active

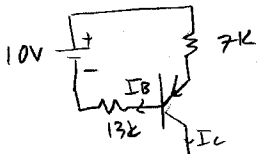

$$I_{E1} = \frac{10 - 1V}{7000 + \frac{13000}{101}} \approx \frac{9}{7000} = 1.28 \text{ mA}$$



For Q_2

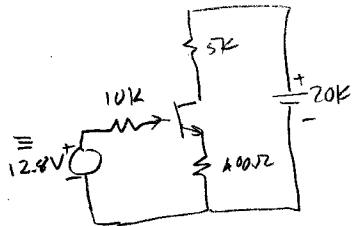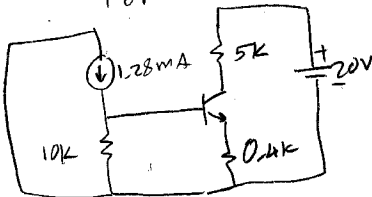

$$I_E = \frac{12.8V - 1V}{400 + \frac{10000}{20}} = \frac{11.8}{900} = 13.1 \text{ mA} \Rightarrow V_{CE} = 20 - 5400(13.1) \times 10^{-3}$$

$\Rightarrow -50.8V$
 \rightarrow not active
 \rightarrow

Assume SAT for $Q_2 \Rightarrow$

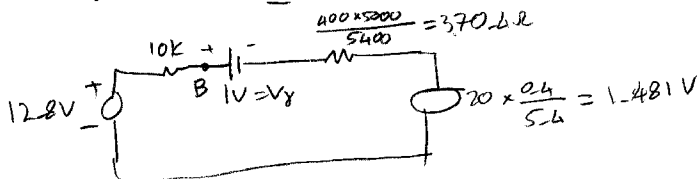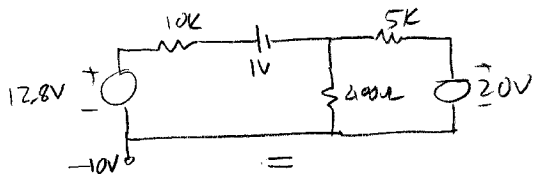

$$\Rightarrow I_B = \frac{12.8 - 1 - 1.481}{10370\Omega} = 0.995\text{mA} \Rightarrow$$

$$V_B - (-10\text{V}) = 12.8\text{V} - 0.995 \times 10000 = 12.8 - 9.95\text{V} = 2.85\text{V}$$

$$\Rightarrow V_3 = -10 + 2.85 = -7.15\text{V}$$


$$V_5 = V_4 = -7.15\text{V} - 1\text{V} = -8.18\text{V}$$

$$V_2 = 10 - 1.28\text{mA} \times 7\text{k} = 1.04\text{V}$$

$$V_1 = 13\text{k} \times \frac{I_{E1}}{\beta + 1} = 13000 \times \frac{1.28 \times 10^{-3}}{101} = 0.164\text{V}$$

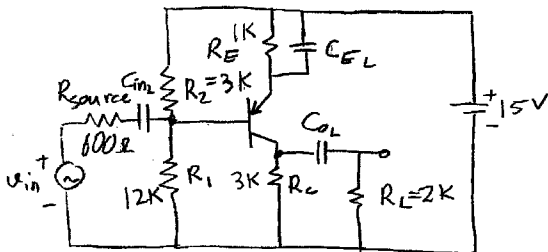3. (30 points, 10 each) For the circuit given below $\beta=90$, $V_{BE(ON)}=V_\gamma=0.5V$ and $V_{CESAT}=0.8V$. Capacitors are very large. Answer the following:

- Find the bias (all voltages and currents) of the transistor.
- Find the peak-to-peak undistorted voltage swing.
- For the purposes of part-c of this question, assume that the DC collector current is $2.5mA$ and the transistor is at forward-active state (which may not be the correct solution). Find the voltage gain of the amplifier.




$$a-) \quad I_E = \frac{\frac{15V \times 3}{3+12} - 0.5}{1000 + \frac{2400}{91}} = \frac{2.5}{1024}$$

$$\frac{3 \times 12}{3+12} = 3 \times \frac{12}{15} = 2.4K$$

$$I_E = 2.44 mA, \Rightarrow I_B = \frac{2.44 mA}{91} = 26.75 \mu A$$
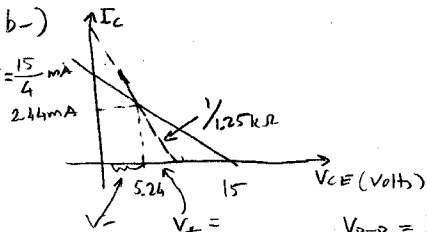
$$V_{CE} = 15V - 4K \times 2.44 mA = 15 - 9.76 = 5.24V$$



$$\frac{3 \times 2}{3+2} = \frac{2 \times 3}{5} = \frac{6}{5} = 1.25K$$

$$V_+ = 2.44 mA \times 1.25K = 3.05V$$

$$V_- = 5.24V - V_{CE,SAT} = 5.24 - 0.8 = 4.44V$$


$$V_{P-P} = 2 \times \min\{3.05, 4.44\}$$

$$V_{P-P} = 6.1V$$

$$c-) \frac{1}{g_m} = \frac{26 \text{ mV}}{2.5 \text{ mA}} = 10.4 \Omega$$

$$r_{\pi} = \frac{90 \times 1}{1 \text{ m}} = 936 \Omega$$

$$g_m = 96.2 \times 10^{-3} \text{ S}$$

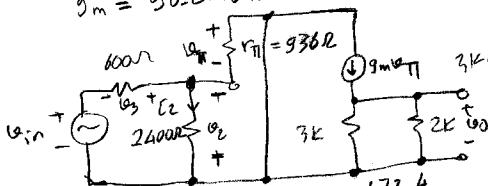

$$3 \text{ k} \parallel 2 \text{ k} = \frac{3 \times 2}{3+2} = \frac{3 \times 2}{5} = \frac{6}{5} = 1.2 \text{ k}$$

$$v_{\pi} = \frac{-2400 \parallel 936}{2400 \parallel 936 + 600} v_{in} = \frac{-673.4}{673.4 + 600} v_{in} = -0.529 v_{in}$$

$$v_o = v_{\pi} \times \frac{1200}{1500} \times 96.2 \times 10^{-3}$$

$$\frac{v_o}{v_{in}} = \frac{1200}{1500} \times 96.2 \times 10^{-3} \times (-0.529) = -0.31 = -61.06$$

another solutions

$$v_2 = \bar{v}_b \times 936$$

$$\bar{v}_2 = \bar{v}_b \frac{936}{2400}$$

$$\Rightarrow v_3 = \left(\bar{v}_b + \bar{v}_b \frac{936}{2400} \right) 600 = \bar{v}_b \left(1 + \frac{936}{2400} \right) 600$$


$$-v_{in} = v_{\pi} + v_3 = \bar{v}_b 936 + \bar{v}_b \left(1 + \frac{936}{2400} \right) 600 = \bar{v}_b (936 + 834) = \bar{v}_b 1770$$

$$v_o = (3 \text{ k} \parallel 2 \text{ k}) 90 \bar{v}_b = 1.2 \text{ k} \times 90 \bar{v}_b = 108 \times \bar{v}_b \times 10^3$$

$$\frac{v_o}{v_{in}} = - \frac{108 \times 10^3}{1770} = -61.01$$

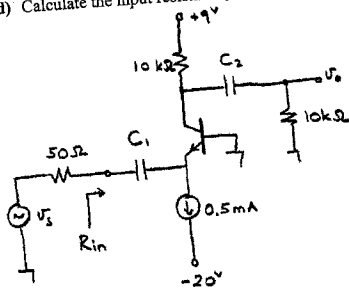4. (32 points) For the amplifier given above $\beta=99$, $V_A=\infty$, $n=1$, $C_1=\infty$, $C_2=\infty$ and $V_{BE(ON)}=V_T=1V$.

- Find the DC base current.
- Draw the small signal equivalent circuit. Show the values of all components.
- Calculate the overall voltage gain, i.e. $A_v = v_o/v_s$.
- Calculate the input resistance, R_{in} .




$$a-) \frac{0.5 \text{ mA}}{\beta + 1} = \frac{0.5 \text{ mA}}{100} = 5 \mu\text{A}$$

b-)

$$g_m = \frac{0.5 \text{ mA}}{26 \text{ mV}} = 19.23 \times 10^{-3} \text{ S}$$
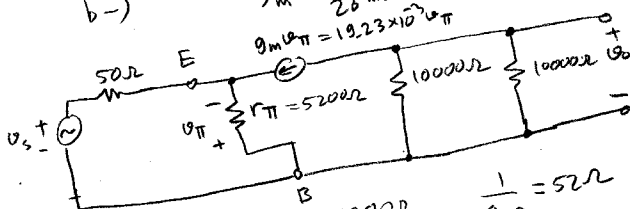
$$g_m r_{\pi} = 19.23 \times 10^{-3} \times r_{\pi}$$



$$r_{\pi} = \frac{26 \text{ mV}}{0.5 \text{ mA}} \cdot 100 = 5200 \Omega$$

$$\frac{1}{g_m} = 52 \Omega$$

$$c-) 5000 \times 19.23 \times 10^{-3} \cdot \frac{50}{\frac{1}{g_m} + 50} = 47.3 \approx \frac{v_o}{v_s}$$

$$d-) R_{in} = \frac{1}{g_m} = 52 \Omega$$