

$$V_{DS} = |V_{DS}| = 1V \quad k_N = k_P = 0.25 \text{ mA/V}^2$$

$$\gamma_1 = 0.02 \text{ V}^{-1} \quad \gamma_2 = 0.01 \text{ V}^{-1}$$

a.) we need to use γ 's of M1 and M2, otherwise we cannot calculate the DC value of V_{out} . (V_L)

$$V_{G1} = \frac{R_3}{R_1 + R_2 + R_3} \cdot 5V = 2V \quad V_{G2} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \cdot 5V = 3V$$

$$I_{D1} = I_{D2} = 0.25 \cdot (5 - 3 - 1)^2 \cdot [1 + \gamma_2 (5 - 4)]$$

$$1 + \gamma_1 V_x = 1 + \gamma_2 (5 - V_x)$$

$$\gamma_1 V_x = 5 \gamma_2 - \gamma_2 V_x$$

$$V_x = 5 \cdot \frac{\gamma_2}{\gamma_1 + \gamma_2} = 5 \cdot \frac{1}{3} = 1.67V$$

$$\frac{m1}{m2} \quad V_{GS} - V_{DS} < V_{DS}$$

$$2 - 1 < 1.67 \quad 2 - 1 < 3.33$$


SAT ✓ SAT ✓

$$I_D = I_{D1} = I_{D2} = 0.25 \cdot 1 \cdot (1 + \gamma_2 \cdot 1.67) = 0.258 \text{ mA} \quad V_{DS1} = 1.67V, V_{DS2} = 3.33V$$

$$g_{m1} = g_{m2} = 2 \sqrt{k_N I_D} = 2 \sqrt{0.25 \cdot 0.258} = 0.508 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\gamma_1 I_D} = \frac{1}{0.02 \cdot 0.258} = 193.8 \text{ k}\Omega$$
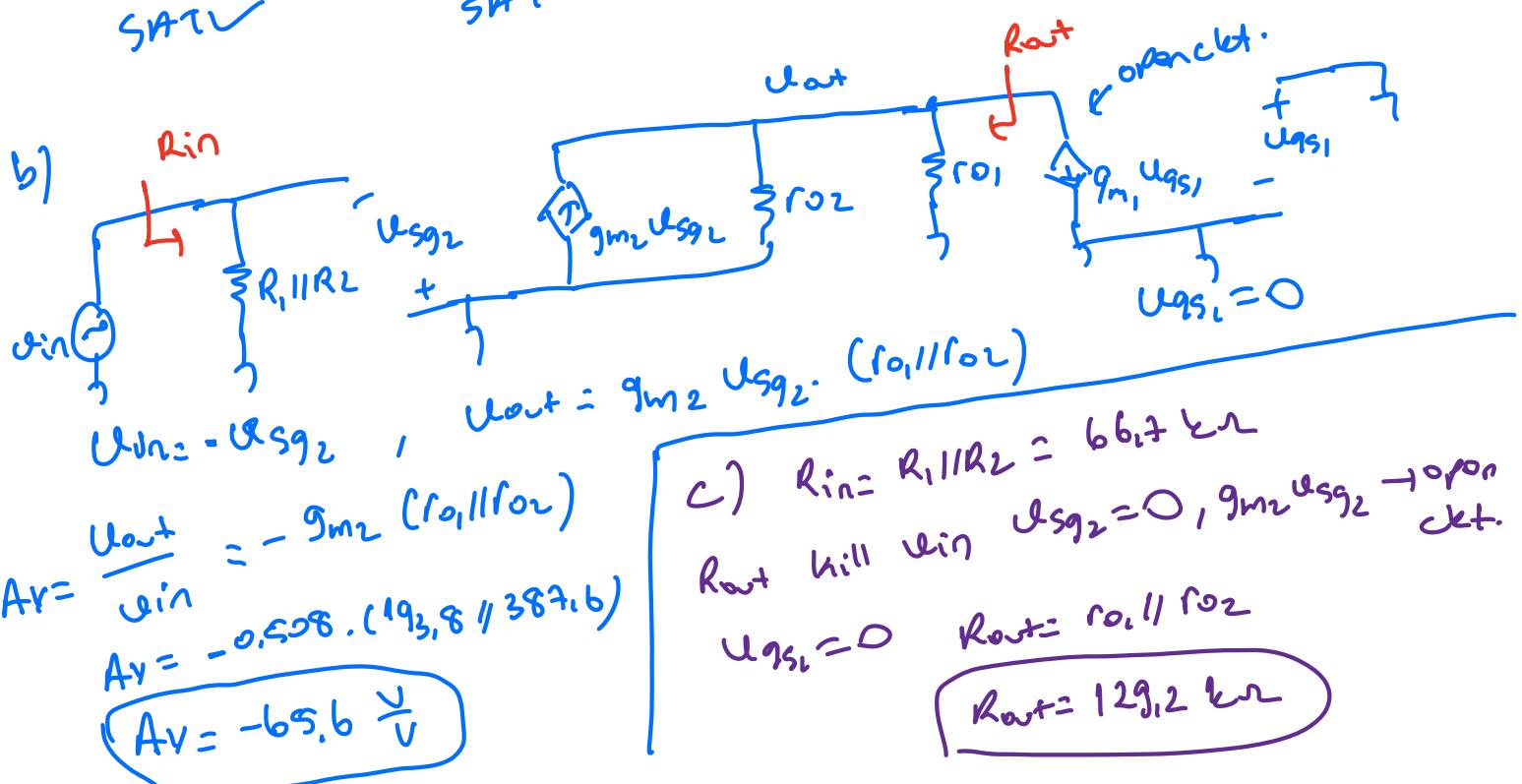
$$r_{o2} = \frac{1}{\gamma_2 I_D} = \frac{1}{0.01 \cdot 0.258} = 387.6 \text{ k}\Omega$$



$$U_{DS} = -U_{SG2}, \quad V_{out} = g_{m2} U_{SG2} \cdot (r_{o1} || r_{o2})$$

c)

$$R_{in} = R_1 || R_2 = 66.7 \text{ k}\Omega$$

Rout will be 0, $U_{SG2} = 0, g_{m2} U_{SG2} \rightarrow 0$ on det.

$$U_{SG1} = 0 \quad Rout = r_{o1} || r_{o2}$$

$$R_{out} = 129.2 \text{ k}\Omega$$

$$A_V = \frac{U_{out}}{U_{in}} = -g_{m2} (r_{o1} || r_{o2})$$

$$A_V = -0.508 \cdot (193.8 || 387.6)$$

$$A_V = -65.6 \frac{V}{V}$$

A Note on calculating g_m and r_o with λ included in DC analysis

$$I_D = k_N (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{2I_D}{2V_{DS}} = 2k_N (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) \quad \text{--- (1)}$$

$g_m = \sqrt{2k_N I_D}$ is not exactly equal to (1)

$g_m = \sqrt{2k_N \cdot I_D \cdot (1 + \lambda V_{DS})}$ is exact.

But for simplicity we accept the error and use

in the solution.

* You do not have to worry abt this, unless you are told to do so.


Similarly for r_o

$$\frac{1}{r_o} = \frac{2I_D}{2V_{DS}} = 2k_N (V_{GS} - V_{TH})^2 \Rightarrow r_o = \frac{1}{2I_D} \text{ is not accurate either.}$$

in this case.

* But you can use the expressions derived in the class.
as we did in the solution.

2)

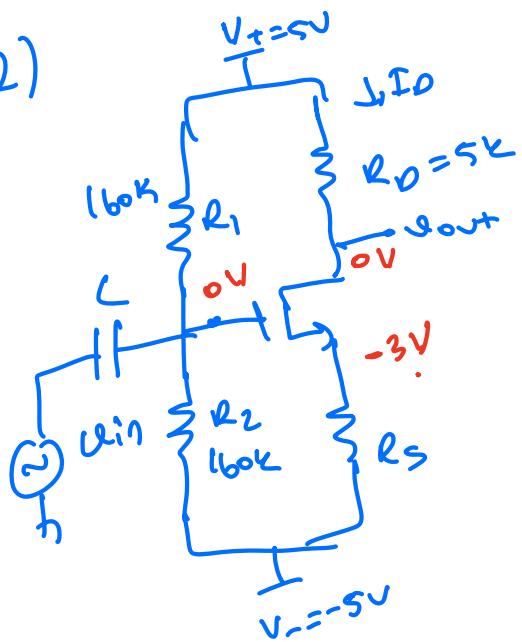

$$K_N = 0.25 \frac{mA}{V_L} \quad V_{TN} = 1V, \alpha = 0.01 V^{-1}$$

a) If we want 0V DC @ last

$$\text{then } I_D = 1mA$$

$$U_G = 0 \text{ note } R_1 = R_2.$$

$$V_S = -5 + R_S$$


$$I = 0.25 (5 - R_S - 1)^2$$

$$I = (4 - R_S)^2$$

$$I = 16 - 8R_S + R_S^2 \quad \boxed{R_S \geq 2k} \quad R_S = 6k$$

$$V_S = 3V, V_{GS} \stackrel{V_{DS}}{\leq} V_{DS} \quad \begin{matrix} 3-1 \\ 3 \end{matrix} \quad \text{SAT} \checkmark$$

b)

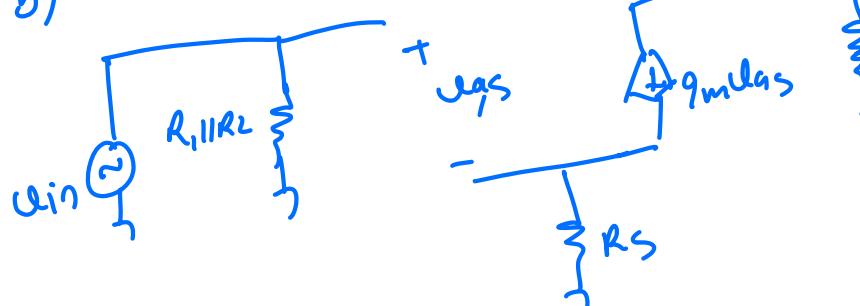

$$g_m = 2\sqrt{K_N I_D}$$

$$g_m = 2\sqrt{0.25 \cdot 1} = \frac{1}{V} mA$$

$$r_o = \frac{1}{2 I_D} = \frac{1}{0.01 \cdot 1} = 100k\Omega$$


$$U_{out} = -g_m U_{ds} R_D \quad \frac{U_{out}}{U_{in}} = \frac{-g_m R_D}{1 + g_m R_S}$$

$$U_{in} = U_{out} + g_m U_{ds} R_S$$

$$U_{in} = U_{out} (1 + g_m R_S)$$

$$A_V = \frac{-1.6}{1+1.2} = 1.67 \checkmark$$

c) we include r_o now.

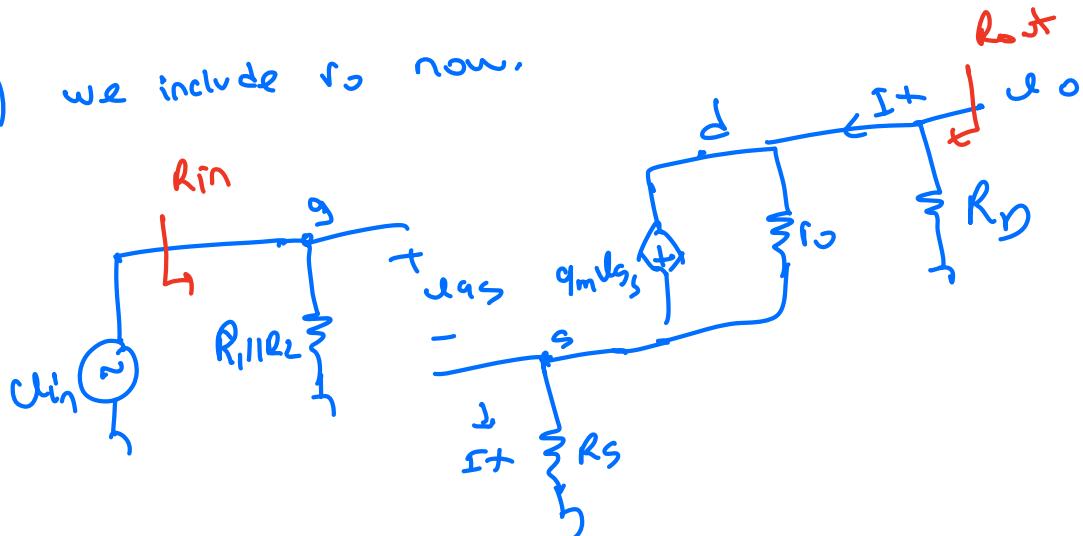

$$U_{QS} = U_{in} - U_S$$

KCL @ the source.

$$\frac{U_S}{R_S} + \frac{U_S - U_O}{r_o} - g_m U_{QS} = 0$$

$$\frac{U_S}{R_S} + \frac{U_S - U_O}{r_o} - g_m(U_i - U_S) = 0$$

$$U_S \left(\frac{1}{R_S} + \frac{1}{r_o} - g_m \right) = g_m U_i + \frac{U_O}{r_o}$$

$$U_S = \left(g_m U_i + \frac{U_O}{r_o} \right) \cdot \left[R_S \parallel r_o \parallel \frac{1}{g_m} \right]$$

$$g_m U_{in} + U_O \left(\frac{1}{r_o} + \frac{1}{R_D} \right) = \frac{1}{r_o \parallel \frac{1}{g_m}} \cdot \left(R_S \parallel r_o \parallel \frac{1}{g_m} \right) \cdot \left(g_m U_i + \frac{U_O}{r_o} \right)$$

$$= \frac{1}{r_o \parallel \frac{1}{g_m}} \cdot \frac{R_S \parallel \frac{1}{g_m}}{R_S + \left(r_o \parallel \frac{1}{g_m} \right)}$$

$$g_m U_{in} + U_O \left(\frac{1}{r_o} + \frac{1}{R_D} \right) = \frac{R_S}{R_S + \left(r_o \parallel \frac{1}{g_m} \right)} \cdot \left(g_m U_i + \frac{U_O}{r_o} \right)$$

$$g_m U_{in} \left[1 - \frac{R_S}{R_S + \left(r_o \parallel \frac{1}{g_m} \right)} \right] = U_O \left[\frac{1}{r_o} \cdot \frac{R_S}{R_S + \left(r_o \parallel \frac{1}{g_m} \right)} - \frac{1}{R_D} - \frac{1}{R_D} \right]$$

$$g_m U_{in} \left[\frac{r_o \parallel \frac{1}{g_m}}{R_S + r_o \parallel \frac{1}{g_m}} \right] = U_O \left[\frac{1}{r_o} \cdot \frac{-r_o \parallel \frac{1}{g_m}}{R_S + r_o \parallel \frac{1}{g_m}} - \frac{1}{R_D} \right]$$

$$\frac{g_m \left[r_o \parallel \frac{1}{g_m} \right]}{R_S + r_o \parallel \frac{1}{g_m}}$$

$$A_V = \frac{U_O}{U_{in}} = \frac{\frac{1}{r_o} \cdot \frac{-r_o \parallel \frac{1}{g_m}}{R_S + r_o \parallel \frac{1}{g_m}} - \frac{1}{R_D}}{\frac{1}{r_o} \cdot \frac{-r_o \parallel \frac{1}{g_m}}{R_S + r_o \parallel \frac{1}{g_m}} - \frac{1}{R_D}}$$

$$\frac{r_o + \infty}{\frac{g_m \cdot \frac{1}{g_m}}{R_S + \frac{1}{g_m}}} = \frac{-\frac{1}{R_D}}{-\frac{1}{R_D}}$$

$$A_V = \frac{-g_m R_D}{1 + g_m R_S}$$

Same as part b.


with some reasonable simplification if we assume $r_{coll} \approx \frac{1}{g_m}$ (b) $\frac{1}{g_m}$

$$A_V = \frac{V_o}{I_{in}} \approx \frac{\frac{g_m \cdot \frac{1}{g_m}}{R_s + \frac{1}{g_m}}}{\frac{1}{R_o} \cdot \frac{\frac{1}{g_m}}{R_s + \frac{1}{g_m}} - \frac{1}{R_o}} = \frac{\frac{g_m}{1+g_m R_s}}{\frac{1}{R_o} \cdot \frac{1}{1+g_m R_s} - \frac{1}{R_o}}$$

reduces the
gain

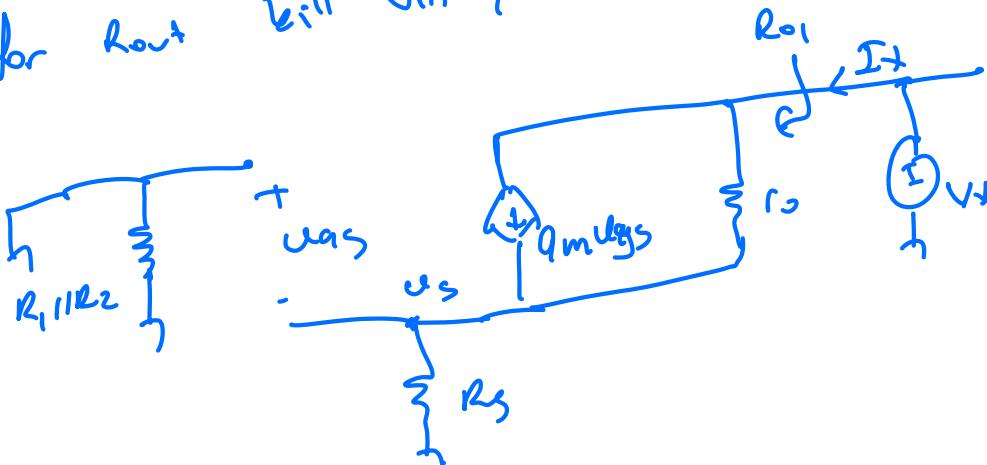d) $R_{in} = R_1 \parallel R_2 = 802 \Omega$.

for R_{out} will V_{in} , let's add R_o at the end.



$$U_{q_m} = U_q - U_S = -U_S$$

$$U_S = I_x R_S$$

$$V_X = (I_x - q_m U_{q_m}) r_o + I_x R_S$$

$$V_X = \left\{ I_x - q_m (-I_x R_S) \right\} r_o + I_x R_S$$

$$V_X = I_x \left[(1 + q_m R_S) r_o + R_S \right]$$

$$R_o = (1 + 1.2) \cdot 100 \Omega$$

$$R_o = 302 \Omega$$


$$R_o = R_o \parallel R_D$$

$$R_o = 302 \parallel 5$$

$$R_o = 4.92 \Omega$$

$$\frac{R_o}{I_d} = \frac{(1 + q_m R_S) r_o + R_S}{I_d} = R_o$$

3)

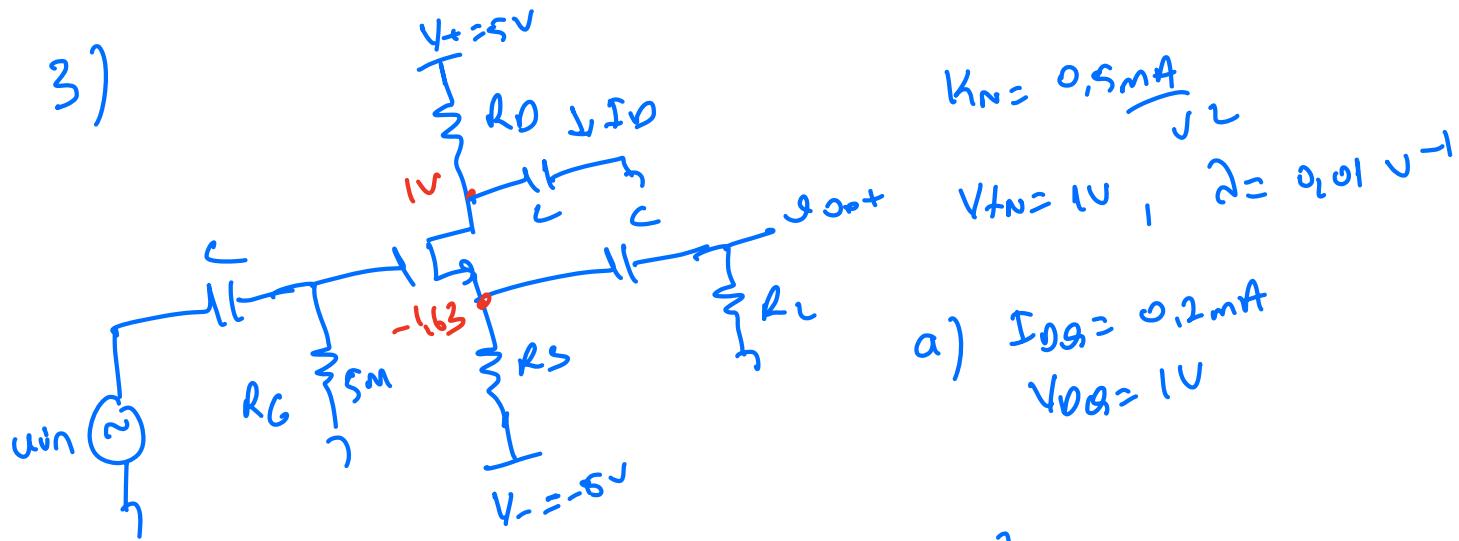

$$a) I_{DS} = 0.2 \text{ mA}$$

$$V_{DS} = 1 \text{ V}$$

$$V_0 = 5 - R_L I_D$$

$$I = 5 - R_L \cdot 0.2$$

$$R_L = 20 \text{ k}\Omega$$

$$0.2 = 0.5 (V_{GS} - 1)^2$$

$$V_{GS} = \pm 0.63 \Rightarrow V_{GS} = 0.63 \text{ V}$$


$$V_0 = 0, \text{ so } V_S = -0.63 \text{ V}$$

$$-5 + R_S \cdot 0.2 = -0.63 \quad R_S = 16.85 \text{ k}\Omega$$

$$V_{GS} - V_{TN} < V_{DS} \text{ satisfied}$$

$$b) g_m = 2\sqrt{0.5 \cdot 0.2} = 0.63 \frac{\text{mA}}{\text{V}}$$
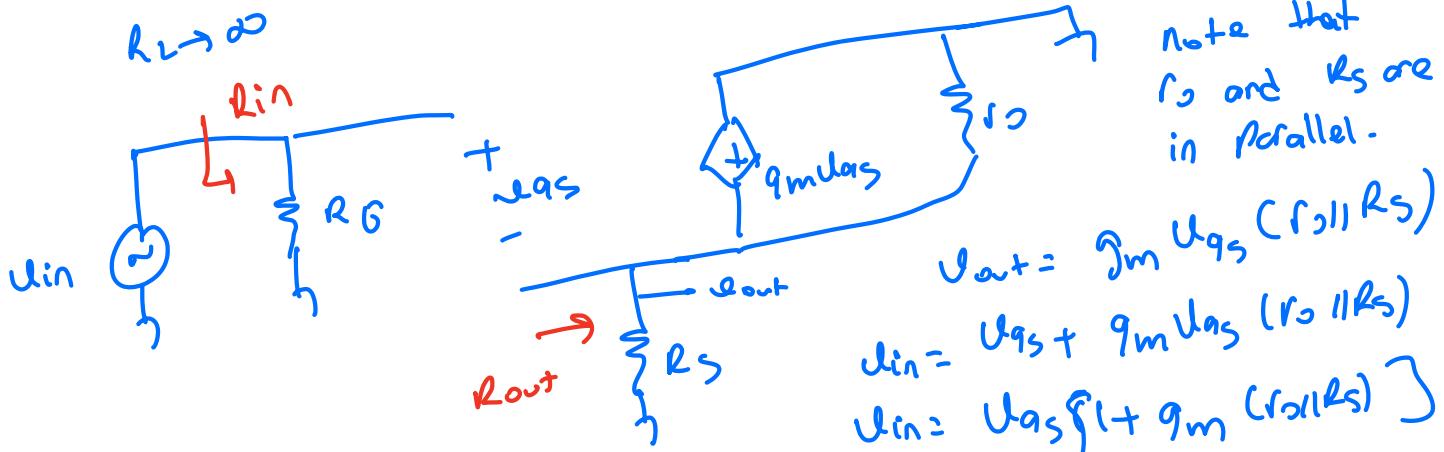
$$r_o = \frac{1}{0.01 \cdot 0.2} = 500 \text{ }\Omega$$



$$A_v = \frac{u_{out+}}{u_{in}} = \frac{g_m (r_o || R_S)}{1 + g_m (r_o || R_S)}$$


$$A_v = \frac{0.63 \cdot (500 || 20)}{1 + 0.63 \cdot (500 || 20)} = \frac{0.63 \cdot 19.23}{1 + 0.63 \cdot 19.23} = 0.92 \text{ V/V}$$

* this is a common drain amplifier and the gain should be < 1

$$c) R_{in} = R_b = 5\text{ M}\Omega$$

$$R_{out} = \frac{1}{g_m} \parallel R_S \parallel r_o \quad (\text{short cut})$$

current source = $\frac{1}{g_m}$

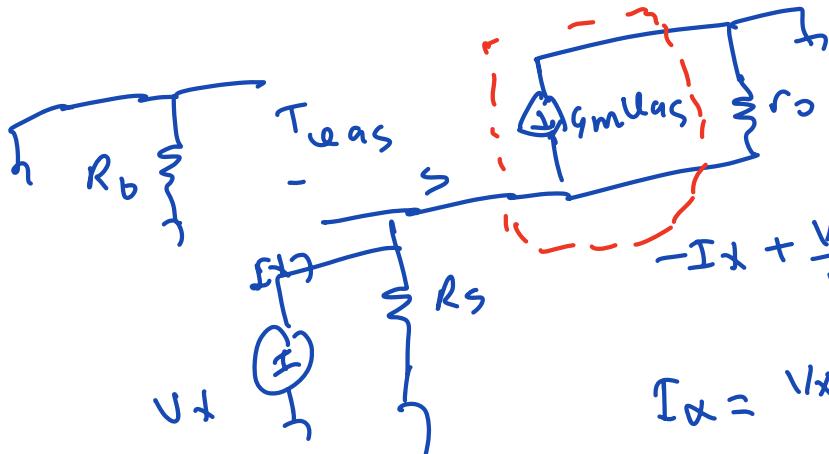

$$U_{AS} = U_g - U_S$$

$$U_{GS} = -U_S \quad V_S = V_x$$

VCL @ the source


$$V_L = -I_x + \frac{V_x}{R_S} - g_m U_{AS} + \frac{V_L}{R_L} = 0$$

$$I_x = V_x \left(\frac{1}{R_S} + \frac{1}{r_o} + g_m \right)$$

$$R_{out} = \frac{V_L}{I_x} = \frac{1}{\frac{1}{R_S} + \frac{1}{r_o} + g_m} = R_S \parallel r_o \parallel \frac{1}{g_m}$$

$$R_{out} = 500 \parallel 20 \parallel 1,59 = 19,23 \parallel 1,59 \Rightarrow R_{out} = 1,47 \text{ k}\Omega$$

↓ black box model of ampl.

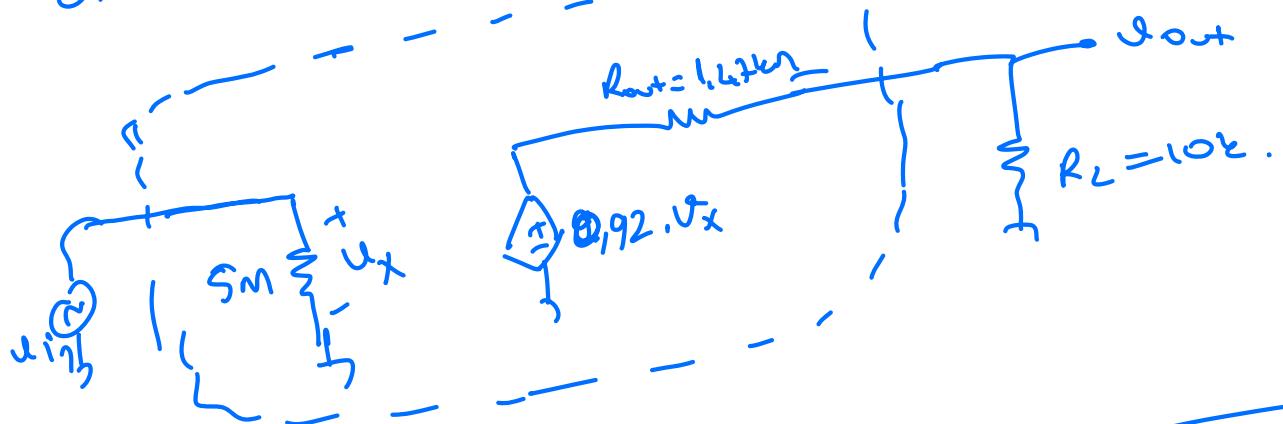


No source resistance $V_{in} = V_x$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_L}{R_L + R_{out}} \cdot 0,92 = \frac{10}{10 + 1,47} \cdot 0,92 \Rightarrow A_V = 0,8 \frac{V}{V}$$


$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_L}{R_L + R_{out}} \cdot 0,92 = \frac{10}{10 + 1,47} \cdot 0,92$$

Note: you would get the same result if R_L was included in part b
then gain would be. $A_V = \frac{g_m (R_L \parallel R_S \parallel R_L)}{1 + g_m (R_L \parallel R_S \parallel R_L)}$

4)

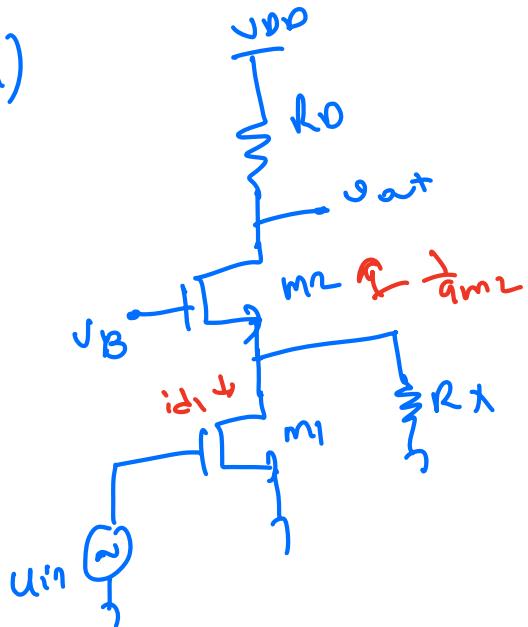

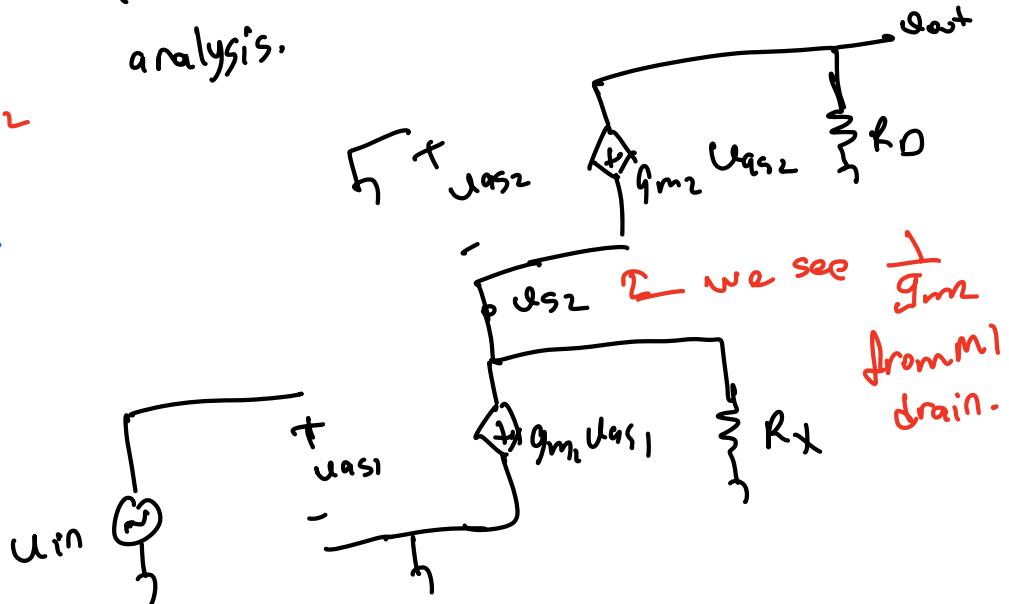m_1 and m_2 are assumed to be in SAT.
 $\gamma = 0$, no values here just symbolic analysis.



$$U_{in} = U_{AS1}$$

$$U_{out} = -g_{m2} U_{AS2} R_D$$

$$U_{AS2} = U_g - U_{S2} = -U_{S2}$$

$$KCL @ V_{S2}$$

$$g_{m1} U_{AS1} + \frac{U_{S2}}{R_X} - g_{m2} U_{AS2} = 0$$

$$g_{m1} U_{in} + \frac{U_{S2}}{R_X} + g_{m2} U_{S2} = 0$$

$$g_{m1} U_{in} = -U_{S2} \left(\frac{1}{R_X} + g_{m2} \right)$$

$$U_{S2} = \frac{-g_{m1}}{\frac{1}{R_X} + g_{m2}} U_{in} \quad \text{--- } \textcircled{*}$$

the gain is \leftarrow
 since when $U_{in} \uparrow$
 $iD1 \uparrow$ and $U_{out} \downarrow$
 $iD1 \uparrow$ to inversion.
 $iD1 \uparrow$ to inversion.

$$U_{out} = g_{m2} U_{S2} R_D$$

using $\textcircled{*}$

$$AV = \frac{U_{out}}{U_{in}} = -g_{m2} R_D \cdot \frac{g_{m1}}{\frac{1}{R_X} + g_{m2}}$$

$$AV = -g_{m2} R_D \cdot \frac{g_{m1} R_X}{1 + g_{m2} R_X}$$


short solution.

$iD1 = g_{m1} U_{in}$
 $iD1$ is divided between $\frac{1}{g_{m2}}$ and R_X
 and converted into voltage through R_D .

$$U_{out} = -g_{m1} R_D \frac{\frac{R_X}{R_X + g_{m2}} \cdot R_D}{g_{m2} \leftarrow \text{current division.}}$$

$$\frac{U_{out}}{U_{in}} = -g_{m1} R_D \frac{g_{m2} R_X}{1 + g_{m2} R_X} \rightarrow \text{same result.}$$

5)

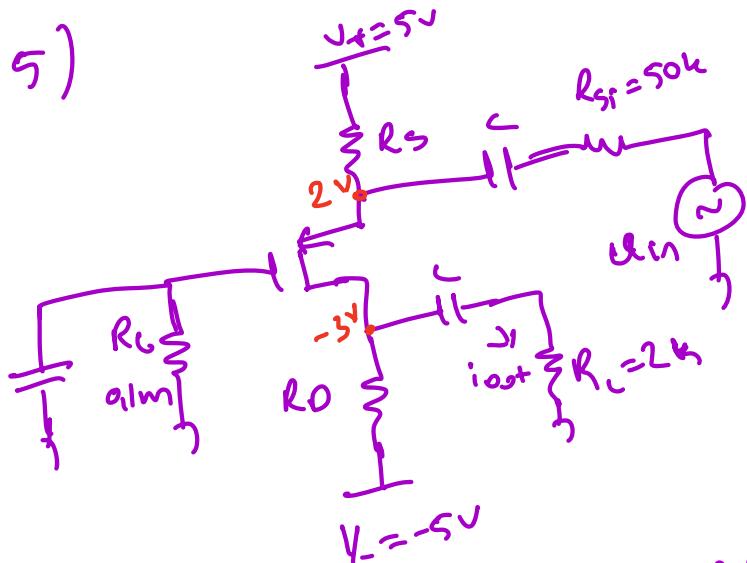

$$V_{Dp} = -1V \quad k_p = 0.5 \text{ mA/V}^2, N=0$$

$$a) I_{DQ} = 0.5 \text{ mA} \quad V_{SDQ} = 5V$$

$$V_{SD} + (R_s + R_D) I_D = 10V$$

$$(R_s + R_D) \cdot 0.5 = 5$$


$$R_s + R_D = 10k$$

$$0.5 = 0.5 \left(\frac{5 - R_s \cdot 0.5 - 0 - 1}{V_S} \right)^2$$

$$V_S - 1 = \pm 1 \quad V_S = 2V$$

$$R_s = 6k \quad R_D = 4k$$

b)

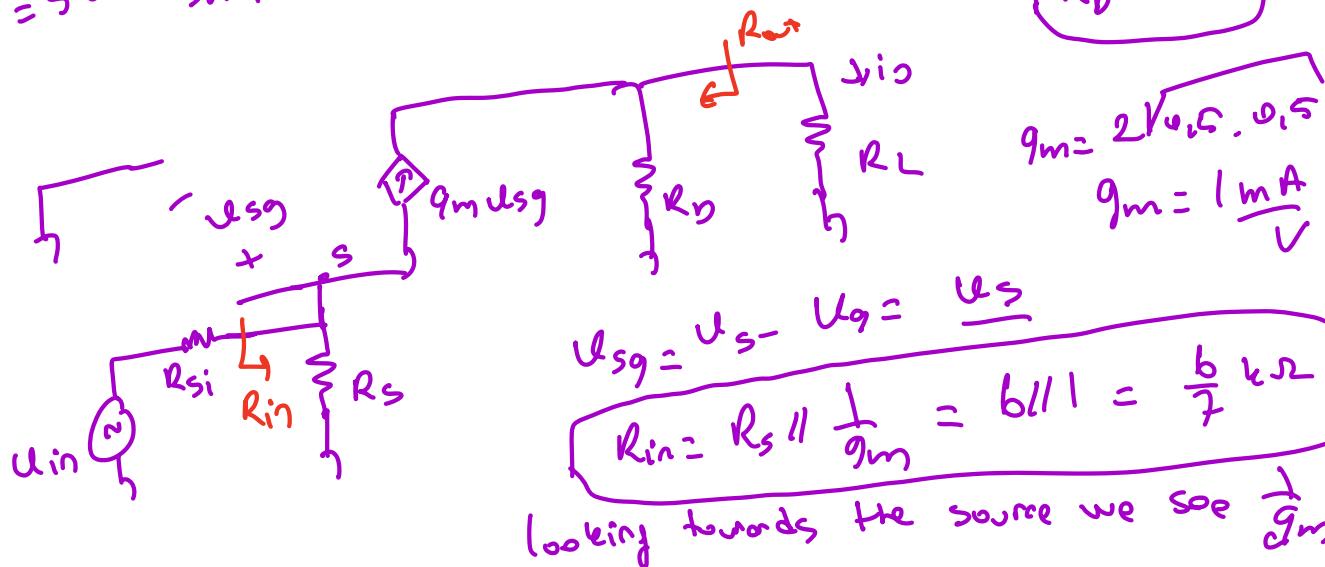

Rout kill din.

$$U_S = -g_m U_{SG} (R_S || R_{SI})$$

$$U_{SG} = U_S$$

$$U_S = -g_m U_S (R_S || R_{SI})$$


$$(U_S = 0)$$

$$\text{or } g_m = -\frac{1}{R_S || R_{SI}}$$


so $g_m U_{SG} = 0$ open ckt.

$$R_{out} = R_D = 4k\Omega$$

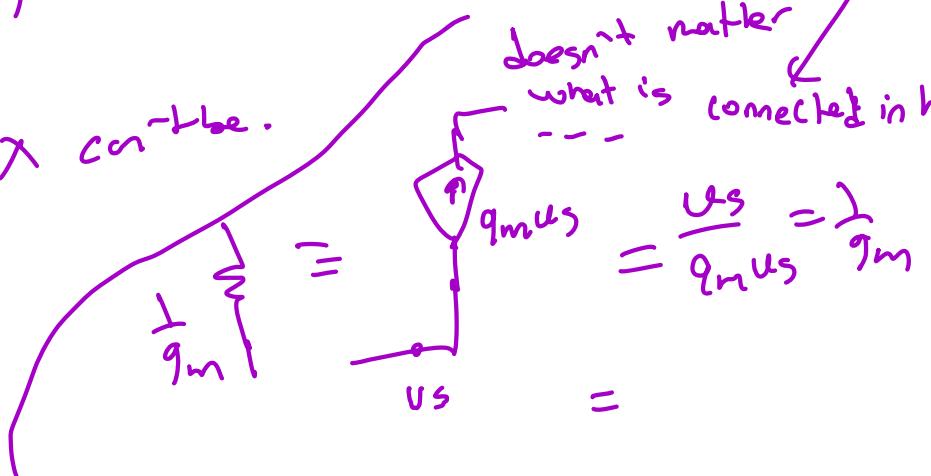doesn't matter
what is connected in here.



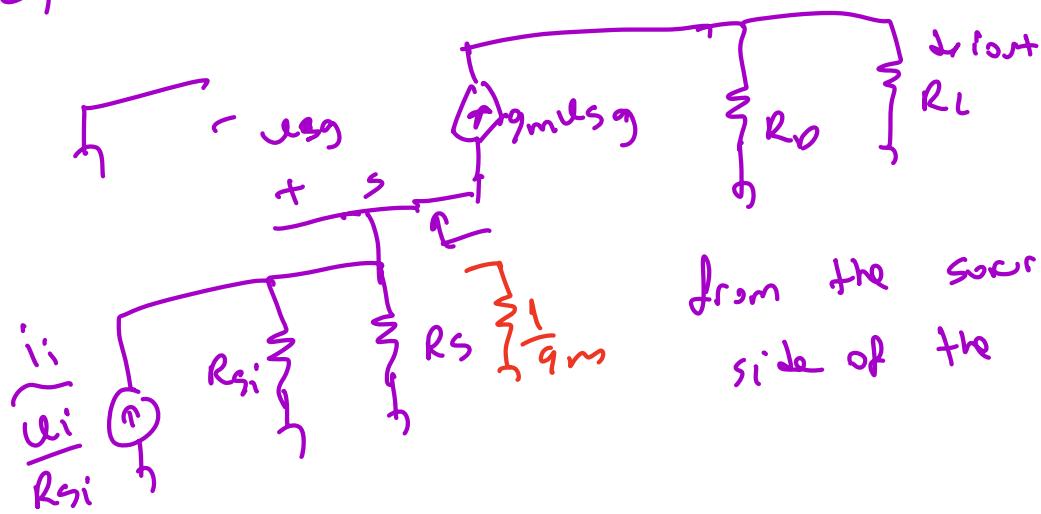c) since the output is current let's work in terms of current.



from the source side the drain side of the ckt seems like $\frac{1}{gm}$.

$$\frac{i_o}{i_i} = \frac{R_{si} \parallel R_s}{R_{si} \parallel R_s + \frac{1}{gm}} \cdot \frac{\frac{R_d}{R_d + R_L}}{\text{current division at the output}}$$

Current of flowing to the drain
gm

$$i_o = \frac{R_{si} \parallel R_s}{R_{si} \parallel R_s + \frac{1}{gm}} \cdot \frac{\frac{R_d}{R_d + R_L}}{\frac{U_i}{R_{si}}} \cdot i_i \quad \text{in terms of } i_i$$

$$i_o = \frac{50 \parallel b}{50 \parallel b + 1} \cdot \frac{1}{4+2} \cdot i_i$$

$$i_o = \frac{5.35}{5.35+1} \cdot \frac{2}{3} \cdot i_i \Rightarrow i_o = 0.56 i_i$$

$$i_o = 0.56 \cdot \frac{0.5 \cos \omega t}{50 k}$$

$$i_o = 5.6 \cdot \cos \omega t \text{ A}$$


$$V_o = i_o \cdot R_L = 11.2 \cos \omega t \text{ V}$$

very small voltage gain.

$$\frac{i_o}{i_i} = 0.0224 \frac{A}{V}$$

$i_o = g_m j_s (R_d \parallel R_L)$
 $j_s = \frac{1/gm \parallel R_s}{1/gm \parallel R_s + R_{si}} \cdot \frac{1}{50k}$
 $R_{si} \gg gm \text{ the NOSAGE with the NOSAGE open.}$

6)

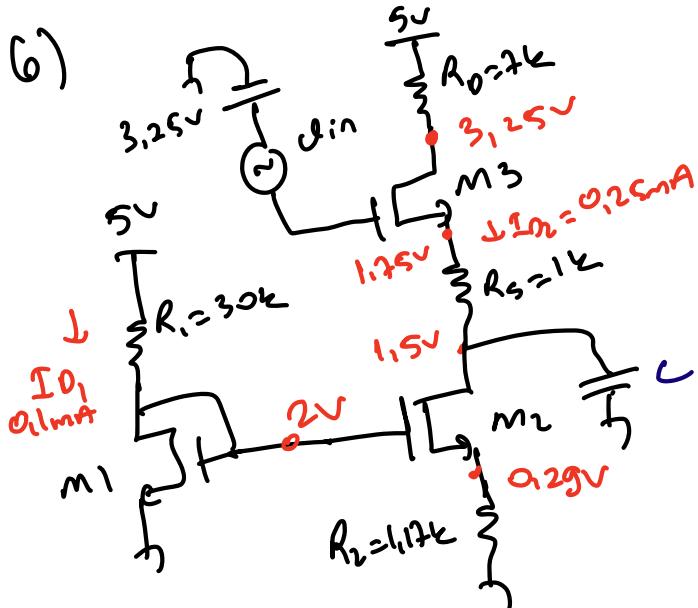

$$\underline{M2} \quad V_{DS2} = 1.17 I_{D2}$$

$$I_{D2} = 0.15 (2 - 1.17 I_{D2} - 1)^2$$

$$2 I_{D2} = (1 - 1.17 I_{D2})^2$$

$$2 I_{D2} = 1 - 2.34 I_{D2} + 1.17^2 I_{D2}^2$$

$$I_{D2} = 2.92 \text{ mA} \times V_{DS2} \leq I_{Dn}$$

$$I_{D2} = 0.25 \text{ mA}$$

$$V_{DS2} = 0.25 \cdot 1.17 = 0.29 \text{ V}$$

$$\underline{M3}: \quad I_{D2} = I_{D3} = 0.25 \text{ mA}$$

$$0.25 = 1 (V_{GS3} - 1)^2$$

$$V_{GS3} = 1 = \pm 0.5$$

$$V_{GS3} = 1.5 \text{ V}$$

$$V_{GS3} = 3.25 \text{ V}$$

$$V_{GS3} = 1.75 \text{ V}$$

$$V_{GS1} = 0.1 \text{ mA/V}^2 \quad k_{m1} = 0.5 \text{ mA/V}^2$$

$$k_{m2} = 1 \text{ mA/V}^2 \quad V_{th} = 1 \text{ V}, \quad \alpha = 0$$

a) M_1 is in SAT. $V_{GS1} = V_{DS1}$,

$$V_{GS1} = 5 - 30 I_{D1}$$

$$I_{D1} = 0.1 \cdot (5 - 30 I_{D1} - 1)^2$$

$$10 I_{D1} = (4 - 30 I_{D1})^2$$

$$10 I_{D1} = 16 - 240 I_{D1} + 900 I_{D1}^2$$

$$900 I_{D1}^2 - 250 I_{D1} + 16 = 0$$

$$I_{D1} = 0.18 \text{ mA} \quad \times \quad V_{GS1} \leq V_{th}$$

$$V_{GS1} = 2 \text{ V}$$


$$\boxed{I_{D1} = 0.1 \text{ mA}}$$

$$\underline{M1}: \quad V_{DS1} = V_{GS1} \quad \text{SAT} \checkmark$$

$$\underline{M2} \quad V_{D2} \geq V_{GS2} - 1 \quad \text{SAT} \checkmark$$

$$\underline{M3} \quad V_{D3} \geq V_{GS3} \quad \text{SAT} \checkmark$$

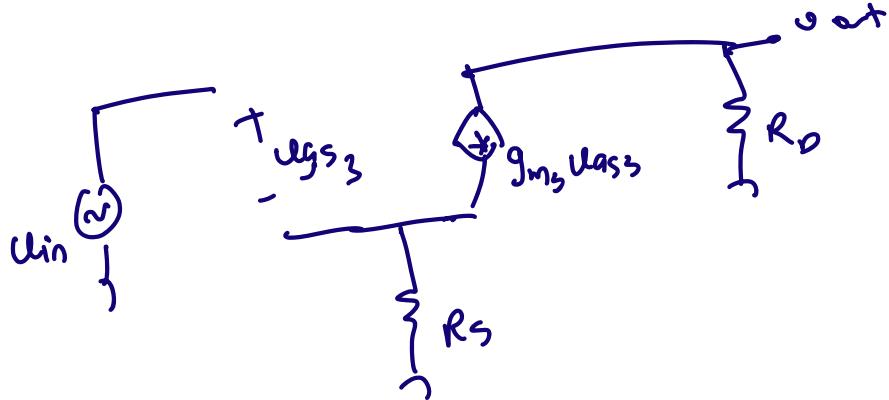b) for small signal C grounds the drain of m₂
so the ckt simplifies to



$$g_m = 2\sqrt{I \cdot 0,25}$$

$$g_m = 1 \text{ mA/V}$$

$$u_{out} = -g_{m3} u_{gs3} R_D$$

$$u_{in} = u_{gs3} + g_{m3} u_{gs3} R_S$$

$$A_v = \frac{u_{out}}{u_{in}} = \frac{-g_{m3} R_D}{1 + g_{m3} R_S}$$

$$A_v = \frac{-1 \cdot 7}{1 + 1 \cdot 1} = -3,5 \text{ V/V}$$

m₂ does not matter because C grounds the drain of m₂.
all the small signal current flows through C to ground w/o
passing through m₂.